

CSEE 3827: Fundamentals of Computer Systems, Spring 2022

Lecture 4

Prof. Dan Rubenstein (danr@cs.columbia.edu)

Agenda (M&K 3.1-3.12, 8.4)

- **Combinatorial Circuit Design**

- Multi-bit output functions
- Standard combinatorial circuits
 - enabler
 - decoder
 - MUX (multiplexer)
 - shifter
 - Code converter
 - Addition / Subtraction
 - half and full adders
 - ripple carry adder
 - carry lookahead adder

Quick Review: K-map with don't care conditions

← Input → Output

$f(W,X,Y,Z)$:

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Quick Review: K-map with don't care conditions

← Input → Output

$f(W,X,Y,Z)$:

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

As Minterms:

$\overline{W}\overline{X}\overline{Y}Z +$

$\overline{W}\overline{X}\overline{Y}\overline{Z} +$

$\overline{W}\overline{X}Y\overline{Z} +$

$\overline{W}XY\overline{Z} +$

$\overline{W}\overline{X}Y\overline{Z} +$

$W\overline{X}\overline{Y}\overline{Z} +$

$W\overline{X}\overline{Y}Z +$

Could optionally include
Don't Cares

Quick Review: K-map with don't care conditions

← Input → Output

$f(W,X,Y,Z)$:

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

As Minterms:

$\overline{W}XYZ + \overline{W}X\overline{Y}Z + \overline{W}XY\overline{Z} + WXY\overline{Z}$

$\overline{W}\overline{X}YZ + \overline{W}\overline{X}Y\overline{Z} + \overline{W}\overline{X}Y\overline{Z} + W\overline{X}Y\overline{Z}$

Could optionally include
Don't Cares

WXY

Quick Review: K-map with don't care conditions

← Input → Output

$f(W,X,Y,Z)$:

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

As Minterms:

$\overline{W}XYZ +$

$\overline{W}X\overline{Y}\overline{Z} +$

$\overline{W}X\overline{Y}Z +$

$\overline{W}XYZ +$

$\overline{W}\overline{X}YZ +$

$\overline{W}\overline{X}Y\overline{Z} +$

$\overline{W}XY$

$X\overline{Y}$

Could optionally include
Don't Cares

$\overline{W}XY$

Quick Review: K-map with don't care conditions

$f(W, X, Y, Z)$:

What
about
 X ?

covers a 0,
can't use as
product term

← Input → Output

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

As Minterms:

$\overline{W}XYZ +$

$\overline{W}X\overline{Y}\overline{Z} +$

$\overline{W}X\overline{Y}Z +$

$\overline{W}XYZ +$

$\overline{W}\overline{X}YZ +$

$\overline{W}\overline{X}\overline{Y}Z +$

$\overline{W}X\overline{Y}$

$X\overline{Y}$

Could optionally include
Don't Cares

$\overline{W}XY$

Quick Review: K-map with don't care conditions

$f(W, X, Y, Z)$:

What about \bar{Y} ?

covers a 0,
can't use as
product term

← Input → Output

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

As Minterms:

$\overline{W}XYZ +$

$\overline{W}X\overline{Y}\overline{Z} +$

$\overline{W}X\overline{Y}Z +$

$\overline{W}XYZ +$

$\overline{W}\overline{X}YZ +$

$\overline{W}\overline{X}\overline{Y}Z +$

$\overline{W}X\overline{Y}$

$X\overline{Y}$

Could optionally include
Don't Cares

$\overline{W}XY$

Quick Review: K-map with don't care conditions

$f(W, X, Y, Z)$:

What about \bar{Y} ?

covers a 0,
can't use as
product term

$X\bar{Y}$ is a prime
implicant

← Input → Output

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

As Minterms:

$\bar{W}XYZ +$

$\bar{W}X\bar{Y}\bar{Z} +$

$\bar{W}X\bar{Y}Z +$

$\bar{W}XYZ +$

$W\bar{X}\bar{Y}\bar{Z} +$

$W\bar{X}\bar{Y}Z +$

$\bar{W}XY$

$X\bar{Y}$

Could optionally include
Don't Cares


$\bar{W}XY$

Quick Review: K-map with don't care conditions


← Input → Output

$f(W, X, Y, Z)$:

W	X	Y	Z	f
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

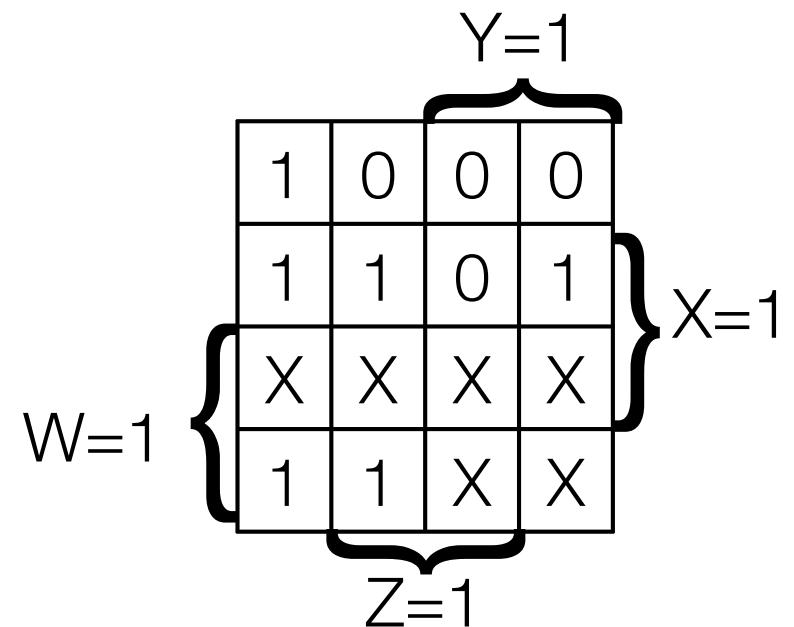

Algebra and Circuit for “f”

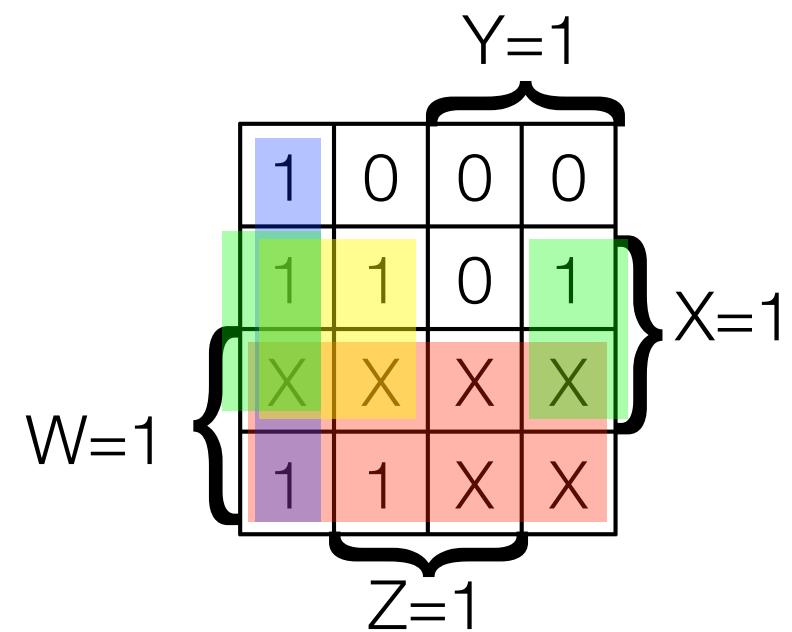

Algebra and Circuit for “f”


A Karnaugh map for four variables (W, X, Y, Z) showing the function $f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$. The map is a 4x4 grid with columns labeled X=1 and columns labeled X=0. Rows are labeled Y=1 and Y=0. The cells are colored based on their values in the algebraic expression:

	X=1	X=0	
Y=1	1	0	0 0
Y=0	1 1	0 1	
W=1	X X X X		
Z=1	1 1 X X		


The cells are colored as follows: Top row (Y=1): Blue (1), White (0), White (0), White (0). Second row (Y=0): Green (1), Yellow (1), White (0), Green (1). Third row (W=1): Green (X), Orange (X), Red (X), Green (X). Bottom row (Z=1): Purple (1), Red (1), Red (X), Red (X).

$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$


Algebra and Circuit for “f”

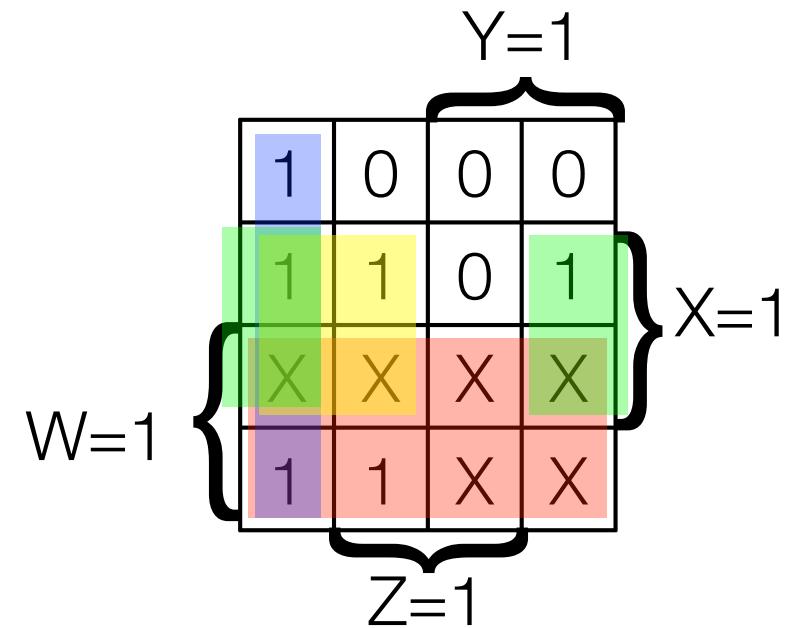

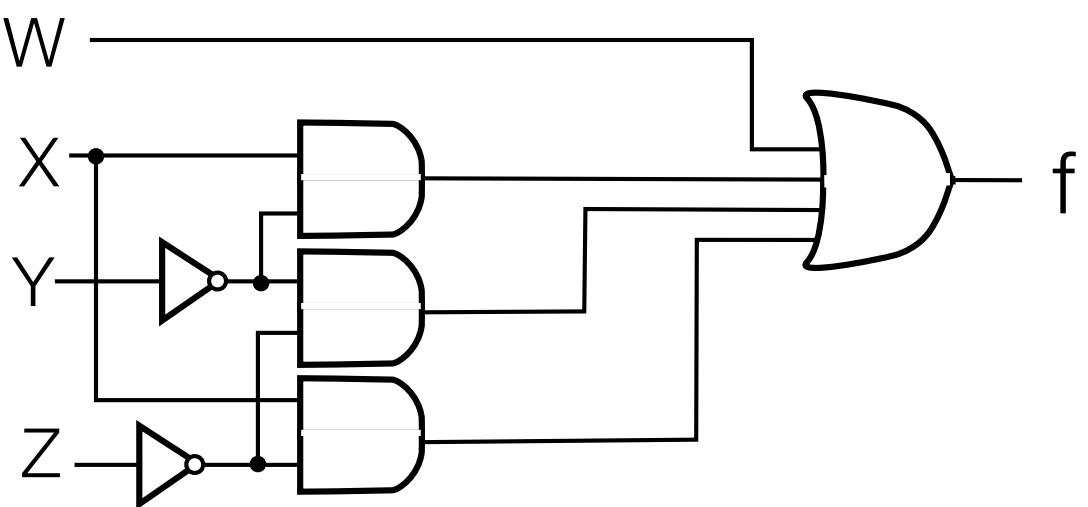
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$



Algebra and Circuit for “f”

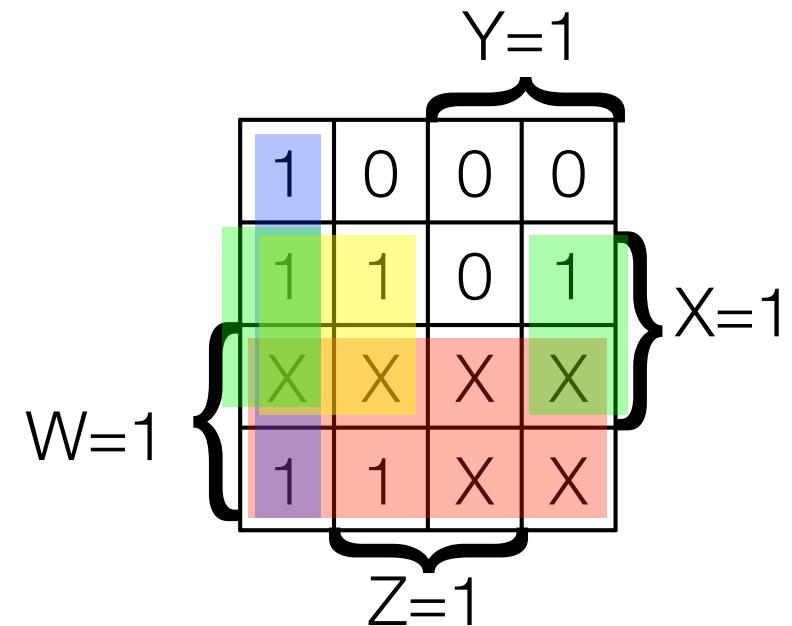

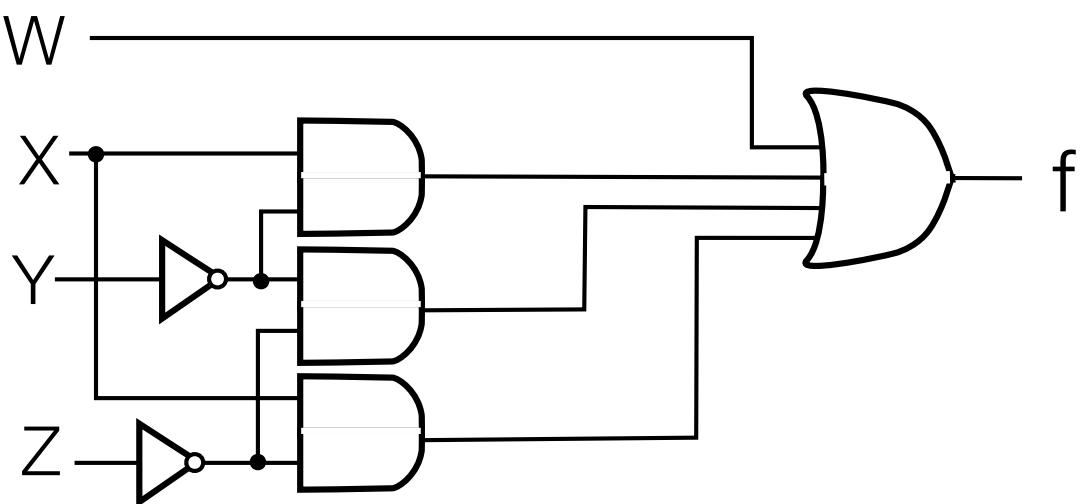
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$





Note $X\bar{Y}$ is essential PI: only PI that covered $\bar{W}X\bar{Y}Z$

So are the other terms ($W, \bar{Y}\bar{Z}, X\bar{Z}$)

Algebra and Circuit for “f”

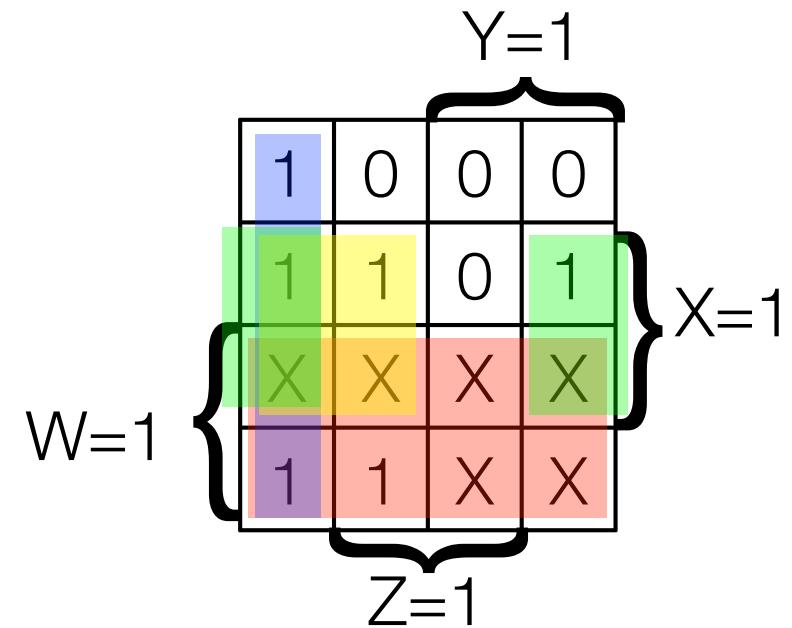

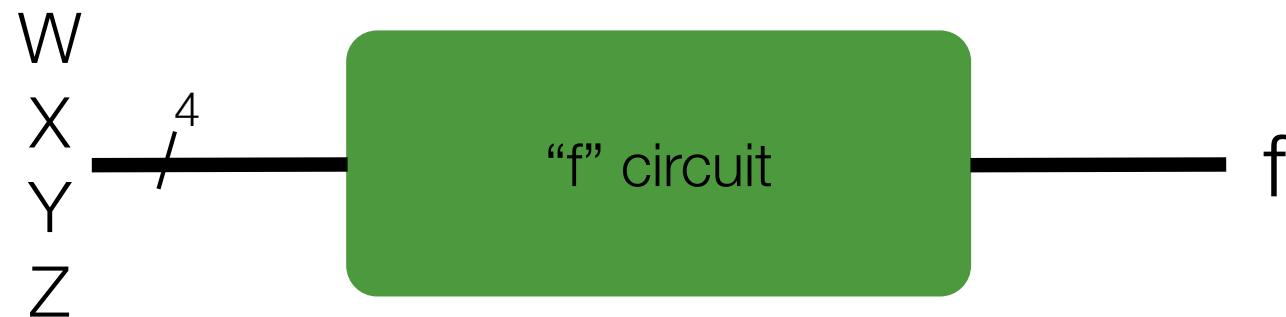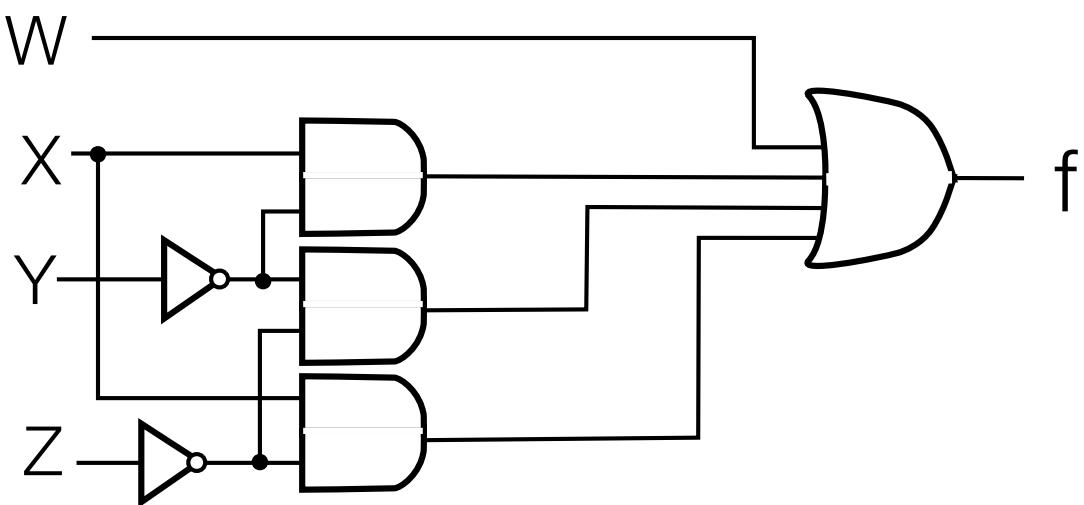
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$



When we know the internals, we can simplify our picture of the circuit (i.e., with a labelled box)

Input Flow... circuit needs time to stabilize
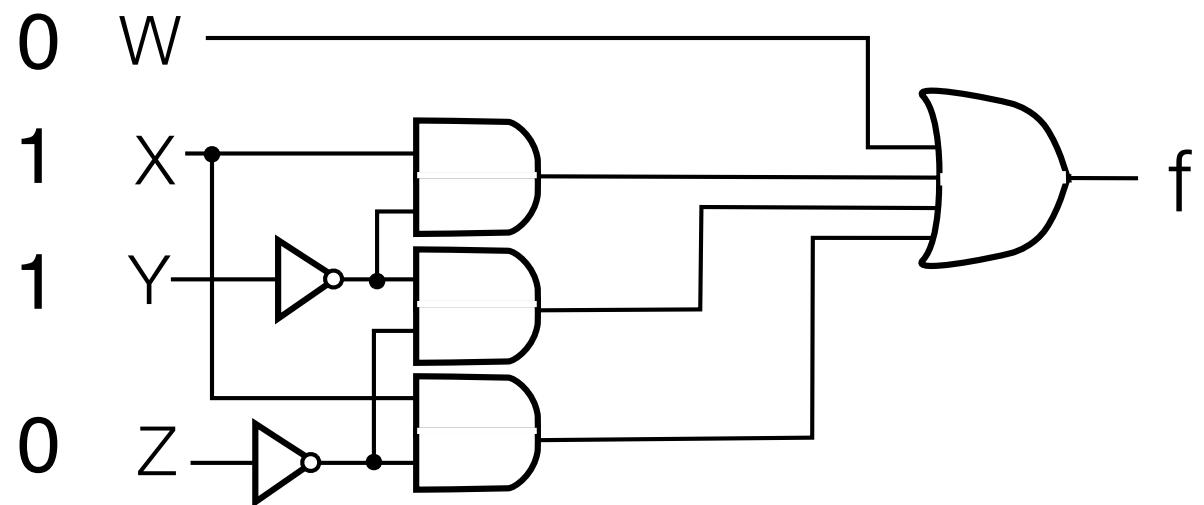
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
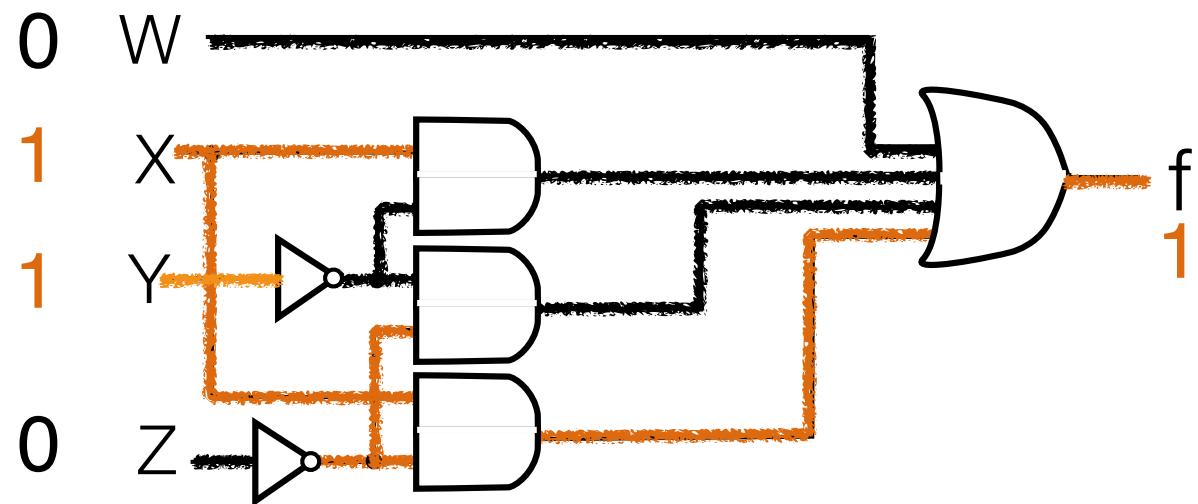
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
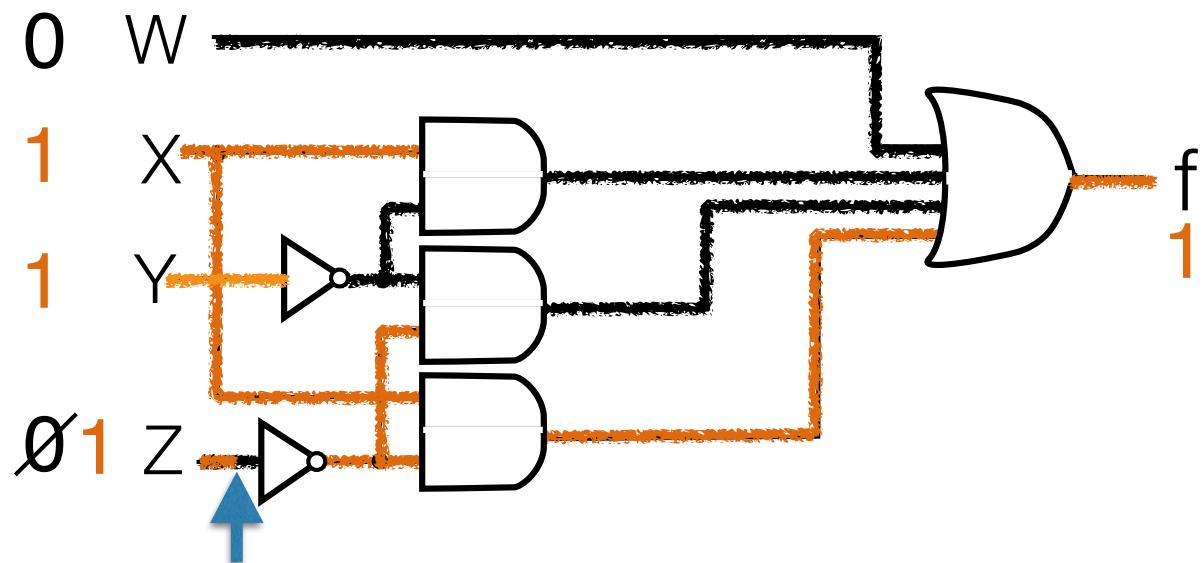
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Updated info ($Z=1$) starts to flow quickly down wire (speed of light)...

Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
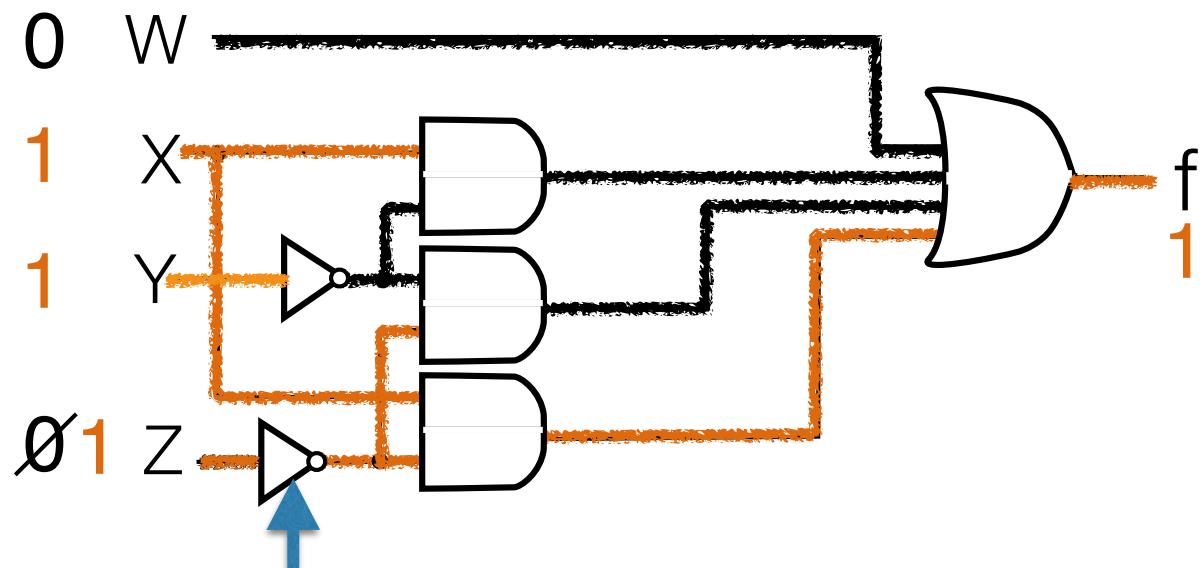
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Reaches NOT gate, takes a bit of time to come out the other side...

Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
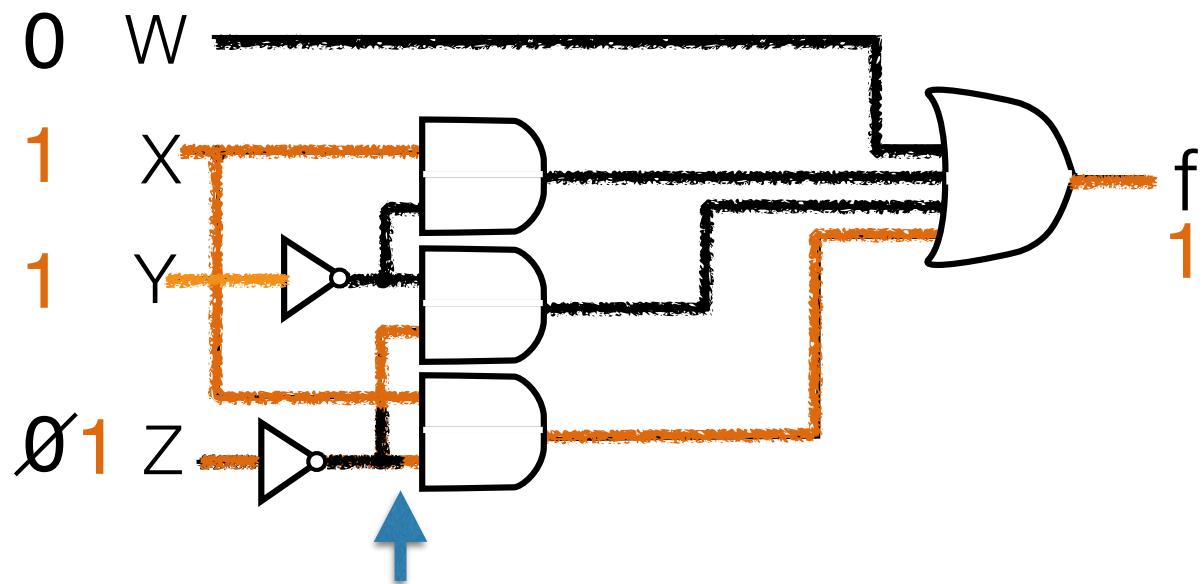
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Down the next wire (quickly)

Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
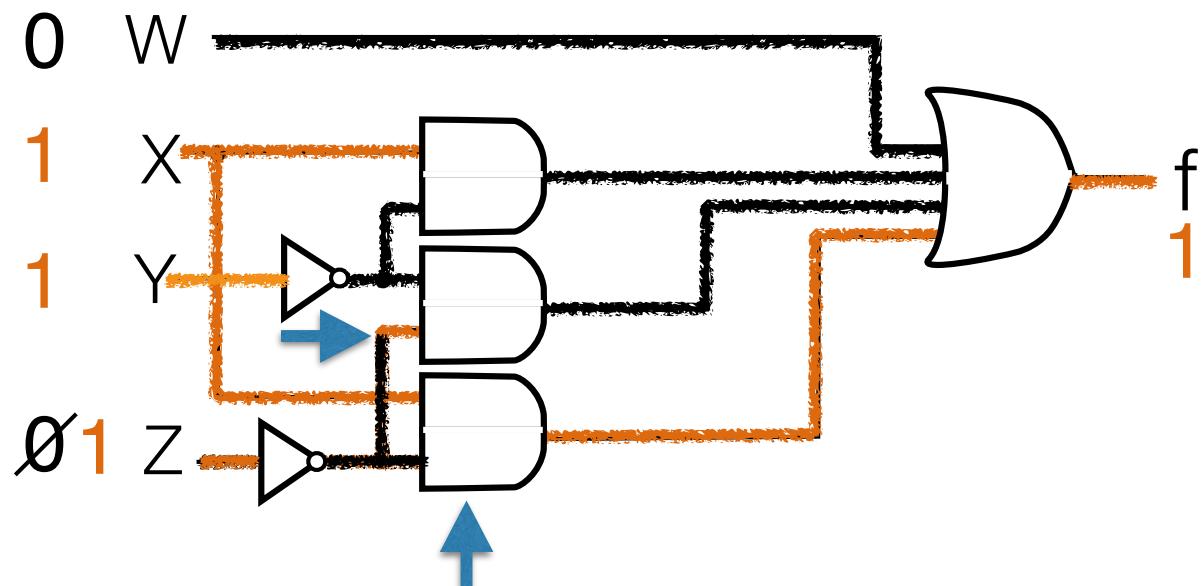
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




In one gate (for a while), almost to other gate

Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
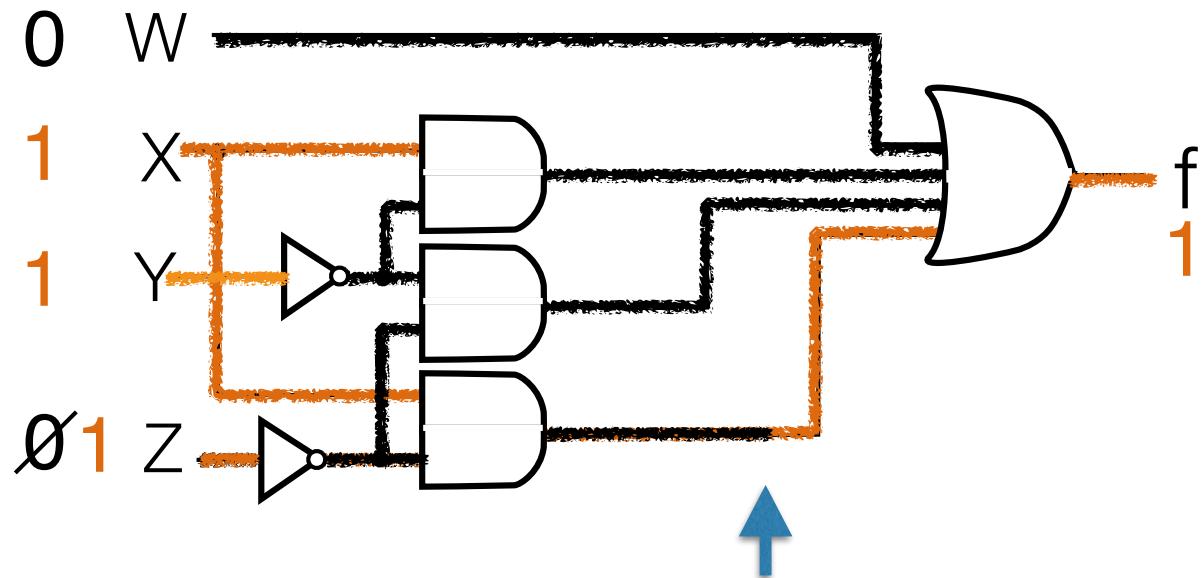
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Out the bottom gate, for the top gate, the output won't change (output stays 0)

Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
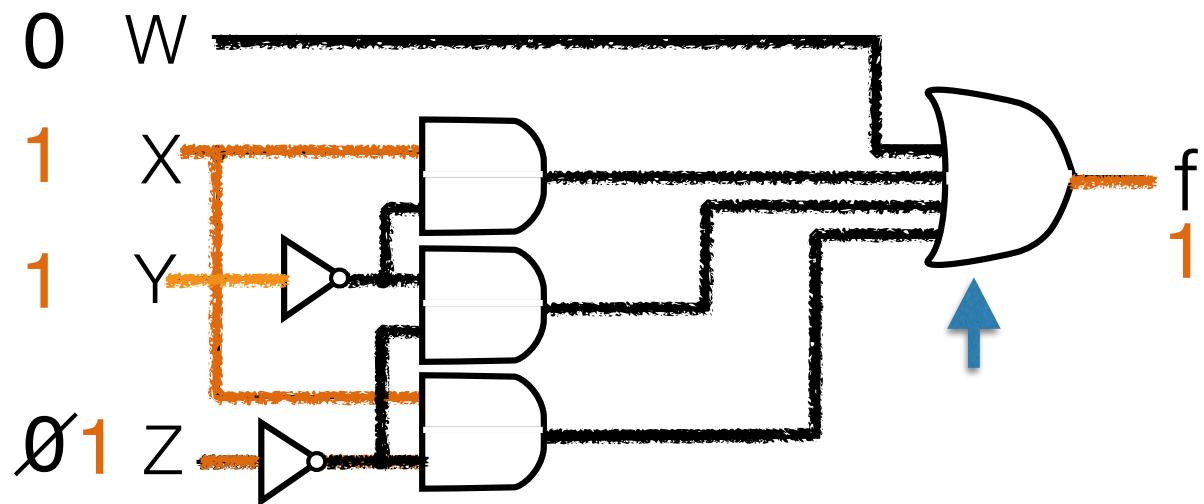
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Enters last gate in the sequence dependent on Z
takes some time (relative to wire speed)

Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"
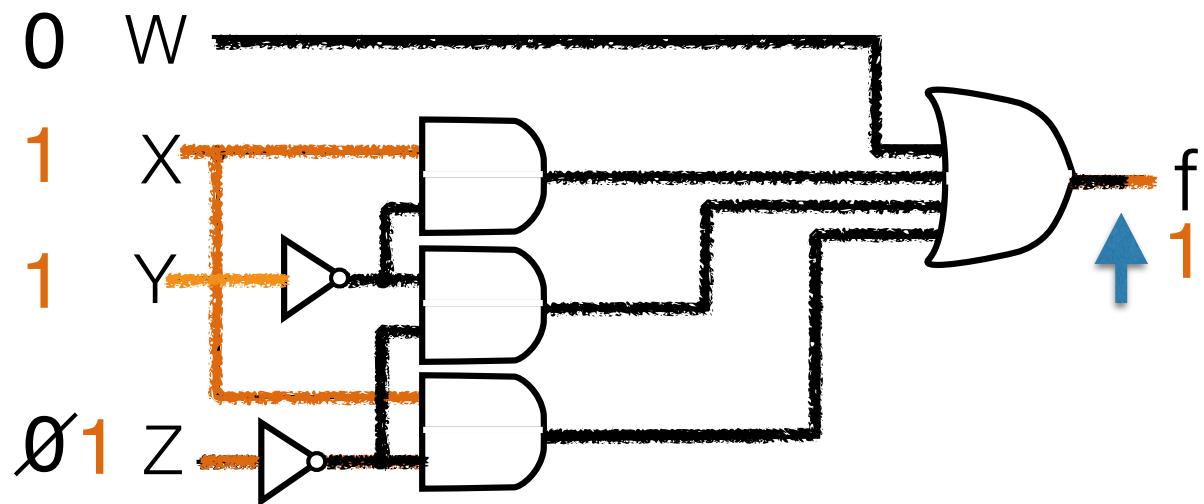
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Finally out the final gate, output soon to change...

Input Flow... circuit needs time to stabilize

Wire carries "0"

Wire carries "1"


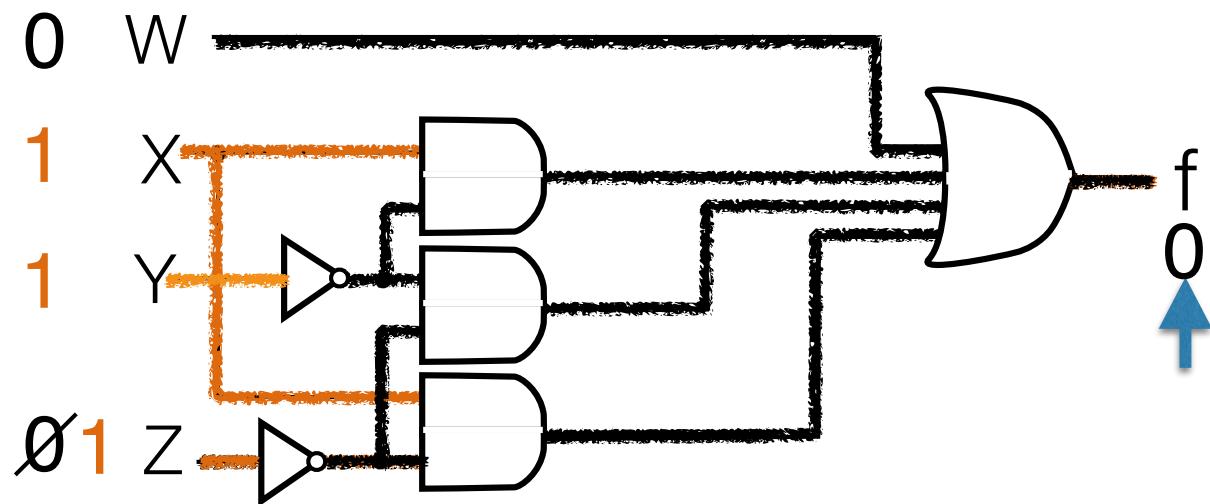
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$



Circuit has "stabilized" - output corresponds to $f(\text{inputs})$

Algebra and Circuit for “f”
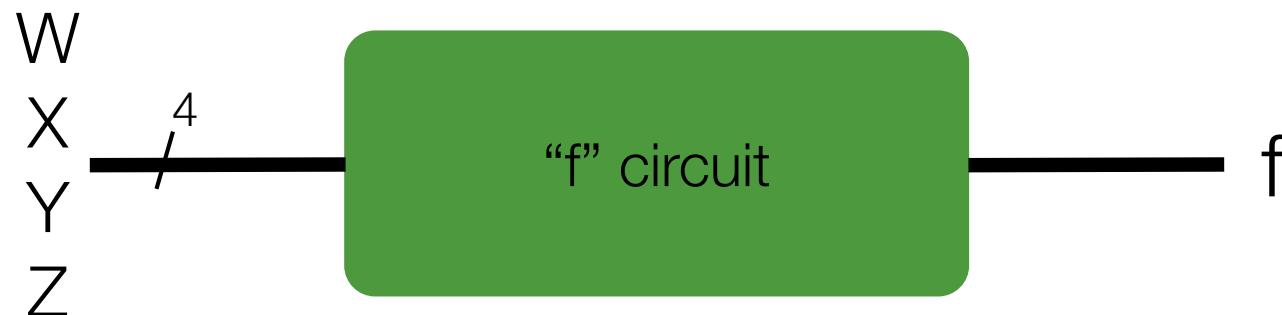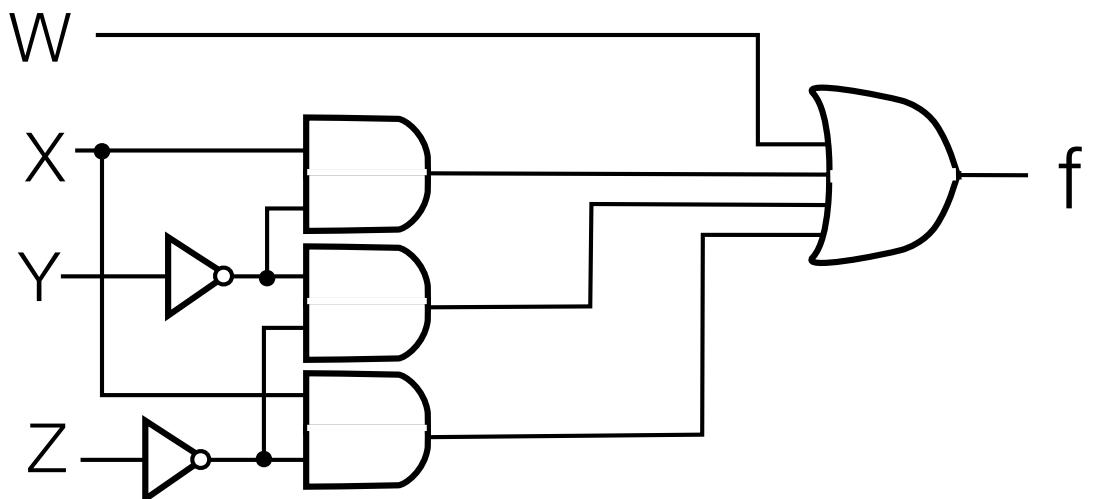
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$



When we use this “box” simplifying representation,
still need to understand how changing inputs takes
time to propagate to output.


Combinational circuits

- Combinational circuits are stateless
- The outputs are functions only of the inputs




Combinational circuits

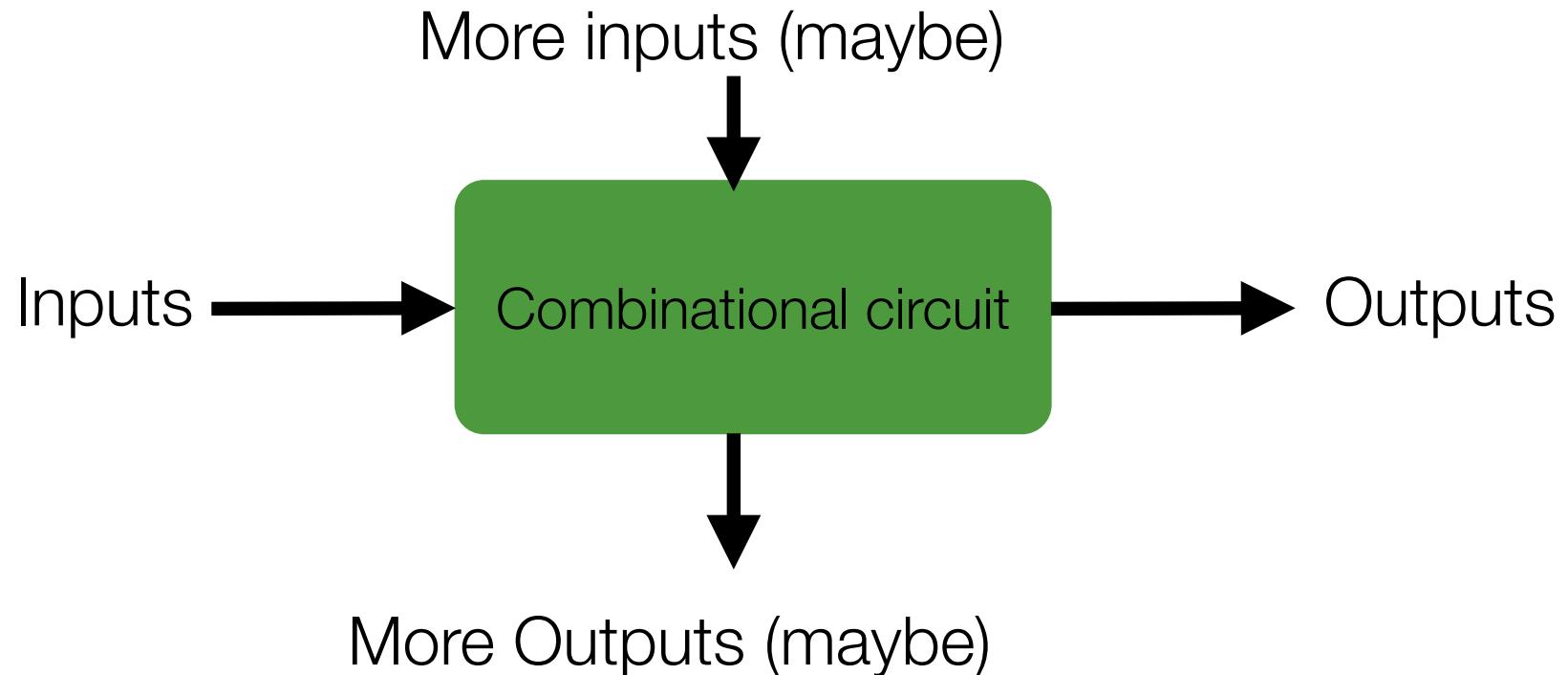- Combinational circuits are stateless
- The outputs are functions only of the inputs



Combinational circuits

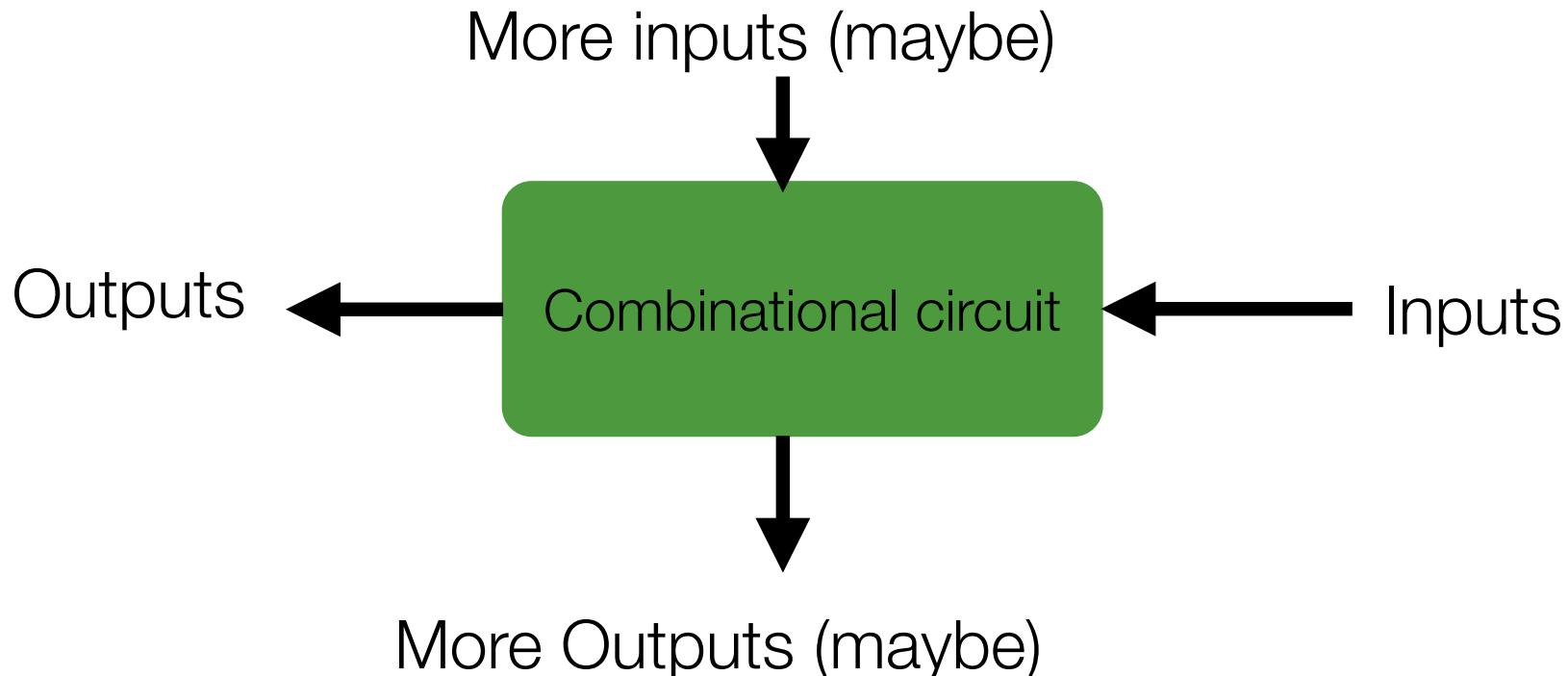
- Combinational circuits are stateless
- The outputs are functions only of the inputs




You can tell what are inputs and what are outputs either
by the arrow directions, or by context (when obvious)

Review: Parallel Multi-wire notation

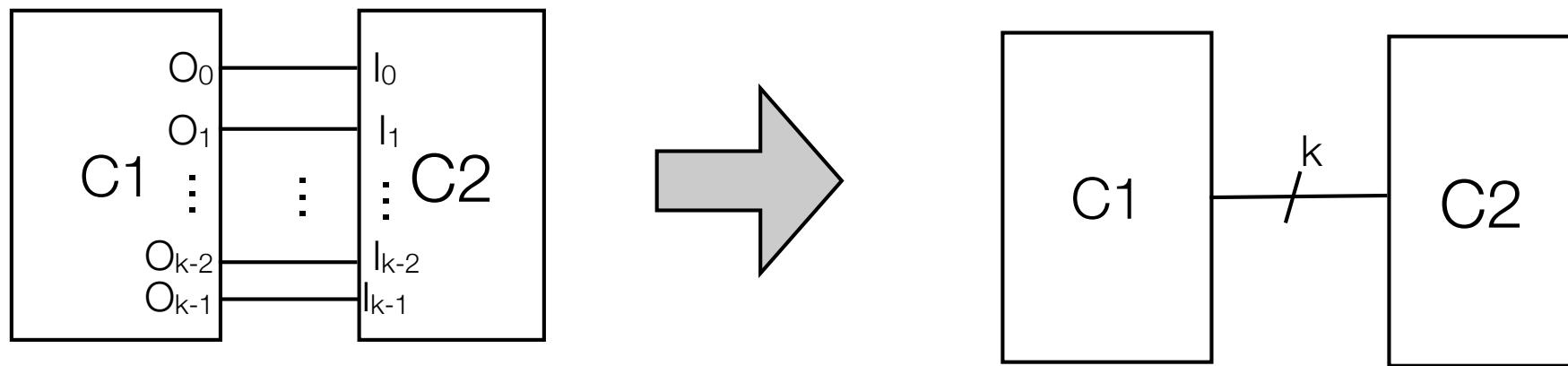- Useful when running a bunch of bits **in parallel** to the same (similar place)



Multi Input and/or Output Circuits

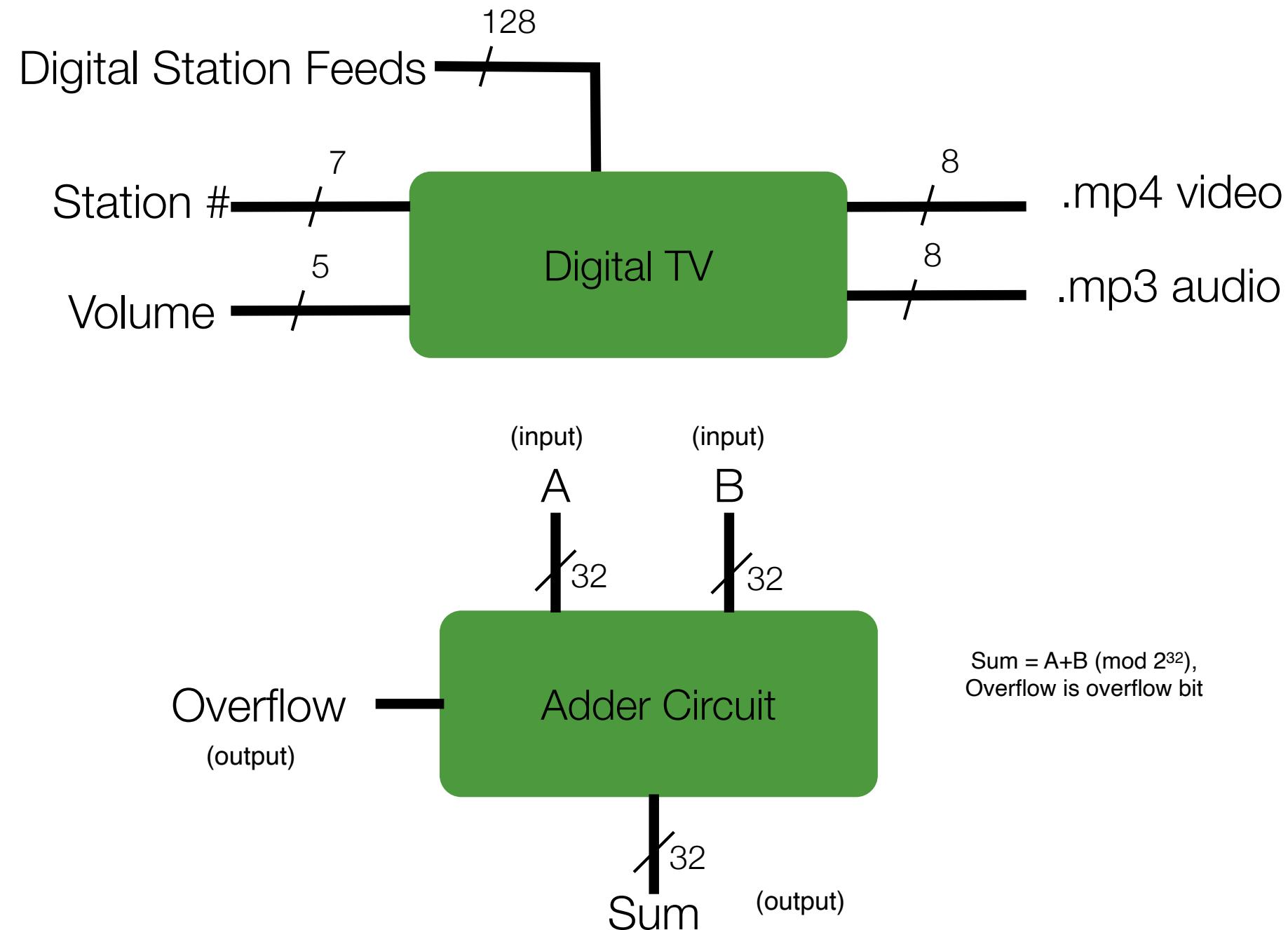


“Standard” Circuits

“Standard Circuits”

- A few types of circuits you will need to become very familiar with
 - how to build
 - how to use
- They are:
 - Enabler
 - Decoder
 - MUX (multiplexer) (also DeMux)
 - (General Purpose) Code Converter
 - Shifter
 - Adder/Subtractor



Enabler Circuit (High-level view):

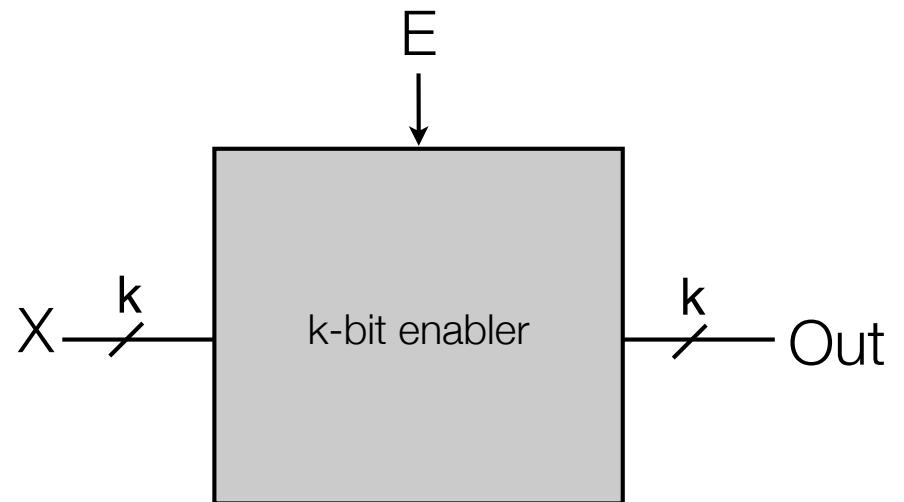- Enabler circuit has 2 inputs
 - data (can be k bits in parallel)
 - enable/disable (i.e., on/off) input
- Output:
 - If $E=1$, output = data input
 - If $E=0$, output = k 0's




Enabler Circuit (High-level view):

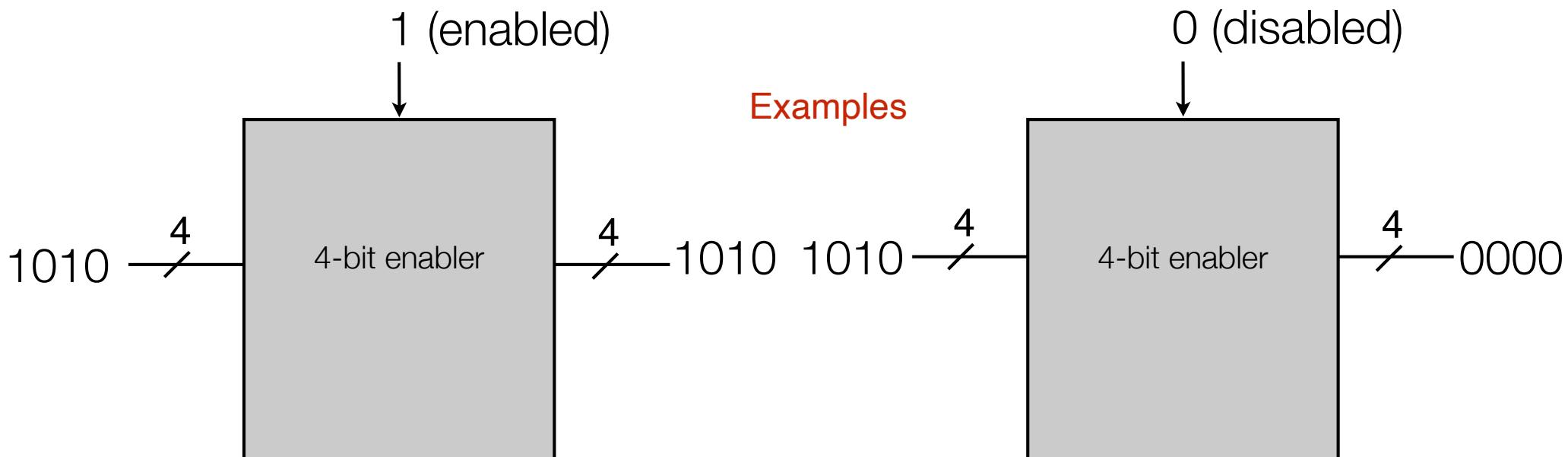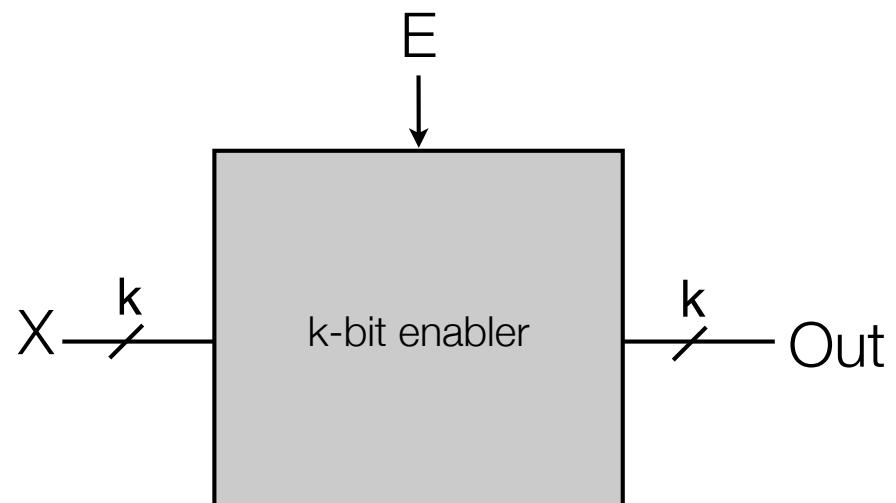- Enabler circuit has 2 inputs
 - data (can be k bits in parallel)
 - enable/disable (i.e., on/off) input
- Output:
 - If $E=1$, output = data input
 - If $E=0$, output = k 0's




Standard Decoder Circuit (high-level view):

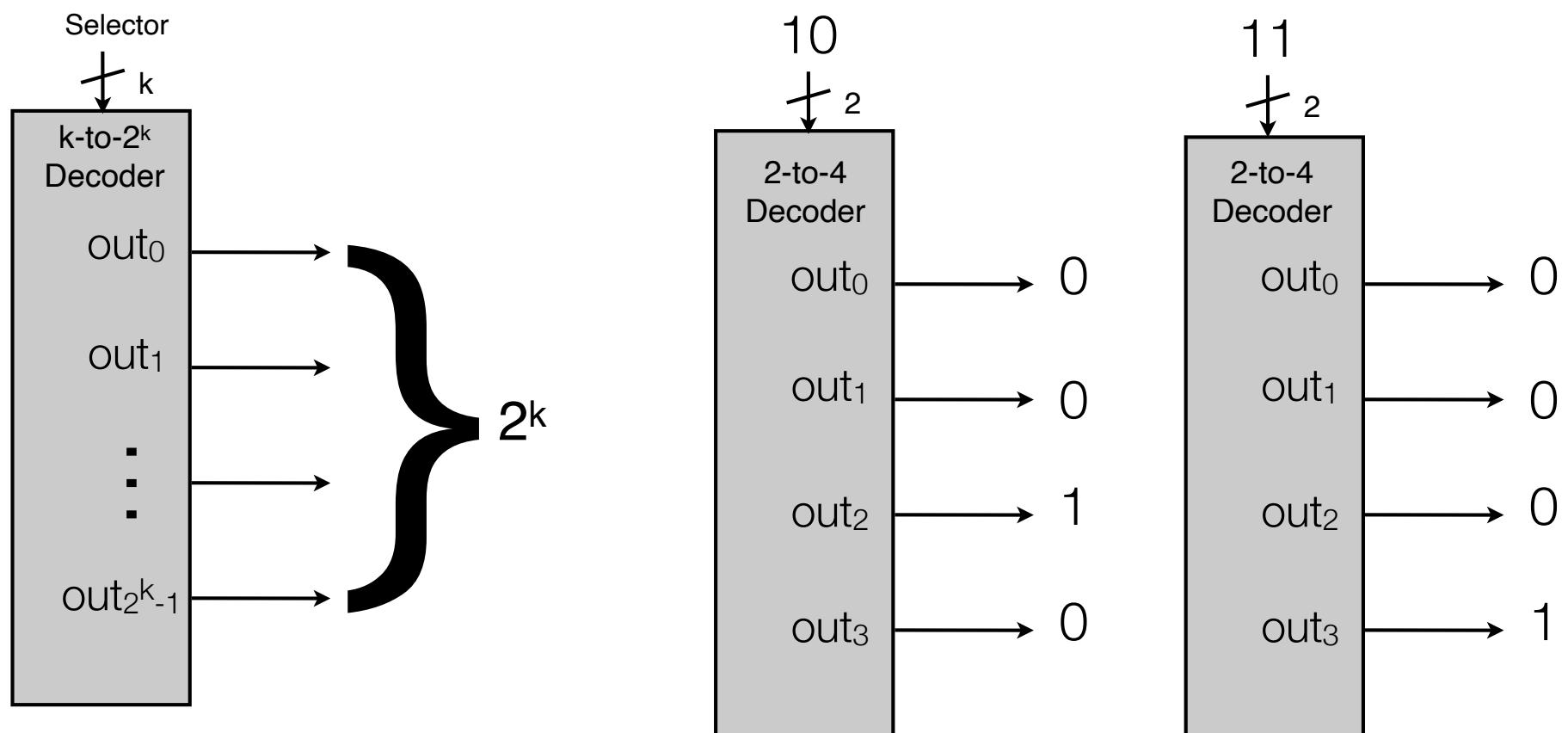- No “DATA” inputs, just a k-bit “selector” input
- 2^k 1-bit outputs
- Selector input chooses which output = 1, all other outputs = 0




Decoder with Enable

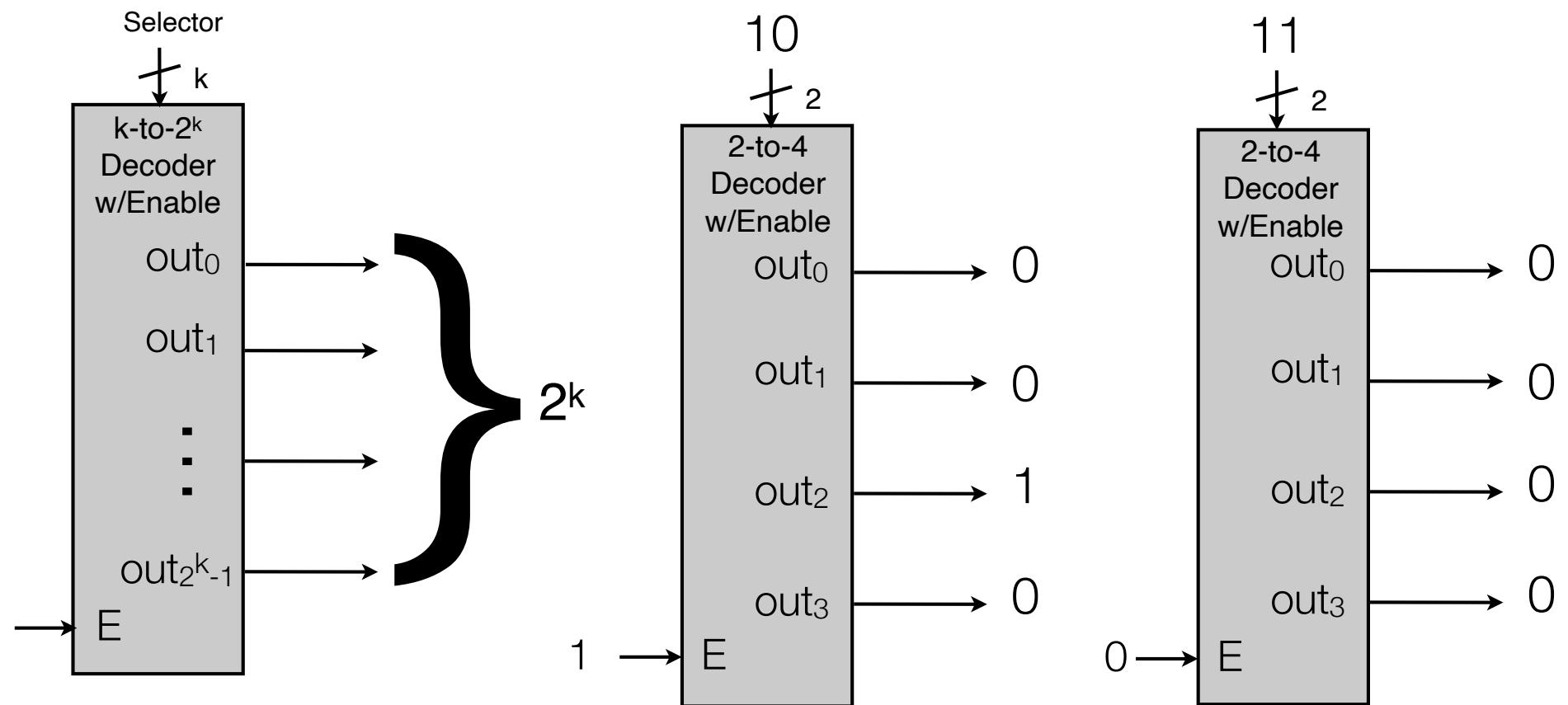- One additional input, E
 - E=1: behaves like standard decoder
 - E=0: all outputs are 0




MUX Circuit (High-level)

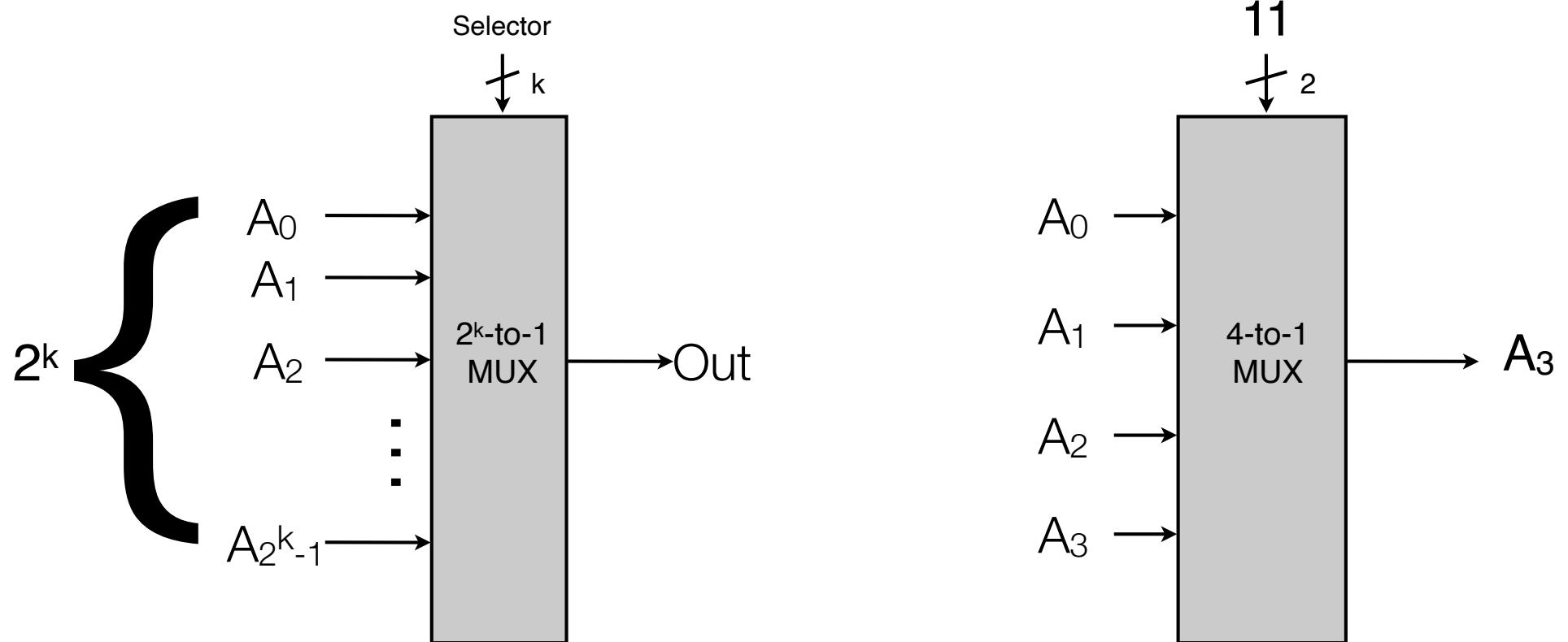- 2^k Data values enter as input
- k-bit selector chooses which one comes out
- Like the A_i are digital music signals (over time) and i chooses the station




MUX Circuit (High-level)

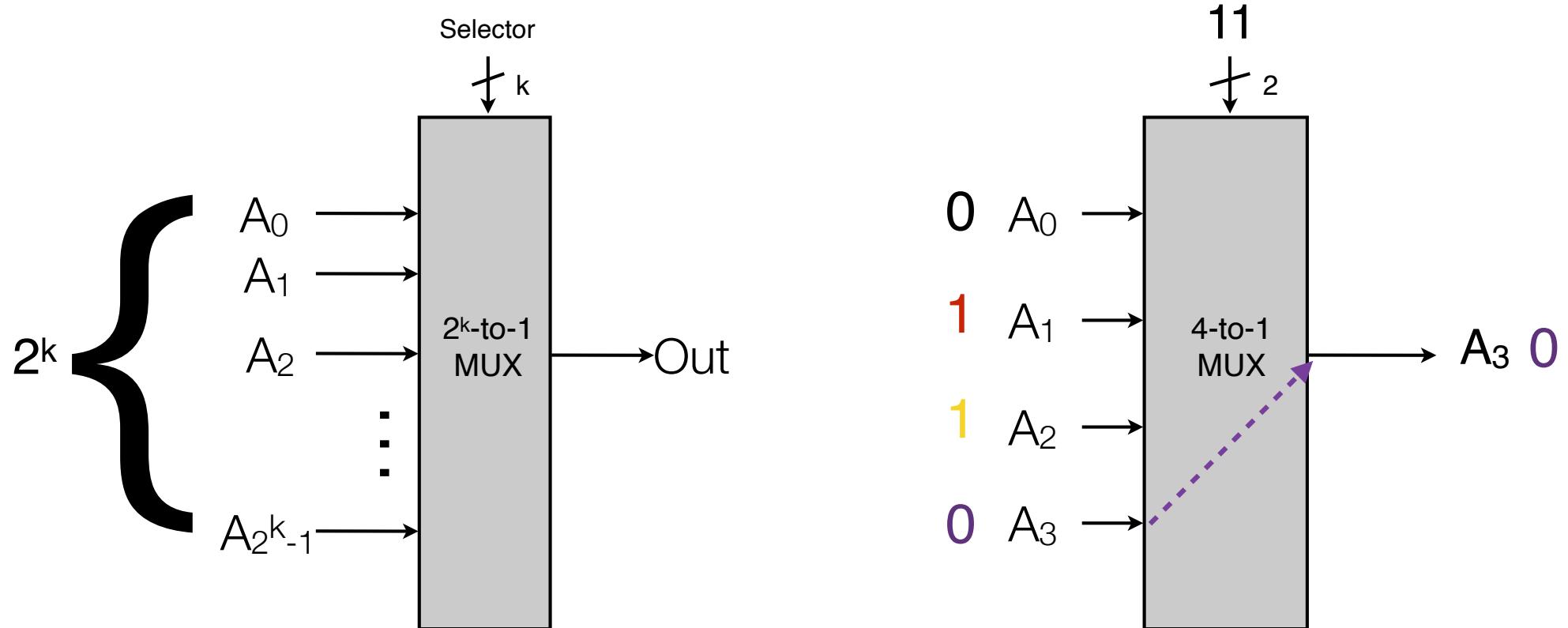- 2^k Data values enter as input
- k-bit selector chooses which one comes out
- Like the A_i are digital music signals (over time) and i chooses the station



Shifter Circuit (High-level)

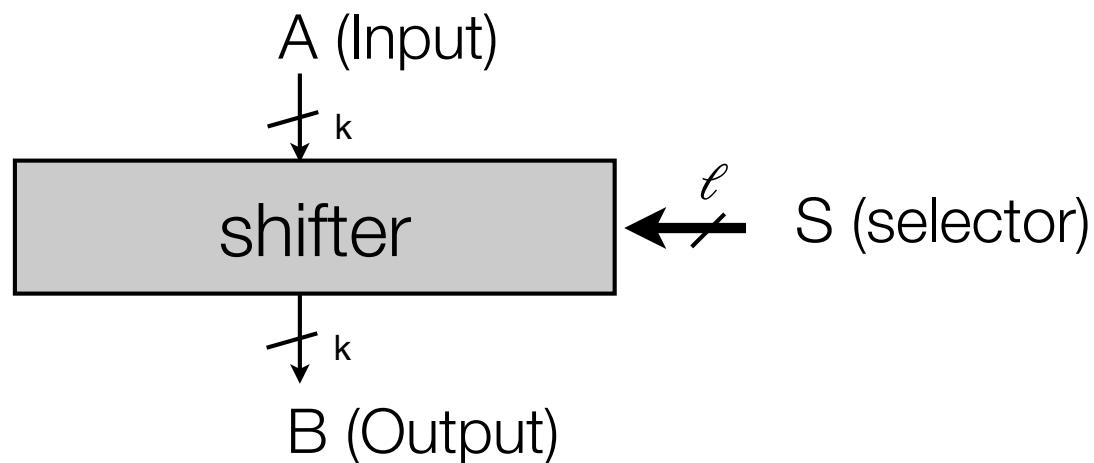- k -bit data value entered as input
- ℓ -bit selector gives instructions how to shift




Barrel Shifter: 8 bits w/ rollout Example

e.g., shift-left-3 11001010

1 1 0 0 1 0 1 0


Barrel Shifter: 8 bits w/ rollout Example

e.g., shift-left-3 11001010

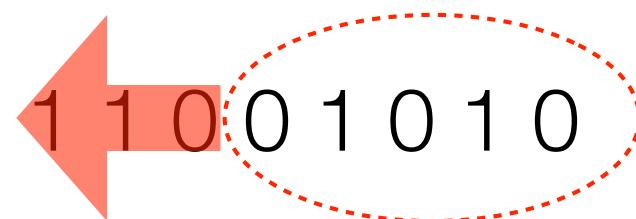

Barrel Shifter: 8 bits w/ rollout Example

e.g., shift-left-3 11001010

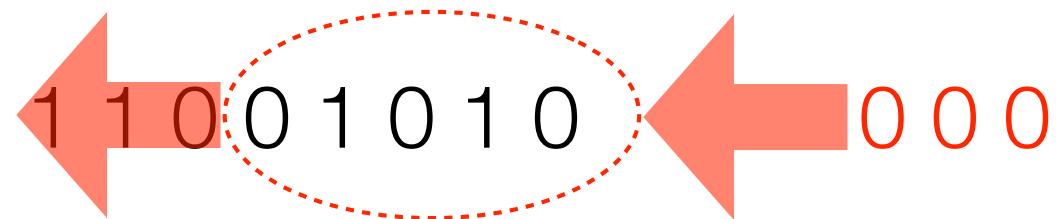

result: 01010000


Barrel Shifter: 8 bits w/ wraparound Example

e.g., shift-left-3 11001010

1 1 0 0 1 0 1 0

Barrel Shifter: 8 bits w/ wraparound Example


e.g., shift-left-3 11001010

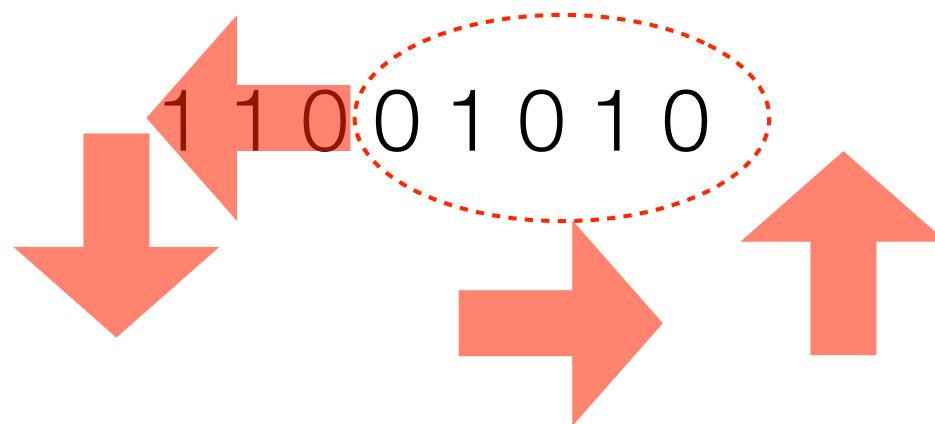


result: 01010110

(Barrel) Shifter Circuit (High-level)

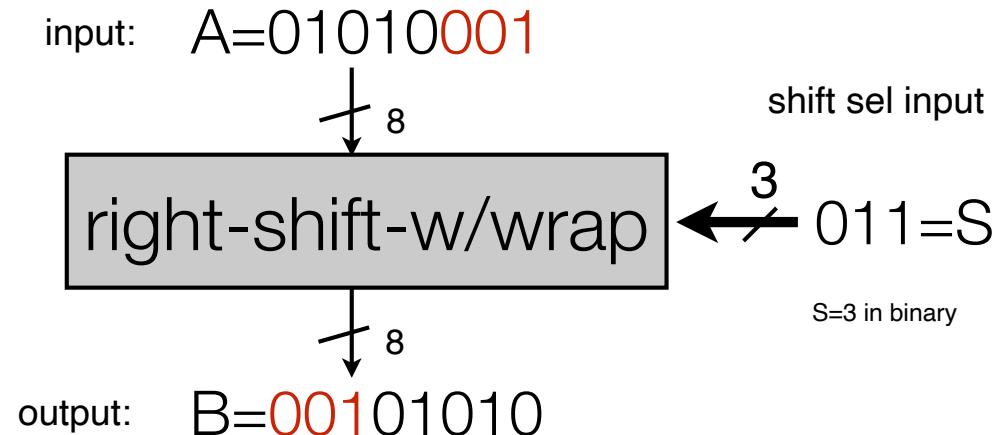- k-bit data value entered as input
- $\ell = \log_2 k$ -bit selector chooses how far bits should be shifted
- Example 1: $k=8$, right shifter with “wraparound”, asked to shift by 3 bits




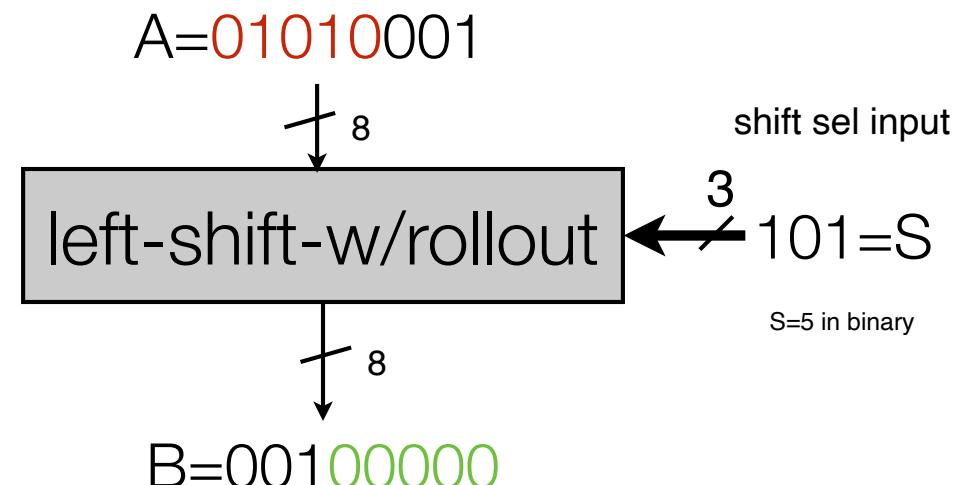- Example 2: $k=8$, left shifter with “rollout”, asked to shift by 5 bits (fill missing bits with 0's)




(Unsigned) Adder Circuit (High-level)

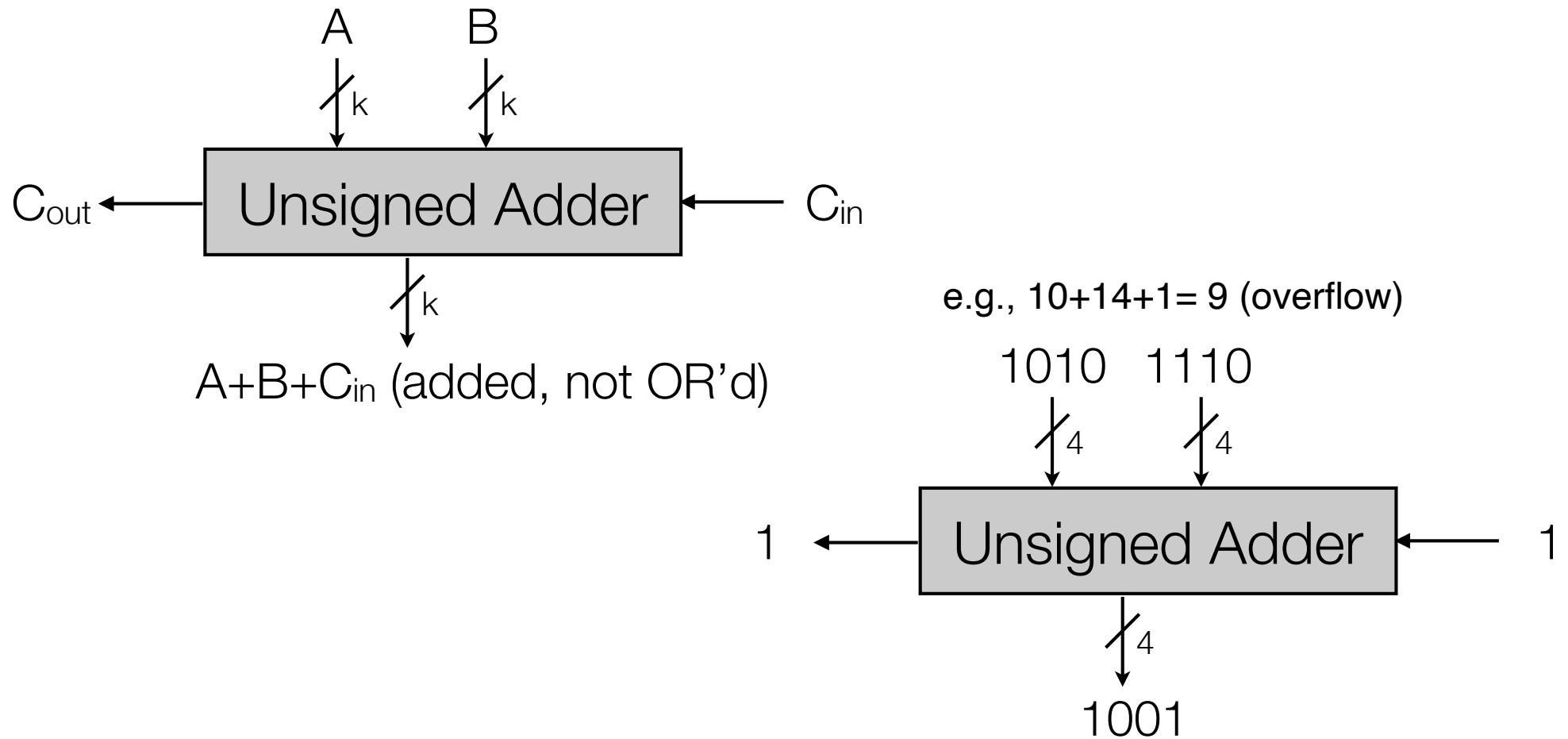- Two k-bit data values, A and B, and 1 bit C_{in} (carry-in) entered as input
- output is k-bit $A+B+C_{in}$ (unsigned binary addition), and 1-bit C_{out} (carry-out), i.e., the overflow



(Signed 2's-C) Adder/Subtractor Circuit (High-level)

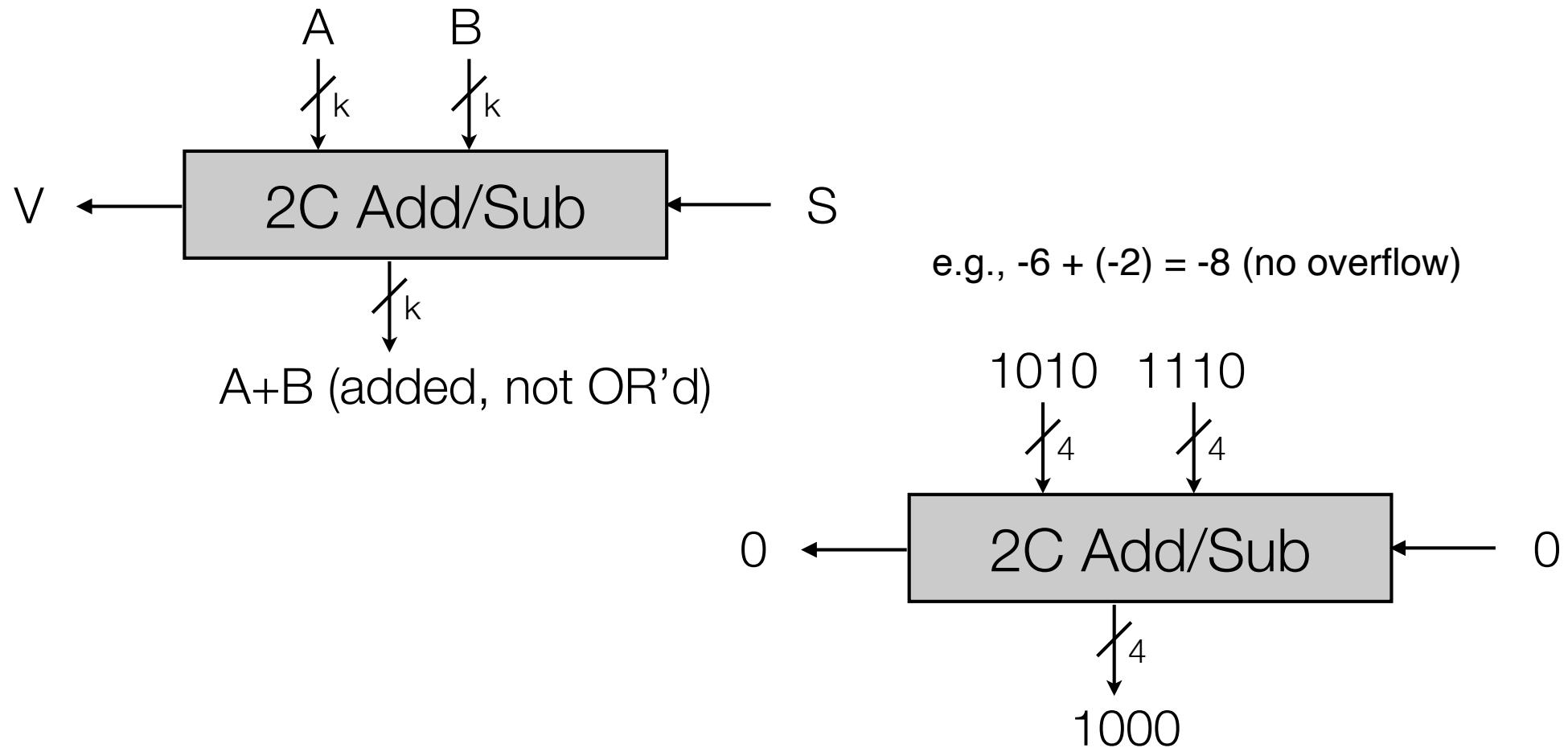- Two k-bit data values, A and B, and 1 bit S=0 for add, S=1 for subtract
- Output is k-bit A+B when S=0, A-B when S=1 (2's comp binary add/sub), and 1-bit overflow, V





“Standard” Circuit Details

(how to build from basic boolean ops)

Enabler

Enabler Circuit (High-level view):

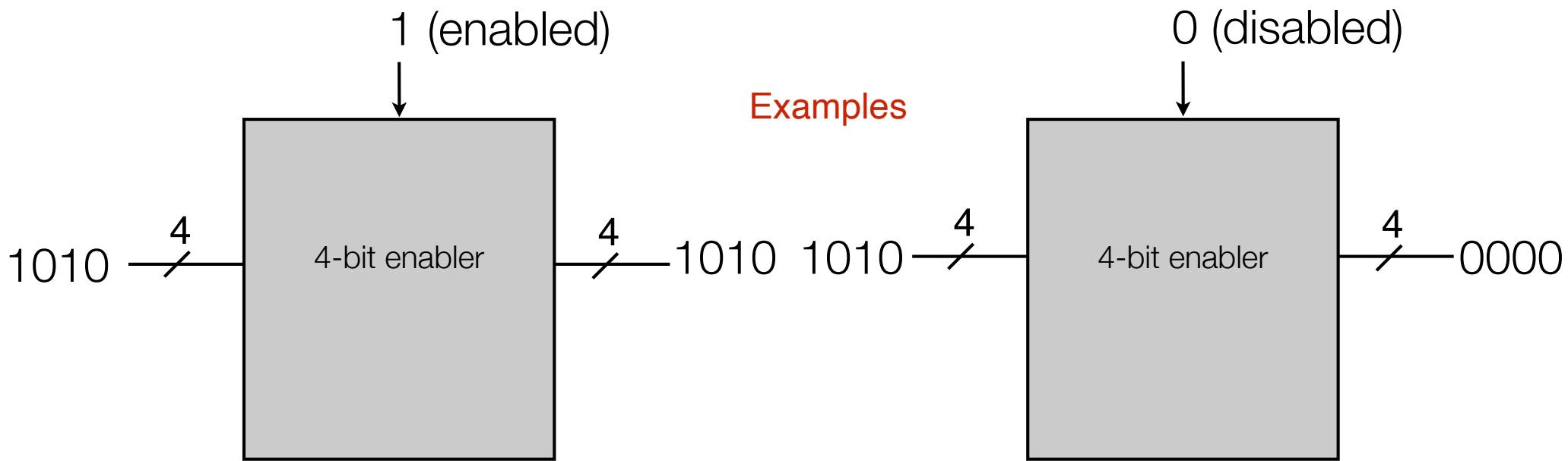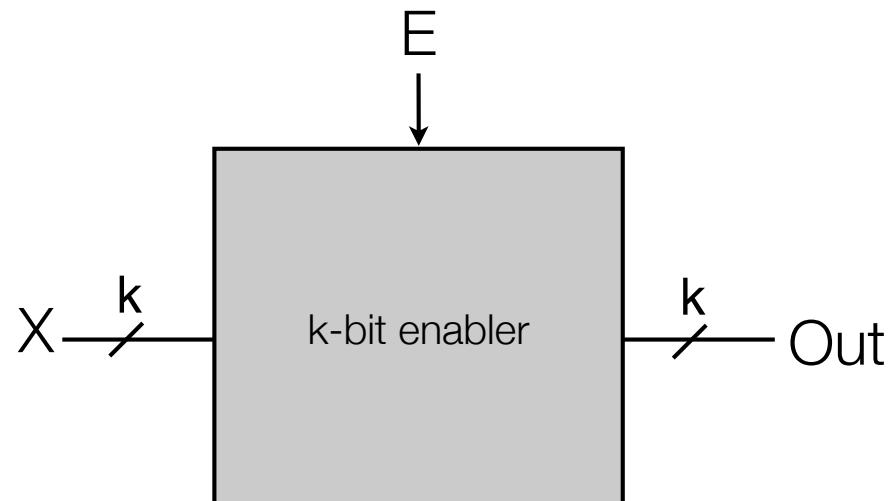
- Enabler circuit has 2 inputs
 - data (can be k bits in parallel)
 - enable/disable (i.e., on/off) input
- Output:
 - If $E=1$, output = data input
 - If $E=0$, output = k 0's



Enabler circuits: 1-bit Data input “A” ($k=1$)


3-15

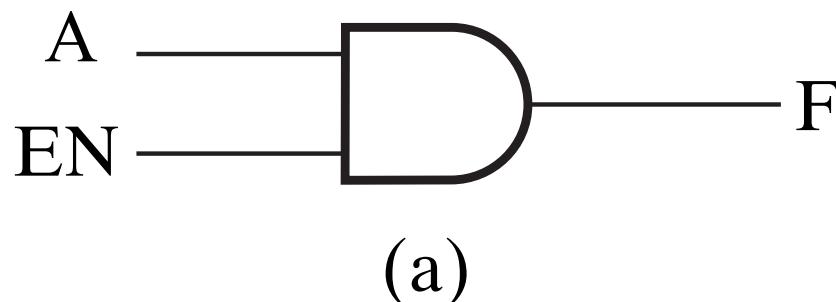Abbreviated truth table (input listed in the output)



EN	F
0	0
1	A


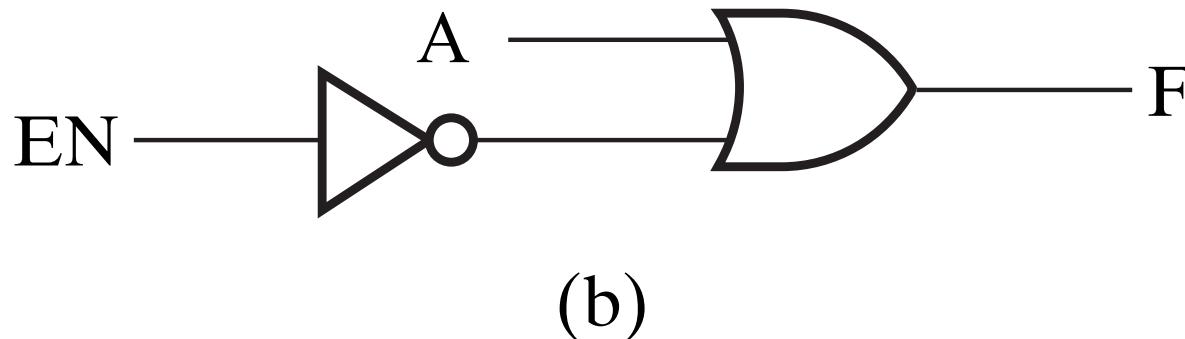
A “reverse” enabler (outputs 1 when disabled):



EN	F
0	1
1	A

For both enabler circuits above, output is “enabled” ($F=X$) only when input ‘ENABLE’ signal is asserted ($EN=1$). Note the different output when DISABLED


k -bit enabler (e.g., $k=8$)

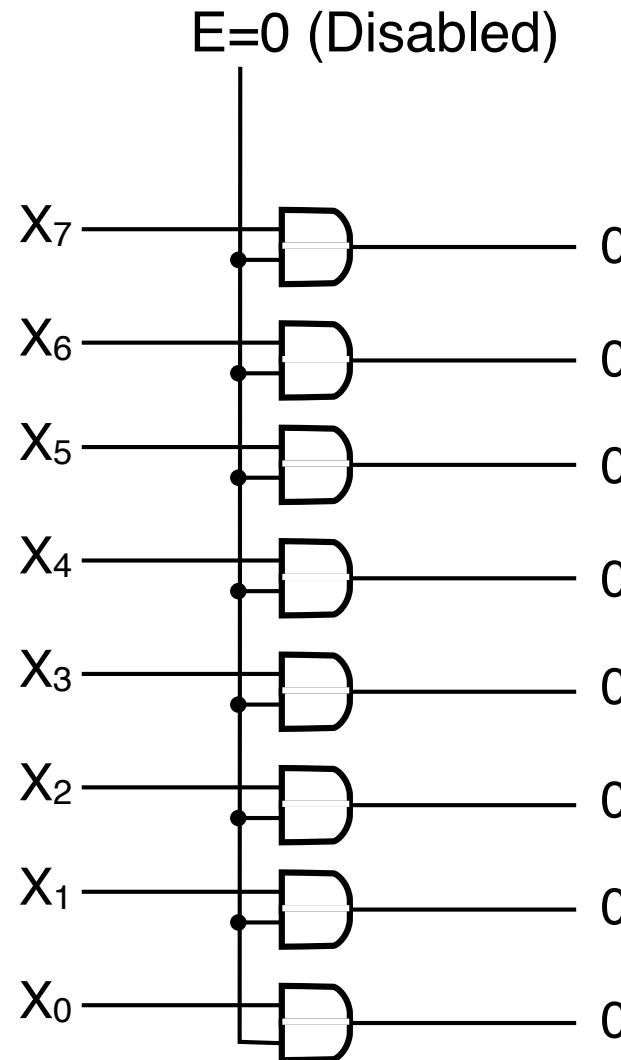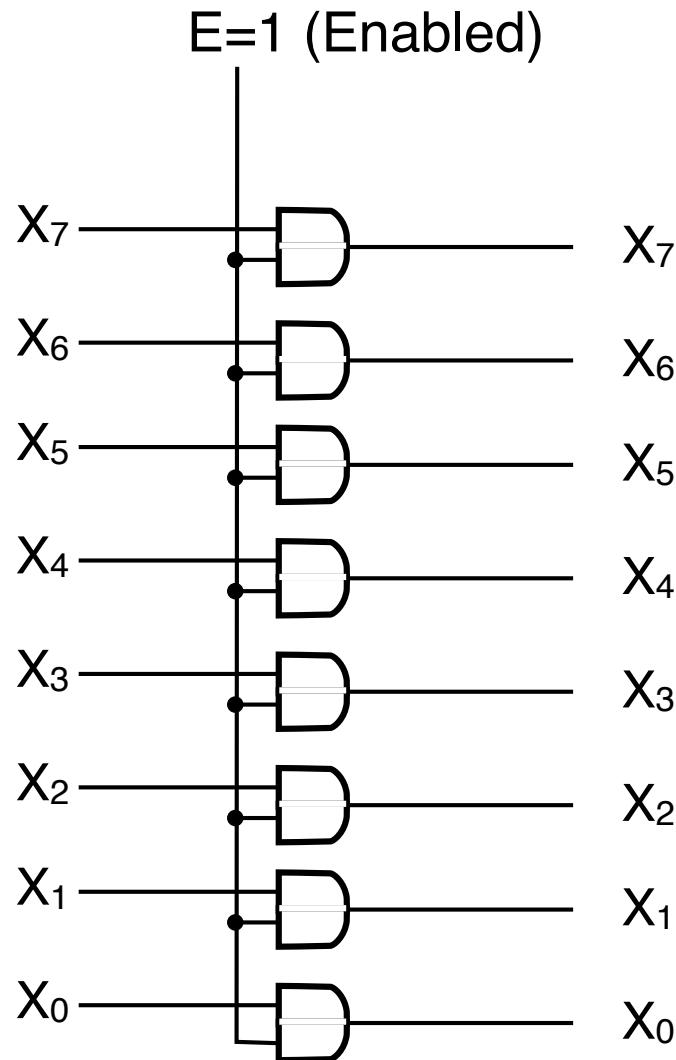

Decoder

Standard Decoder Circuit (high-level view):

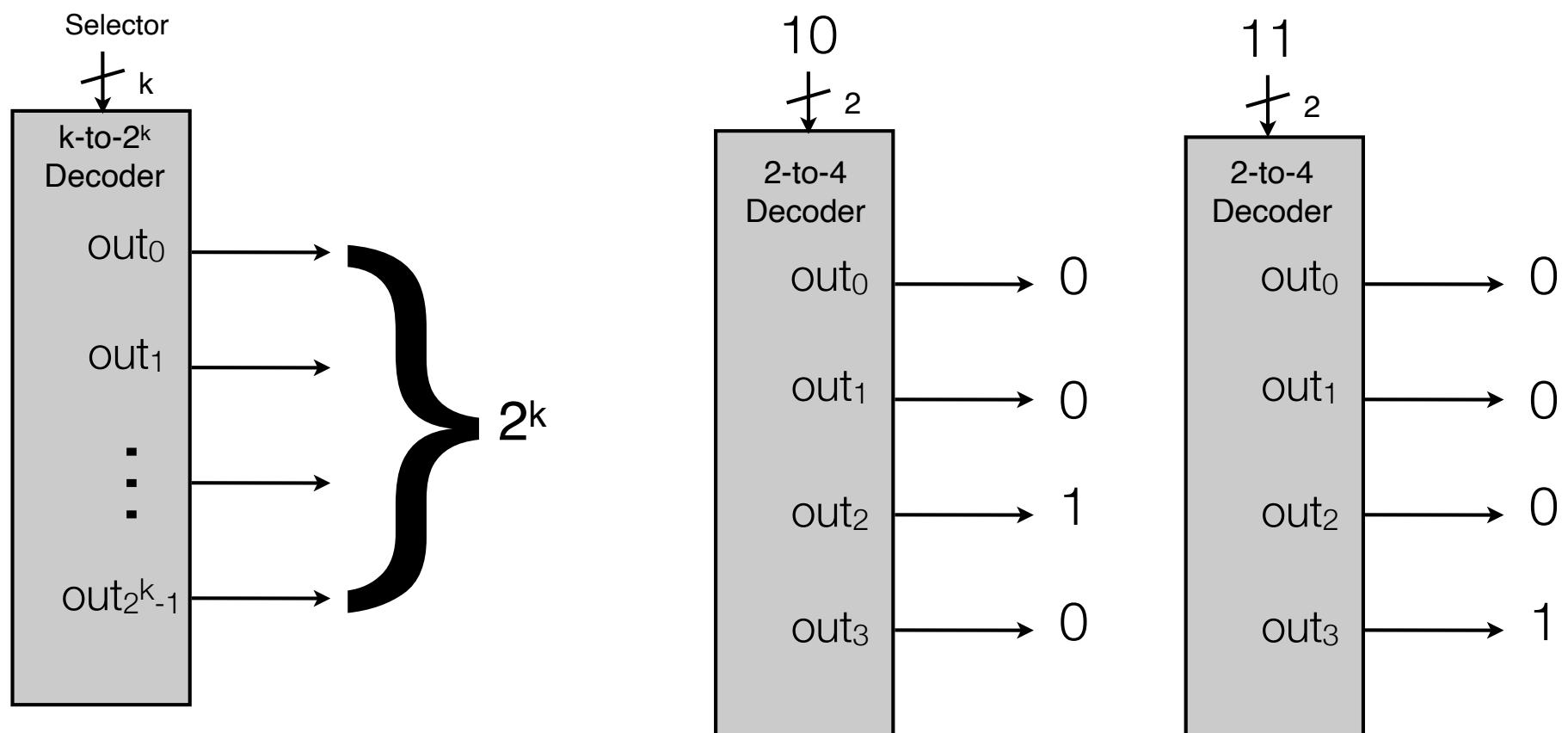- No “DATA” inputs, just a k -bit “selector” input
- 2^k 1-bit outputs
- Selector input chooses which output = 1, all other outputs = 0




Decoder (1:2) Internal Design

3-17

A	D ₀	D ₁
0	1	0
1	0	1

(a)

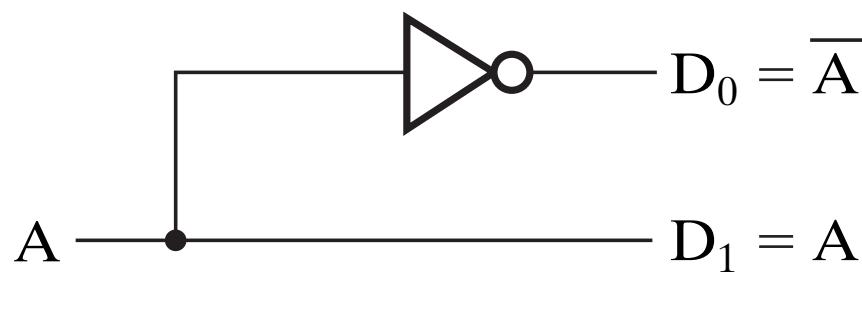

(b)


Decoder (2:4)

3-18

“Standard” Decoder: i^{th} output = 1, all others = 0,
where i is the binary representation of the input

A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

(a)

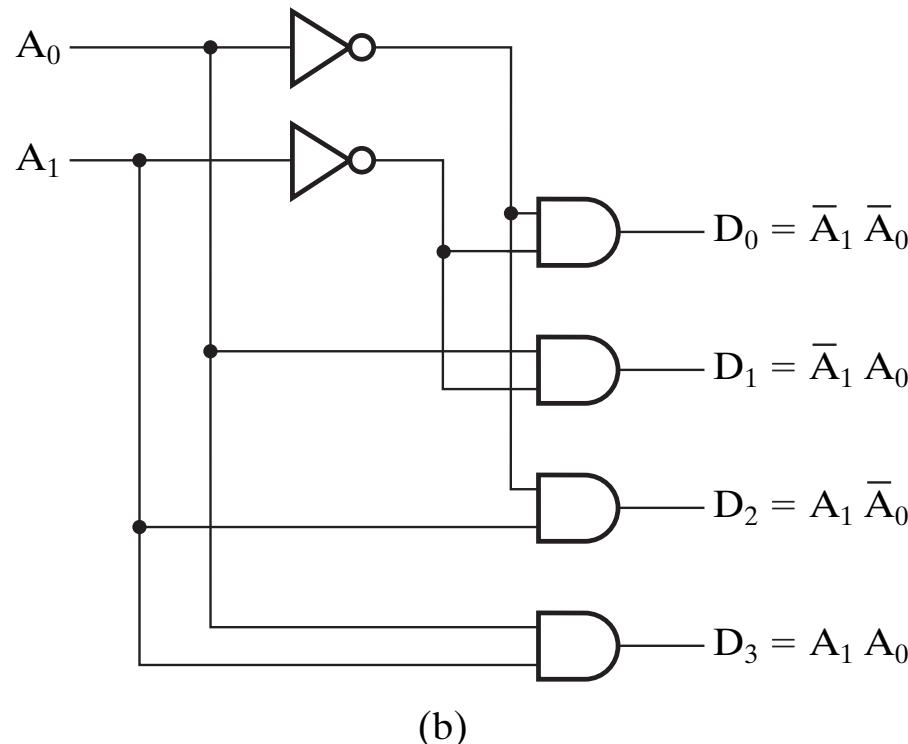


(b)

i^{th} output is just the i^{th} midterm!

Building a Decoder from scratch (building Minterms)

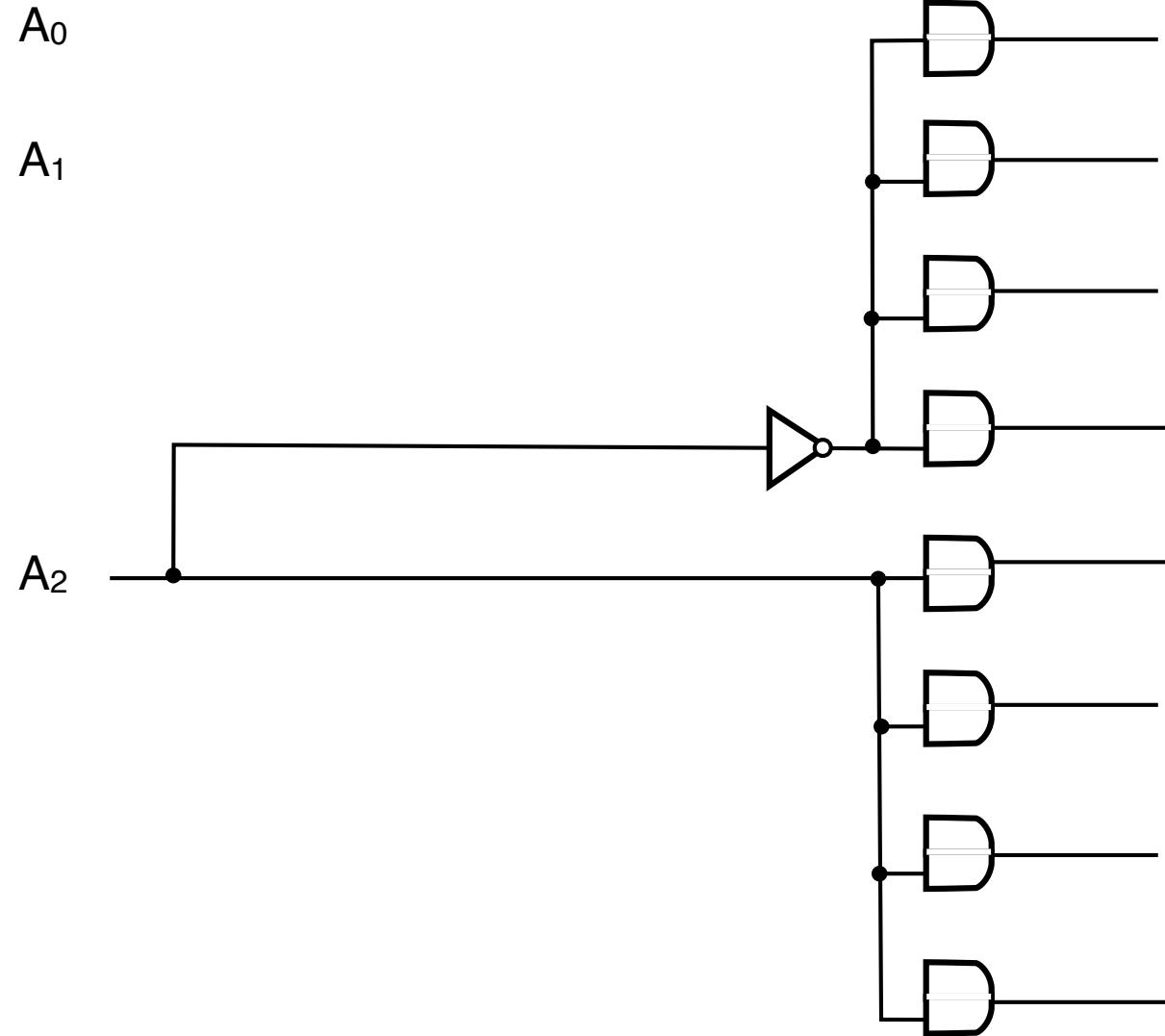
- A_2 is 0 for top 4 gates, 1 for bottom 4



A_2	A_1	A_0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Building a Decoder from scratch (building Minterms)

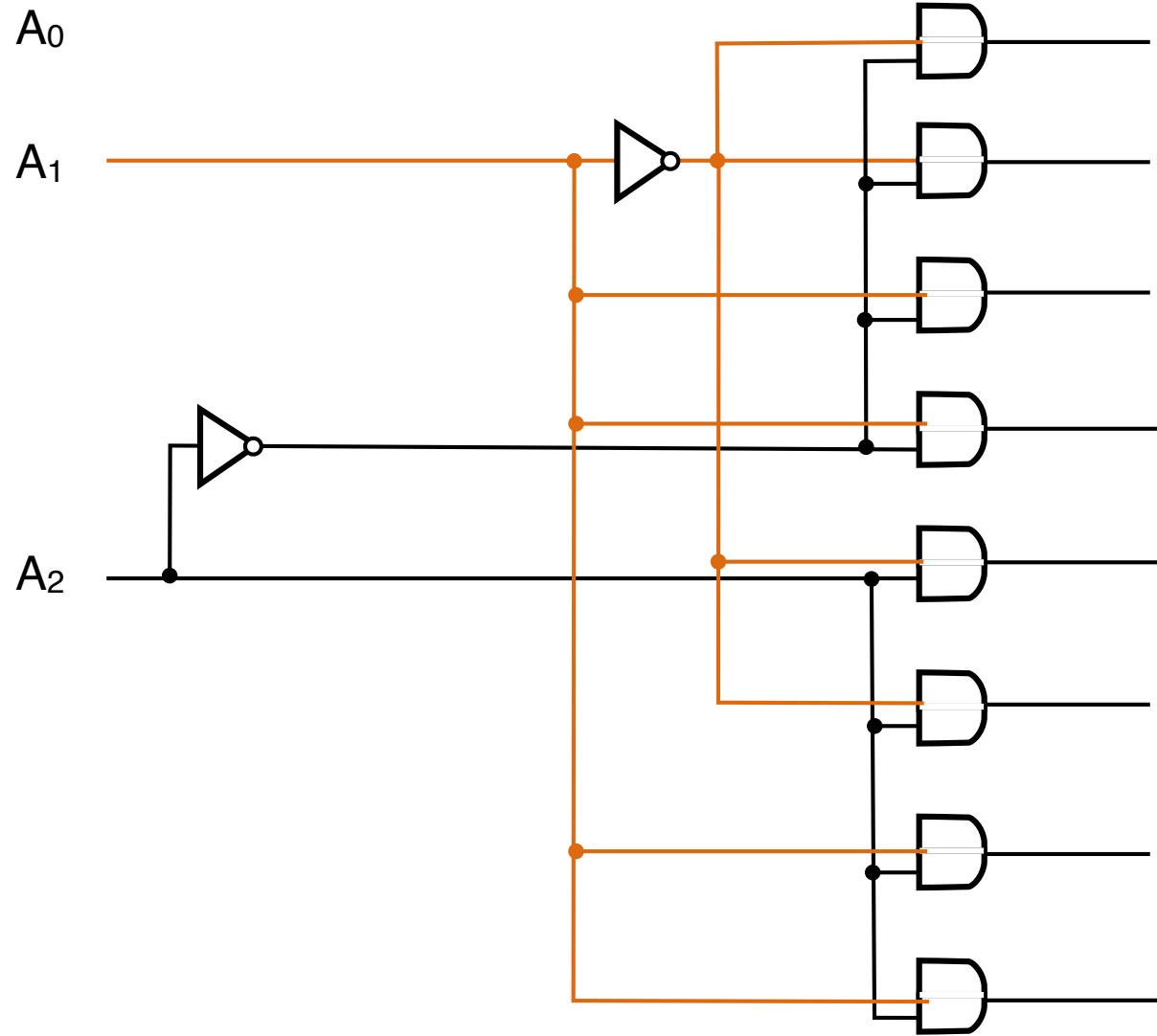
- A_1 is 0 for gates 0,1,4,5, is 1 for gates 2,3,6,7



A_2	A_1	A_0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


Building a Decoder from scratch (building Minterms)

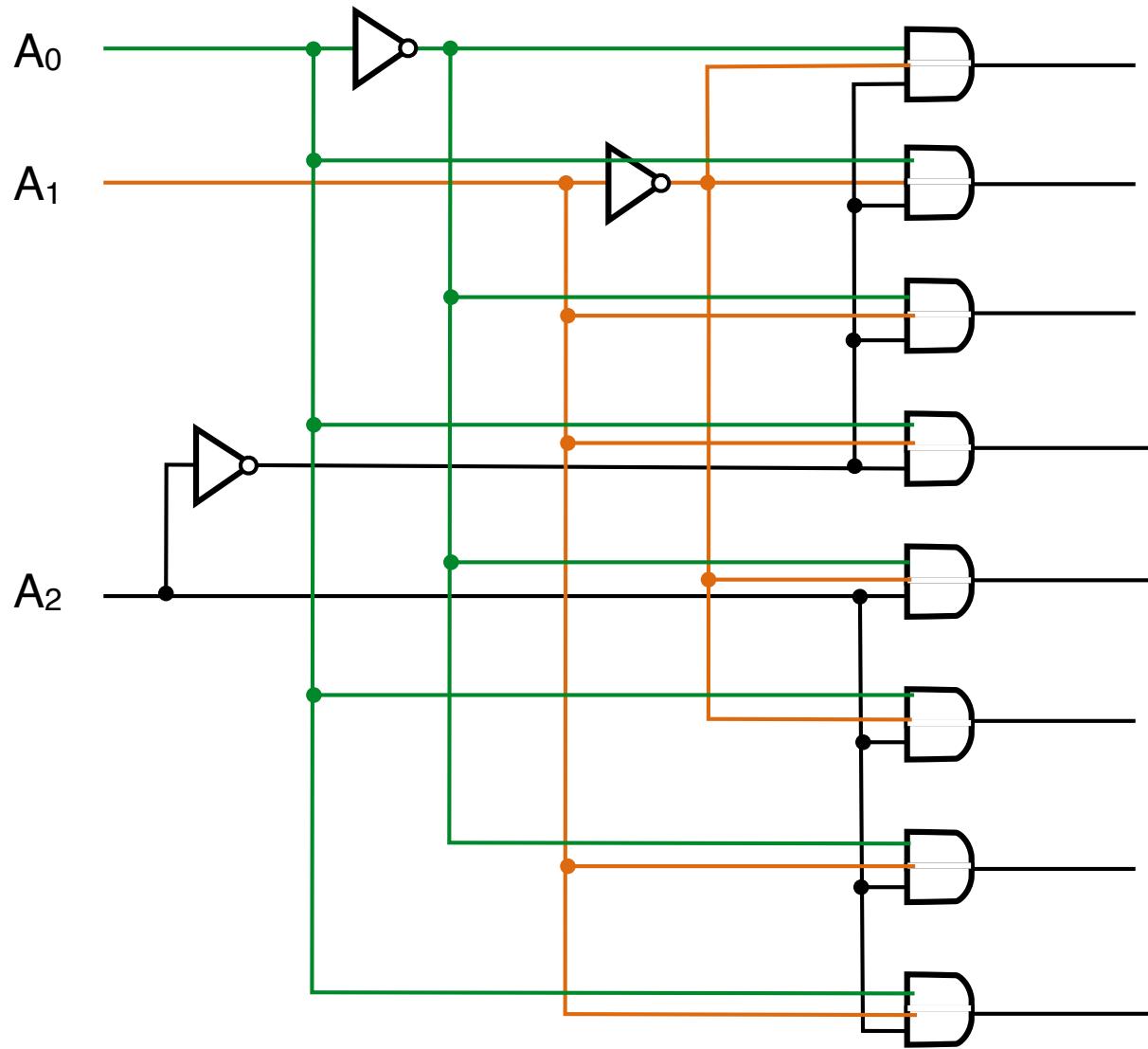- A_0 is 0 even gates (0,2,4,6), 1 for odd




A₂	A₁	A₀
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Example: $A = A_2A_1A_0 = 110$

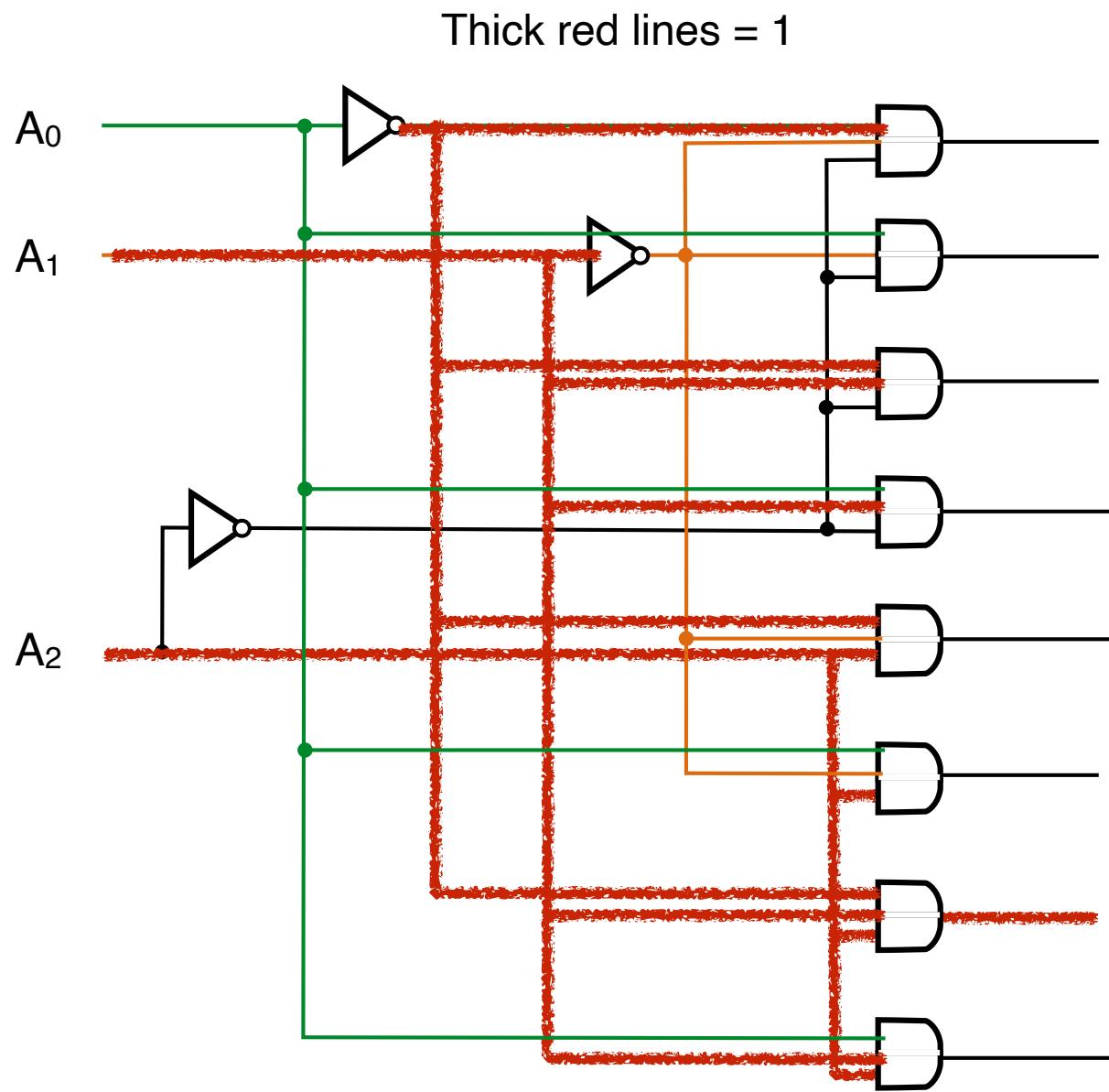

A_2	A_1	A_0
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1


Decoder with Enable from Decoder

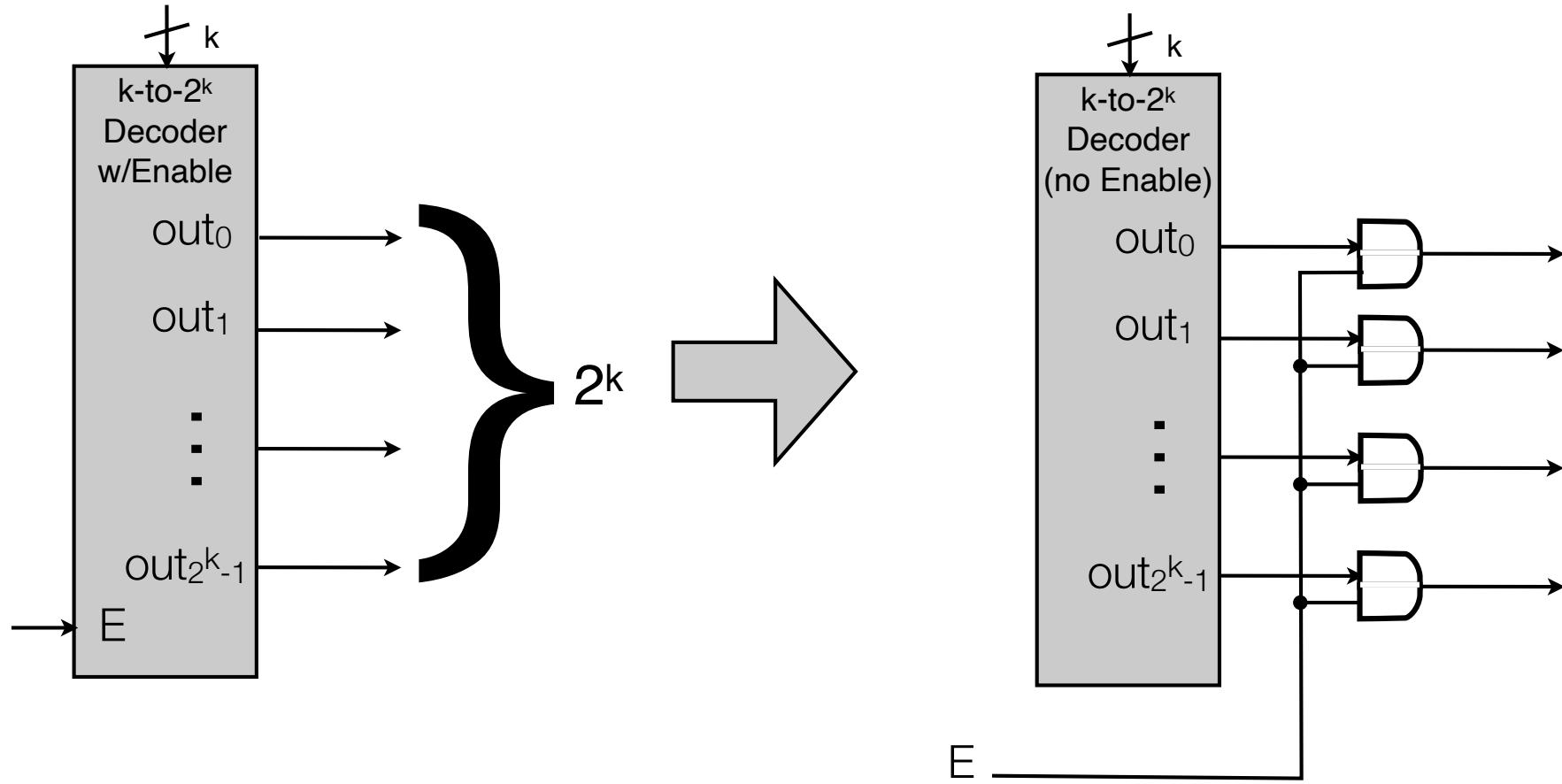

Merging a signal with
known 0 signals


Merge-with-known-0's

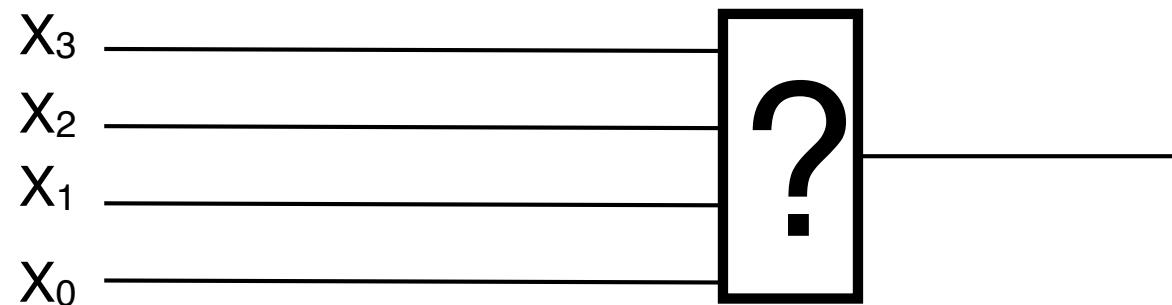- Suppose have m input signals
- We know all of them = 0 except maybe one X_j . (but we don't know which X_j is possibly non-0)
- Circuit to retrieve the value of the one unknown



Merge-with-known-0's

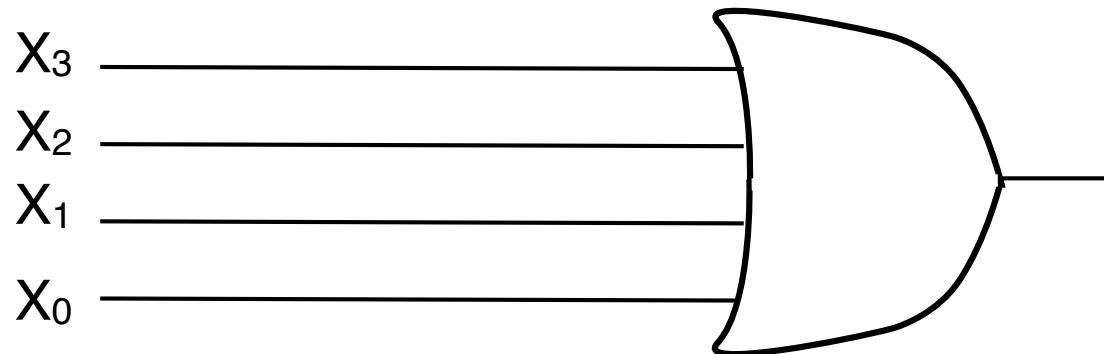- Suppose have m input signals
- All of them = 0 except maybe one X_j .
- Circuit to retrieve the value of the one unknown




- If all $X_i=0$ for $i \neq j$, then the OR over all X_i (including X_j) = X_j

Multiplexer (MUX)

MUX Circuit (High-level)

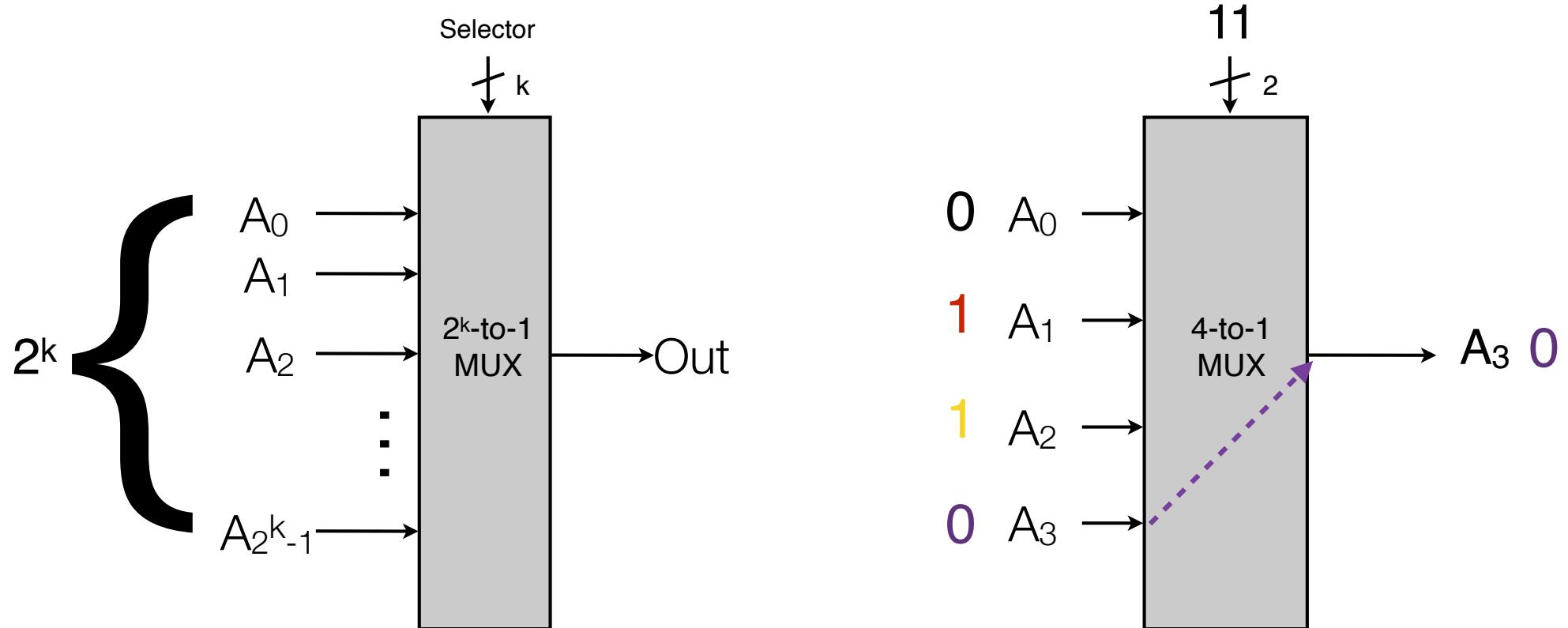- 2^k Data values enter as input
- k-bit selector chooses which one comes out
- Like the A_i are digital music signals (over time) and i chooses the station



Hierarchical Design


Recall

- AND, OR, NOT gates are really built from NANDs (or NORs)
- When we show a circuit in terms of AND,OR,NOT, the real underlying design is hierarchically built from NANDS

Similarly, big circuits built from “smaller parts”


3-4

“Big”Circuit

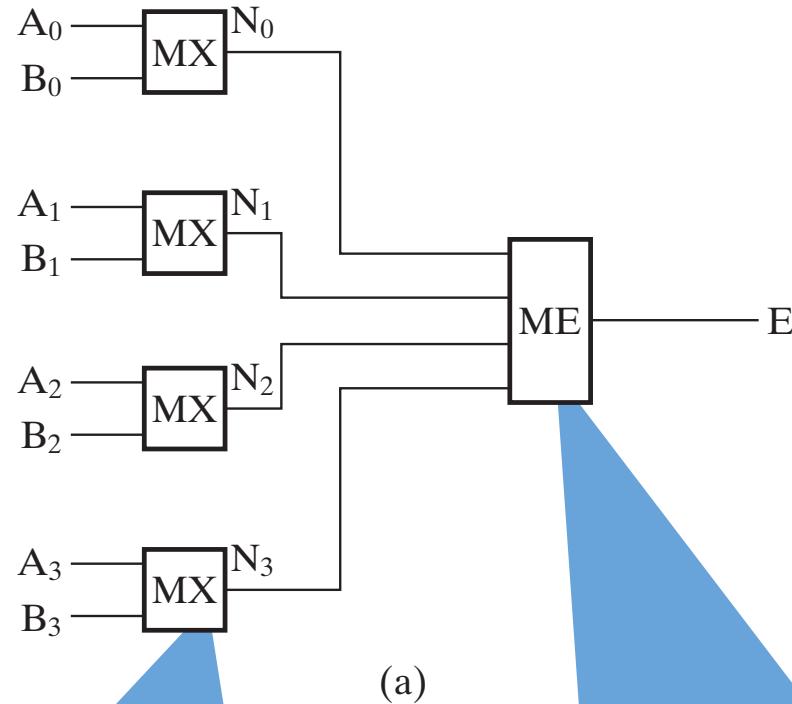


(a)

Smaller Circuits

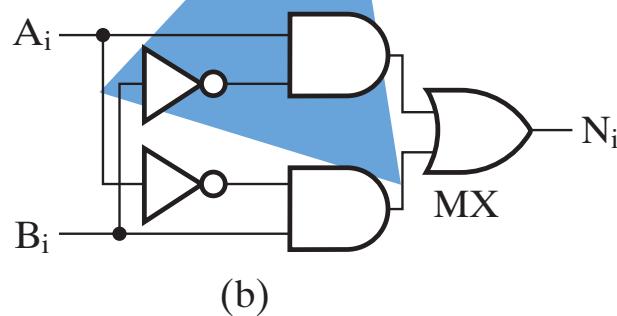

(b)

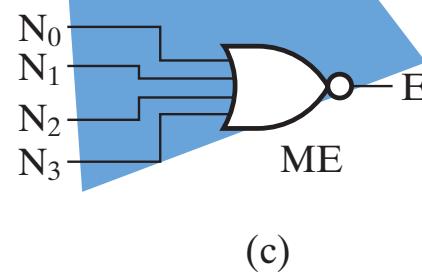


(c)

Big circuit can be built by combining smaller circuits, which are themselves built from even smaller circuits

MUX internals (hierarchical design example)


3-26

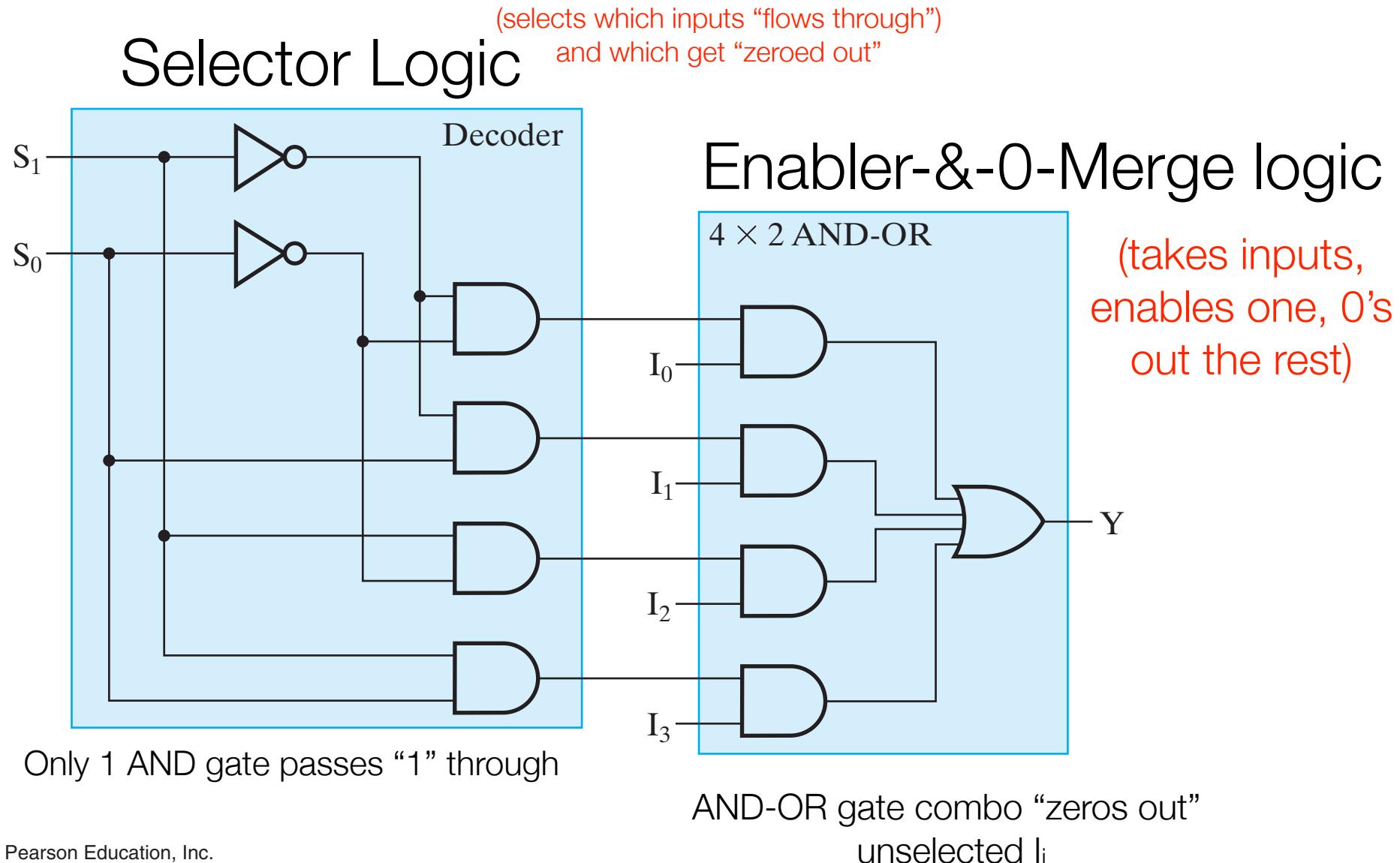

MUX Example: $S_1=1$, $S_0=0$


3-26

Selector Logic

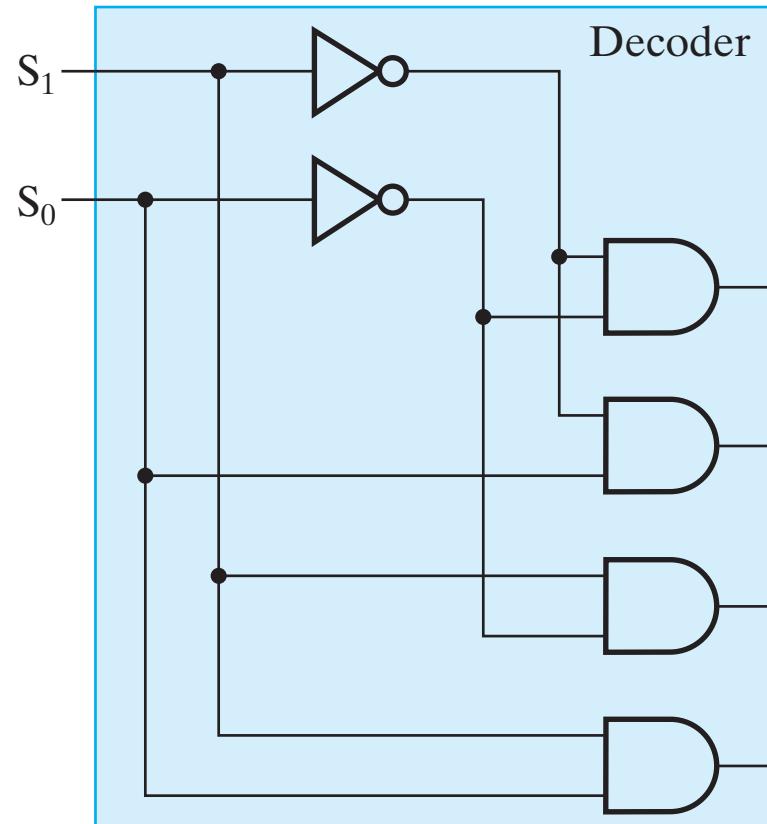

Only 1 AND gate passes “1” through

Enabler-&-0-Merge logic

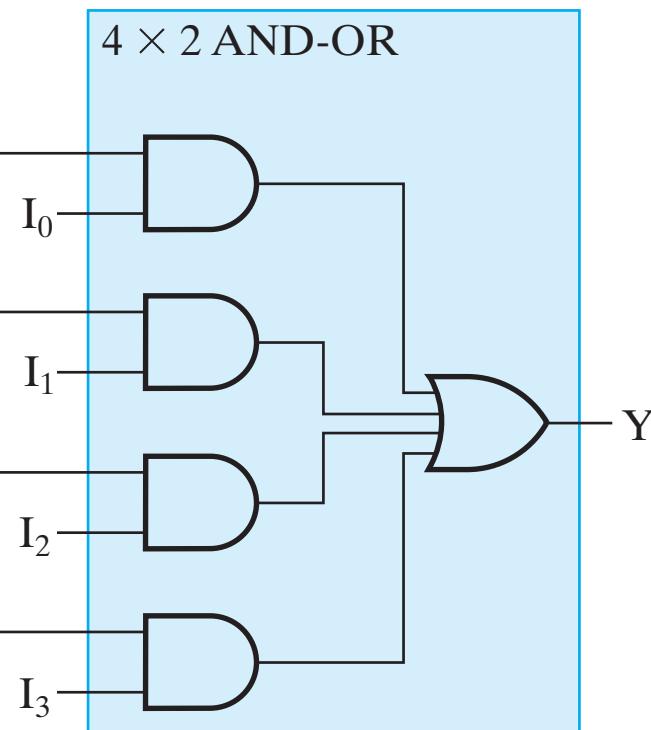


AND-OR gate combo “zeros out”
unselected I_i

MUX Example: $S_1=1$, $S_0=0$ (i.e., $S = 2$)


3-26

Selector Logic

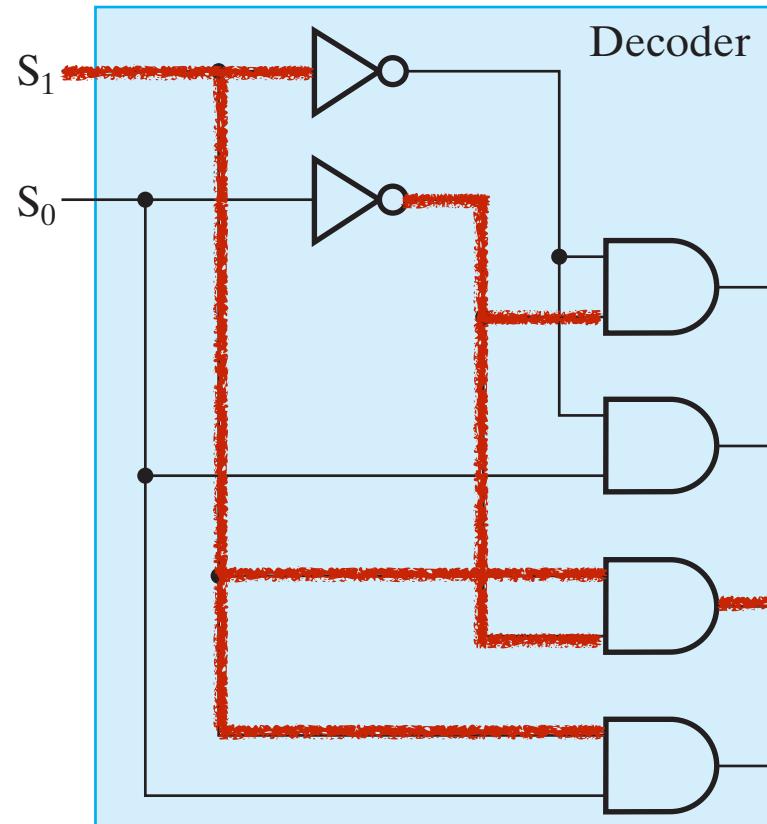


Only 1 AND gate passes “1” through

Enabler-&-0-Merge logic

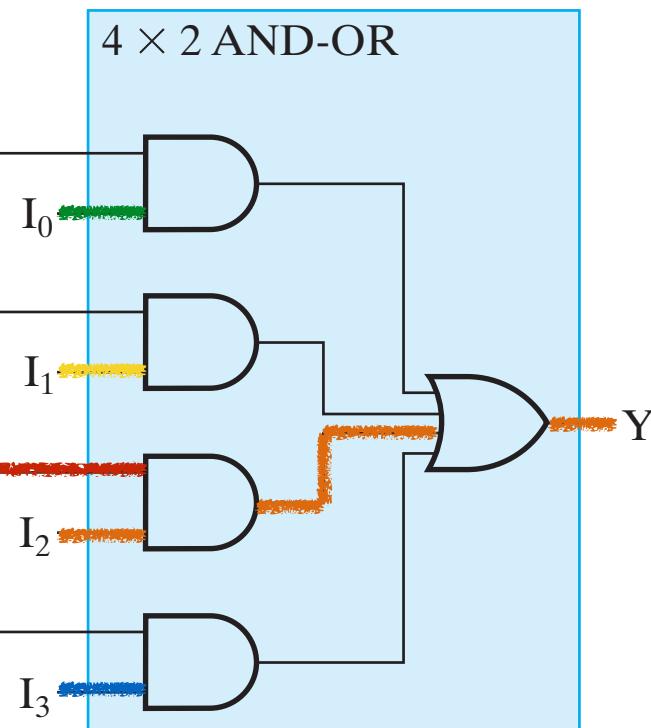


AND-OR gate combo “zeros out”
unselected I_i

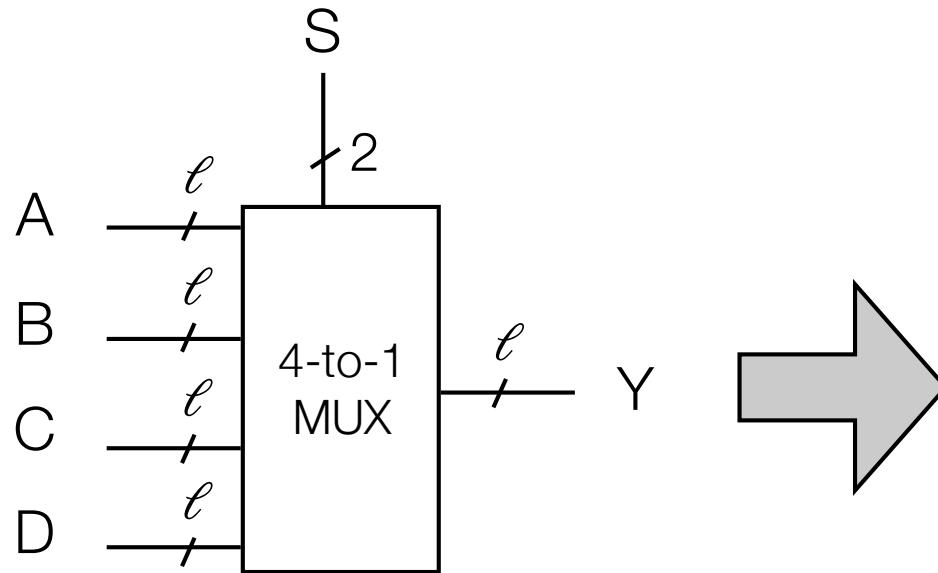Multi-bit Data Input MUX shorthand notation



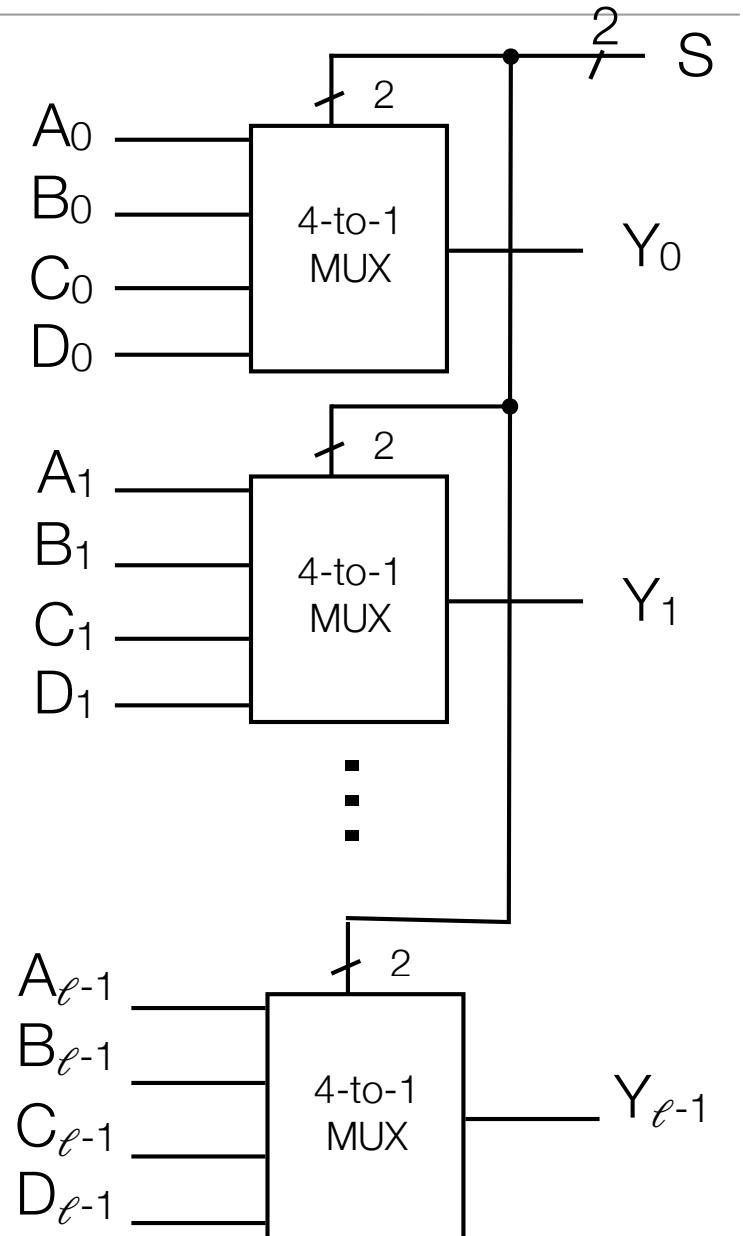- ℓ -bit 4-to-1 MUX: ℓ -bit quantities fed into a multiplexer, which selects one of those quantities
- Implemented by feeding each of k bits into k separate 1-bit 4-to-1 MUX, same selector bits fed into each MUX





Building Functions from Decoders and MUXes

Representing Functions with Decoders and MUXEs

- e.g., $F = \bar{A}\bar{C} + BC$


A	B	C	minterm	F
0	0	0	$\bar{A}\bar{B}\bar{C}$	0
0	0	1	$\bar{A}\bar{B}C$	0
0	1	0	$\bar{A}BC$	0
0	1	1	$\bar{A}BC$	1
1	0	0	$\bar{A}\bar{B}\bar{C}$	1
1	0	1	$\bar{A}\bar{B}C$	0
1	1	0	$\bar{A}BC$	1
1	1	1	ABC	1

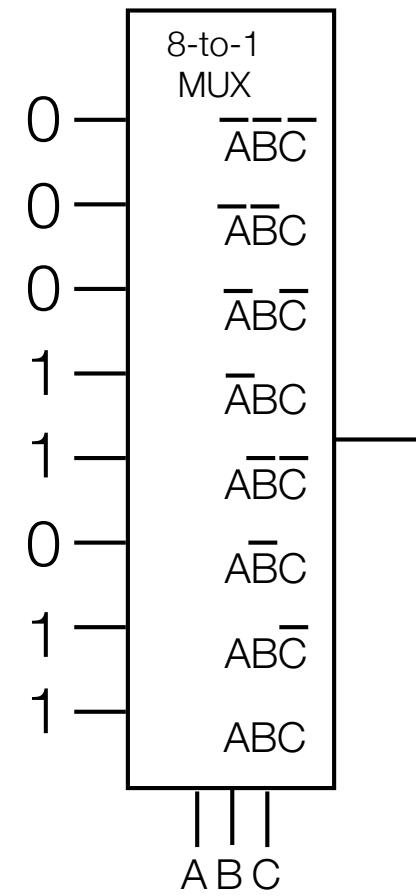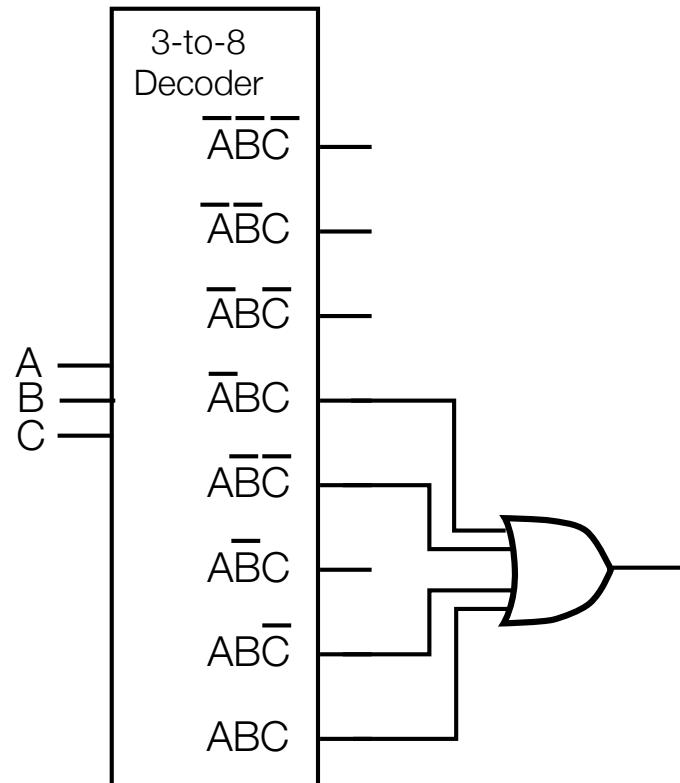

- Decoder: OR minterms for which F should evaluate to 1
- MUX: Feed in the value of F for each minterm


A Slick MUX trick

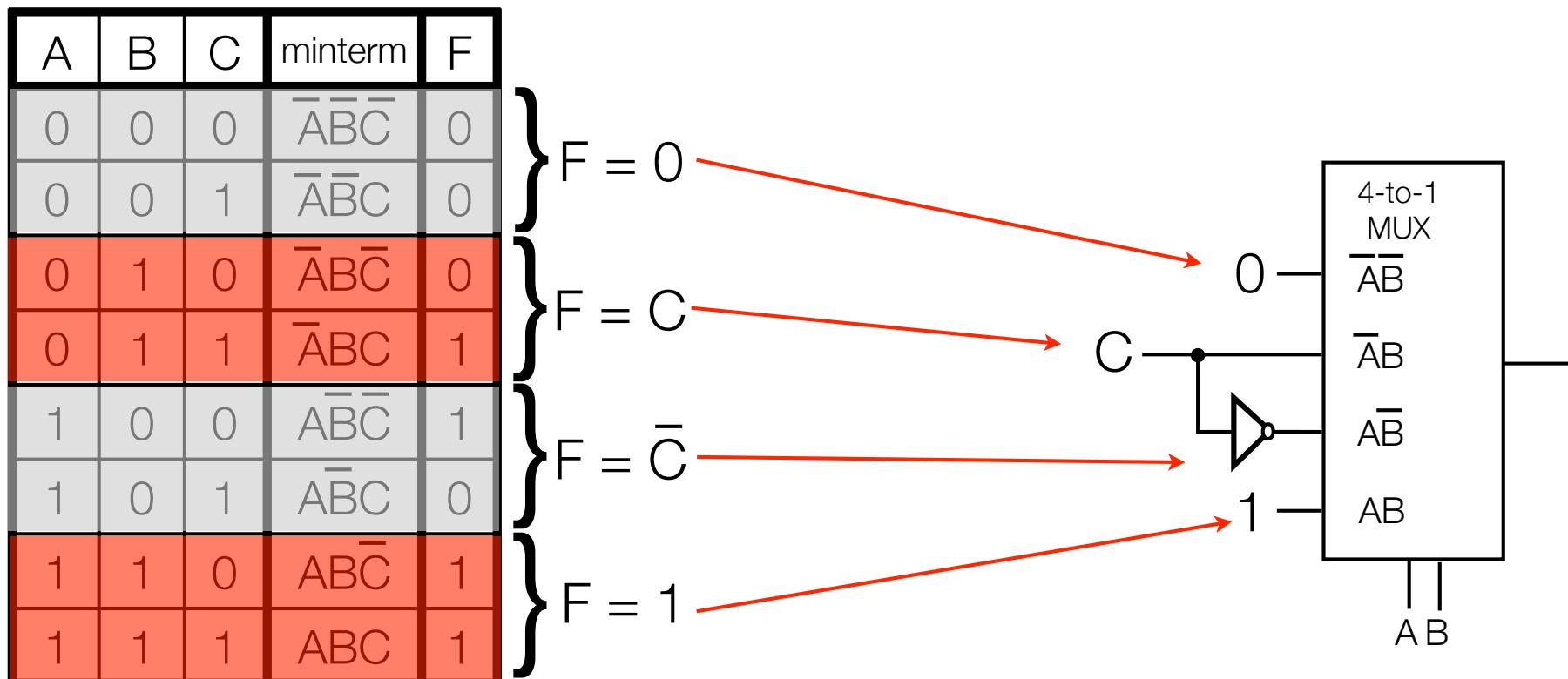- Can use a smaller MUX with a little trick e.g., $F = AC + \bar{B}\bar{C}$
- Note for rows paired below, A&B have same values, C iterates between 0&1
- For the pair of rows, F either equals 0, 1, C or \bar{C}




Slick MUX trick: Example

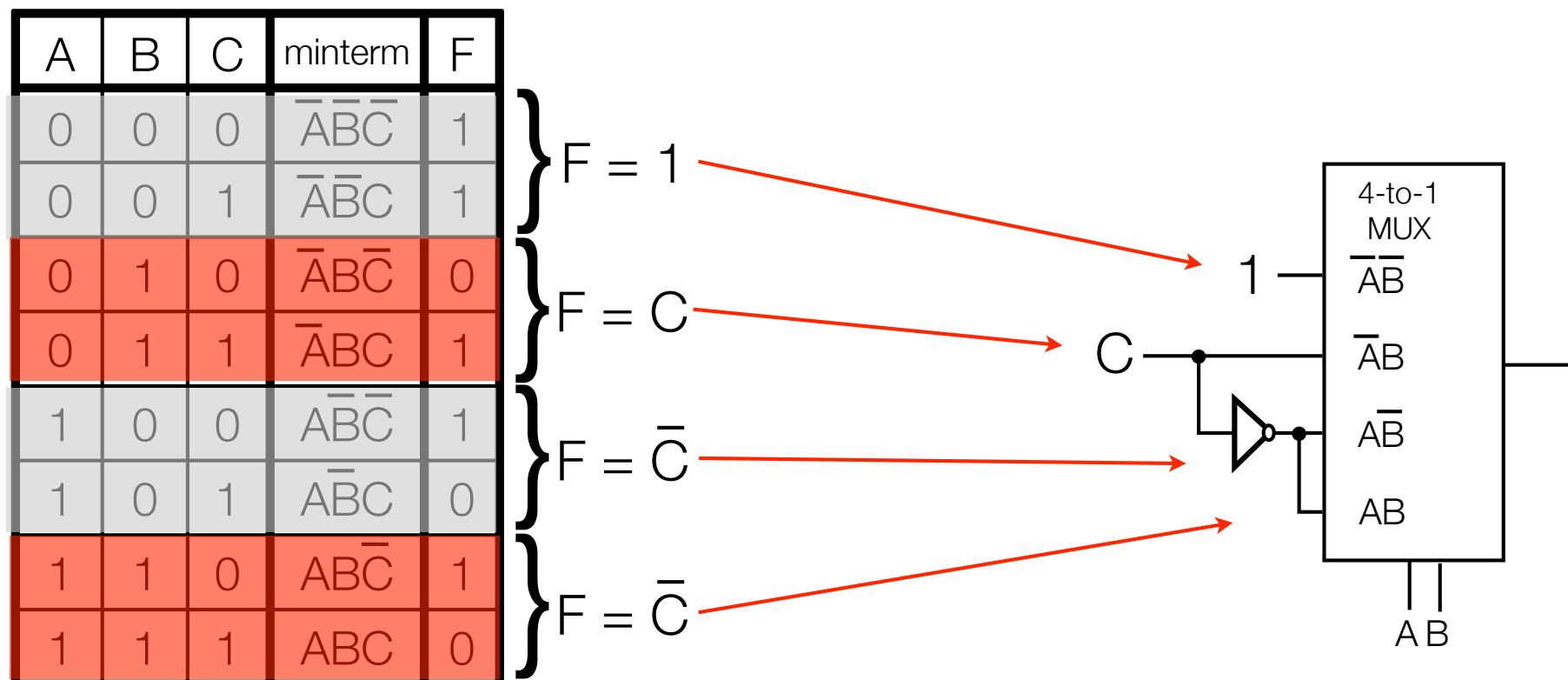- e.g., $F = \bar{A}C + \bar{B}\bar{C} + A\bar{C}$



Slick MUX trick: Example 2

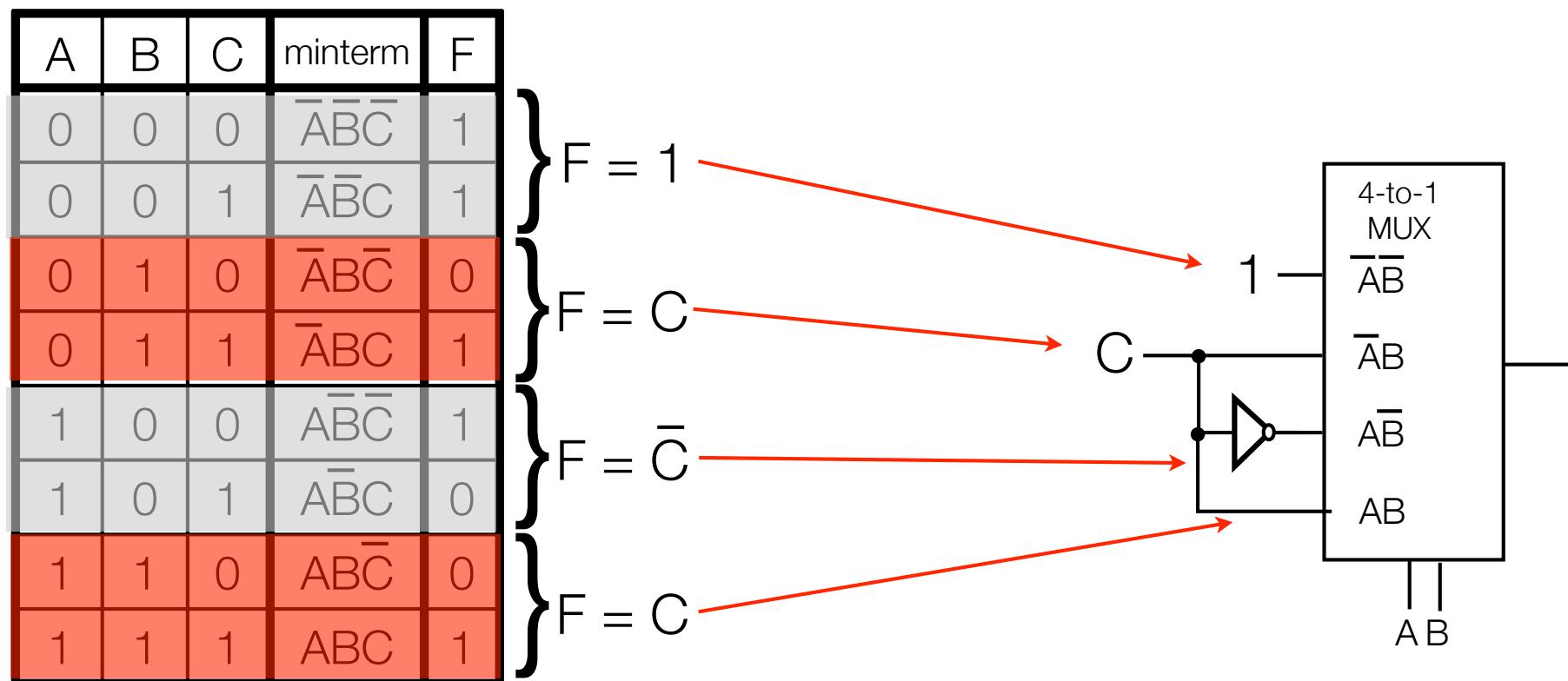
- e.g., $F = \bar{A}C + \bar{B}\bar{C} + BC$




Shifter

(Barrel) Shifter Circuit (High-level)

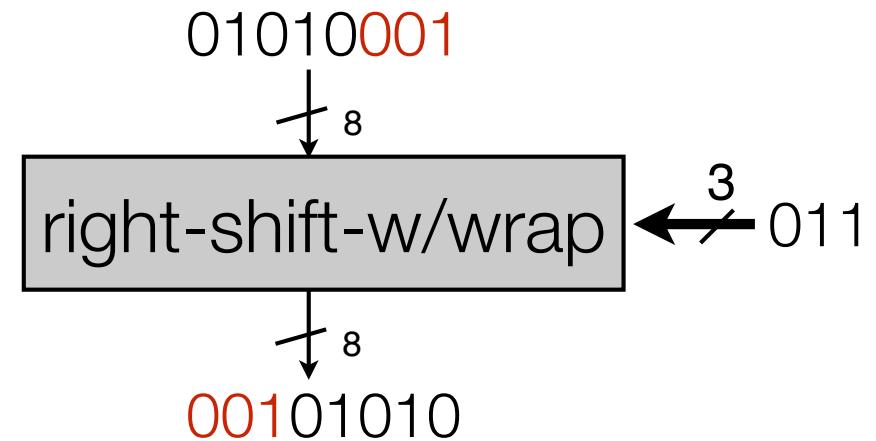
- k-bit data value entered as input
- $\ell = \log_2 k$ -bit selector chooses how far bits should be shifted
- Example 1: $k=8$, right shifter with “wraparound”, asked to shift by 3 bits



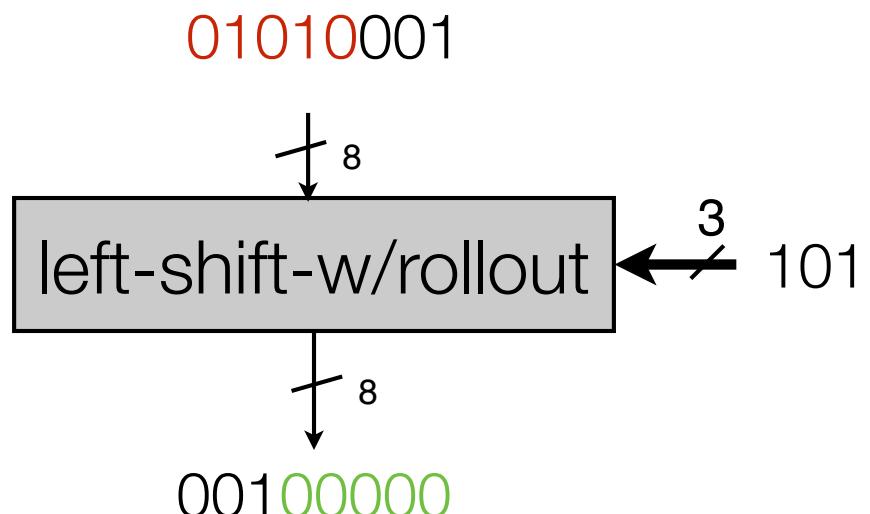- Example 2: $k=8$, left shifter with “rollout”, asked to shift by 5 bits (fill missing bits with 0's)




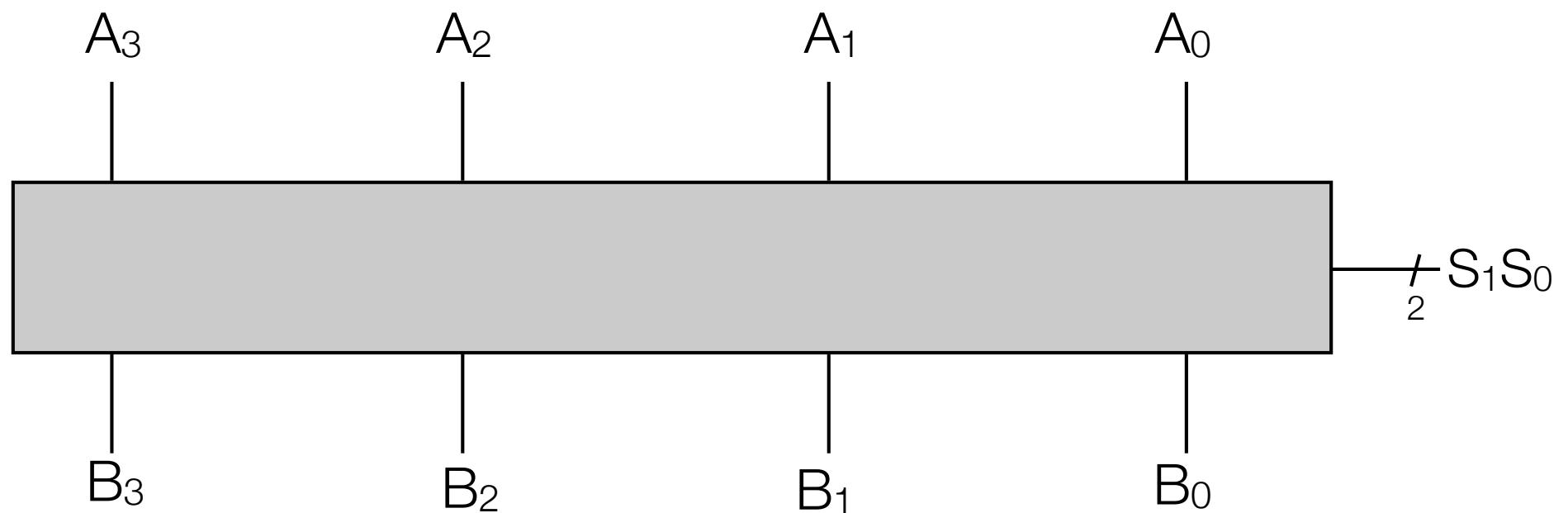Barrel Shift-Left Design with wraparound (using MUXs)



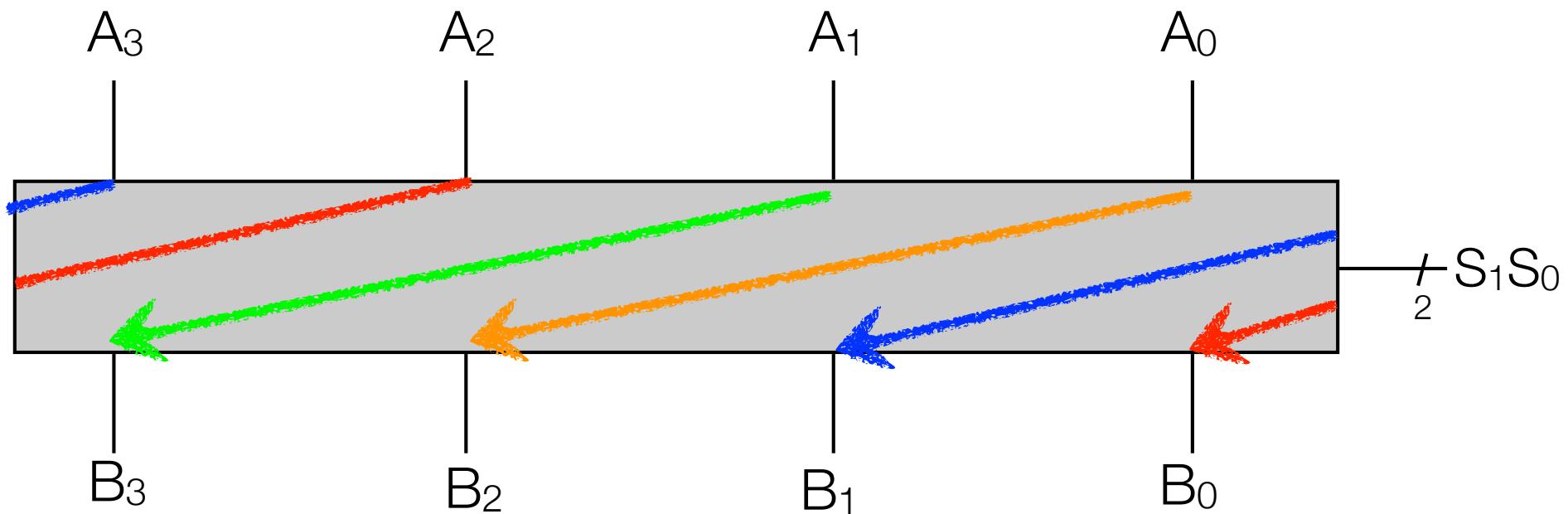
- EXAMPLE: $S = 2$ ($S_1S_0 = 10$)
- $B_{i+2} = A_i \text{ (mod 4)}$

Barrel Shift-Left Design with wraparound (using MUXs)



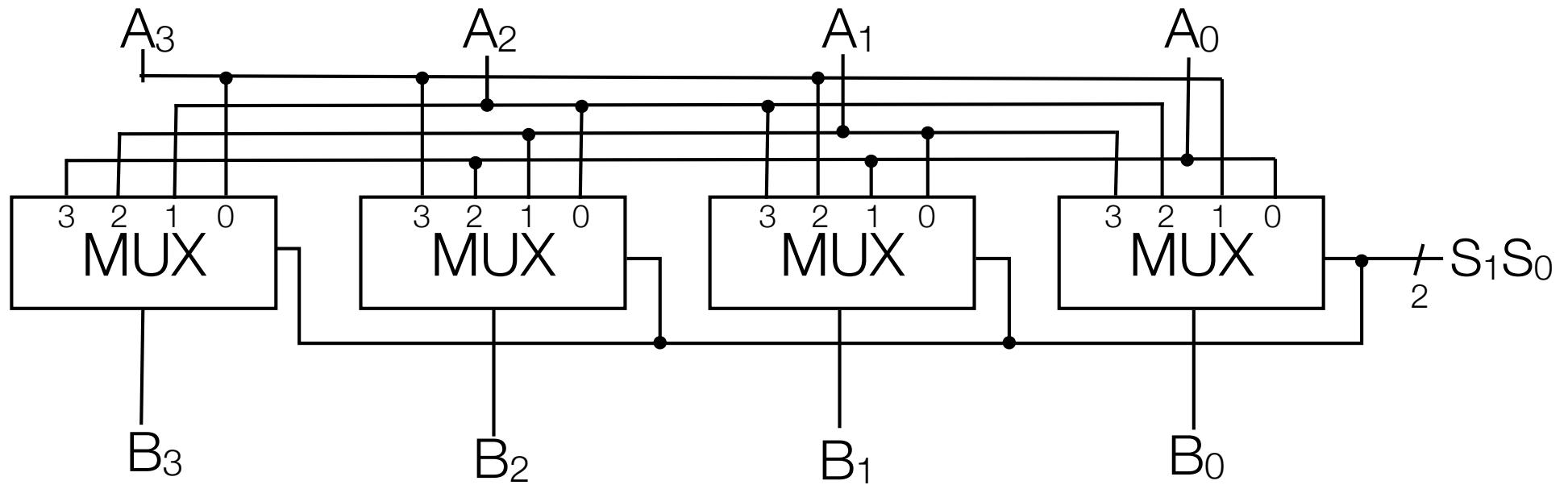
- EXAMPLE: $S = 2$ ($S_1S_0 = 10$)
- $B_{i+2} = A_i \pmod{4}$
- In general, if shifter = j , $B_{i+j} = A_i \pmod{\# \text{ data bits}}$

Barrel Shift-Left Design with wraparound (using MUXs)




- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$

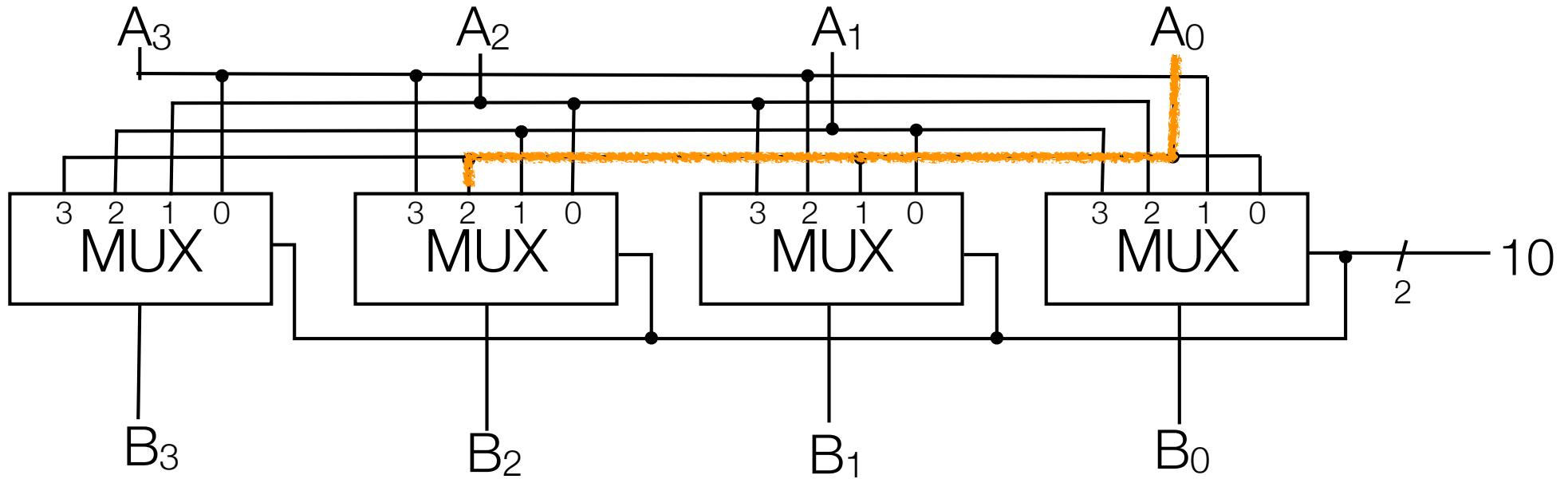Barrel Shift-Left Design with wraparound (using MUXs)



- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$
- Selector is 10 (i.e., 2 binary):
 - each MUX entry 2 is selected
 - A_0 flows into the '2' input of the MUX whose output is B_2

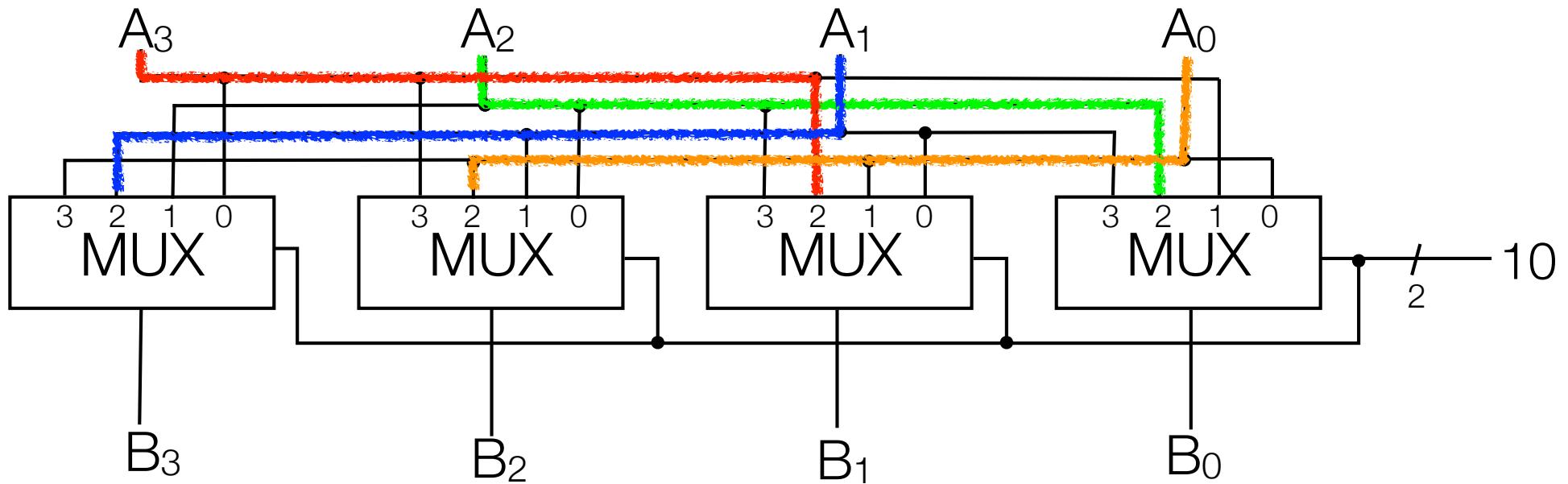Barrel Shift-Left Design with wraparound (using MUXs)




- Basic form of design: Each A_i feeds into each MUX connecting to B_j into input $(j-i) \bmod 4$
- Selector is 10 (i.e., 2 binary):
 - each MUX entry 2 is selected
 - $B_3 B_2 B_1 B_0 = A_1 A_0 A_3 A_2$


L-R Shift Circuit with Rollout

- k-bit data value entered as input
- $\ell = 2$ Specifies action

S_1	S_0	Action
0	0	none
0	1	none
1	0	shift-left (by 1 bit)
1	1	shift-right (by 1 bit)

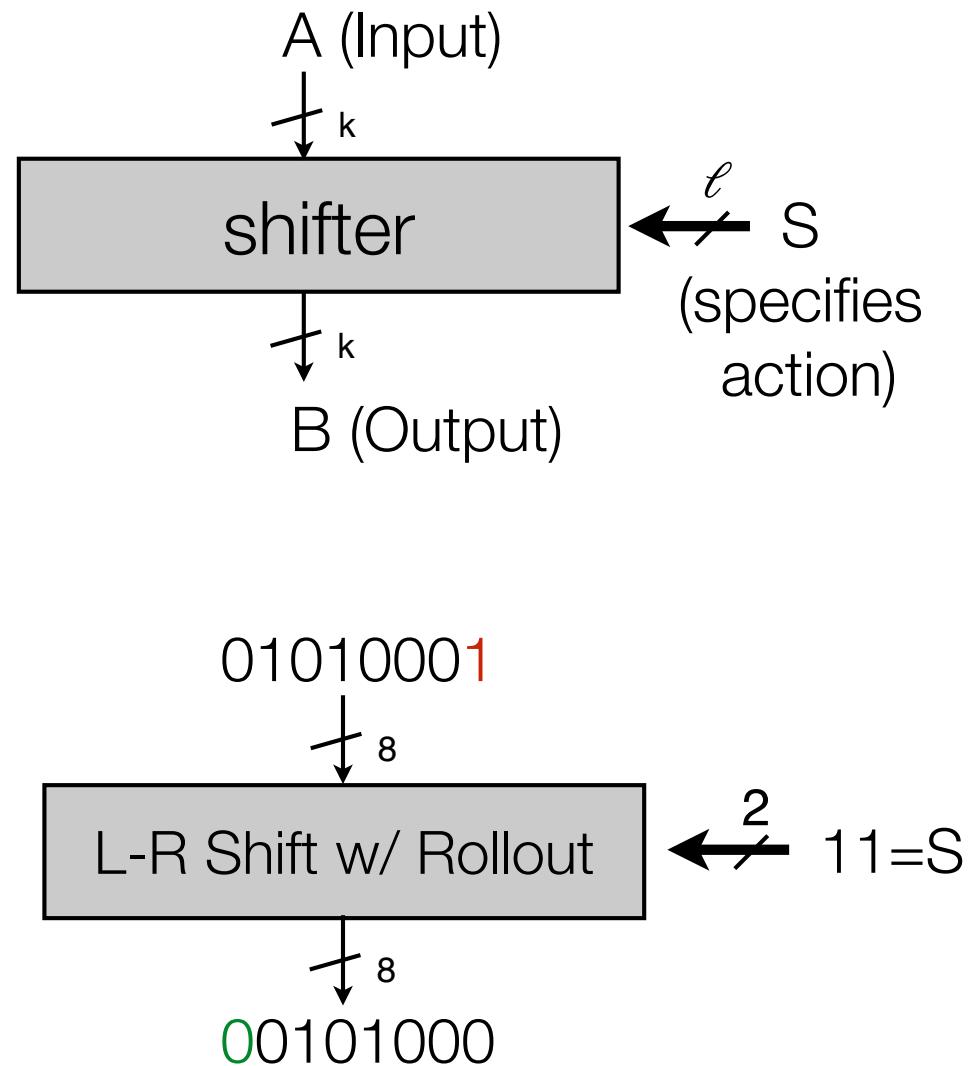


L/R Shift w/ Rollout

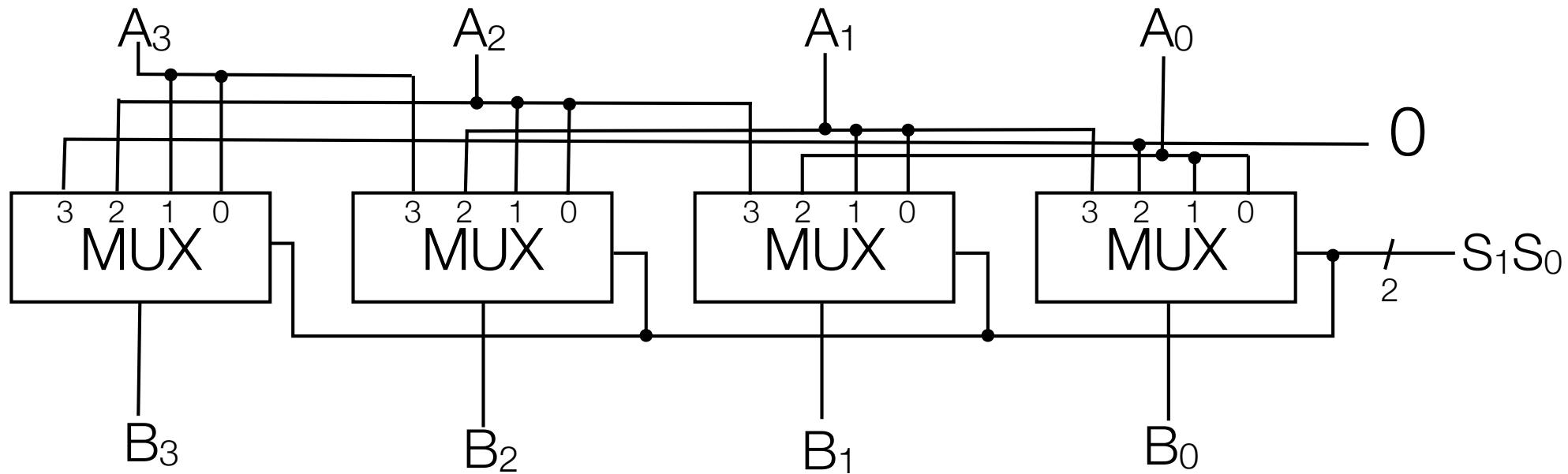

- Basic form of design:
 - 0 & 1 MUX selectors ($S_1 = 0$) feed A_i to B_i
 - 2 MUX selector feeds from left ($B_i = A_{i-1}$), 3 MUX from right ($B_i = A_{i+1}$)
 - Note 0 feeds (0's roll in when bits rollout)

L/R Shift w/ Rollout

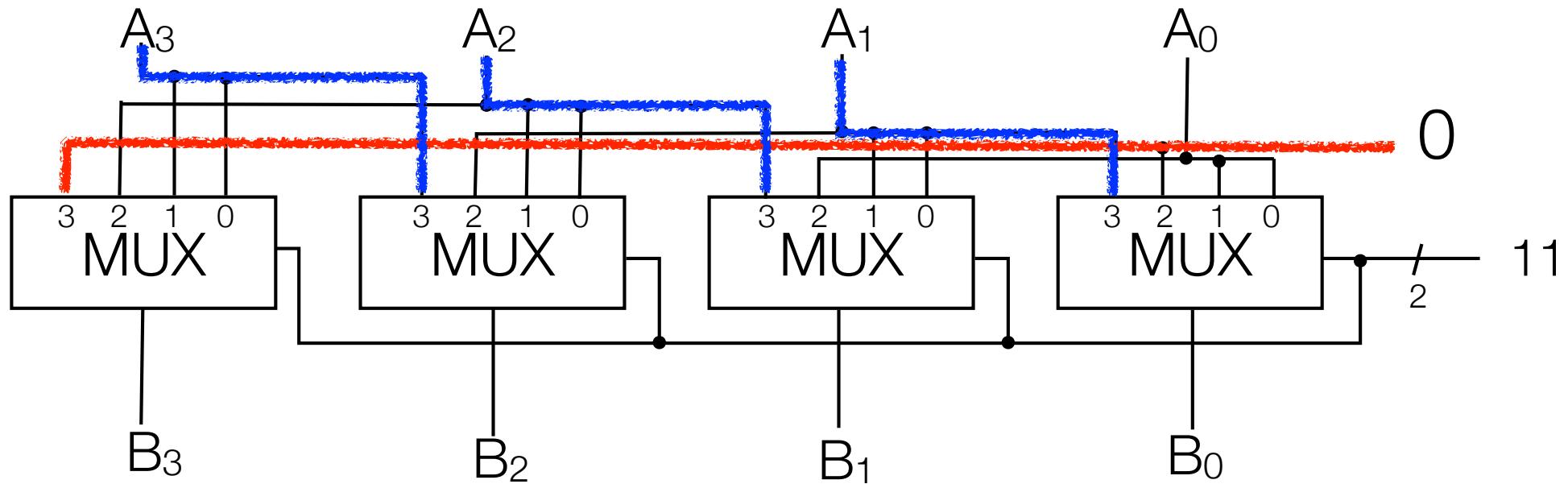


- Basic form of design:
 - 0 & 1 MUX selectors ($S_1 = 0$) feed A_i to B_i
 - 2 MUX selector feeds from left ($B_i = A_{i-1}$), 3 MUX from right ($B_i = A_{i+1}$)
 - Note 0 feeds (0's roll in when bits rollout)

General Code Converters


Code Converter

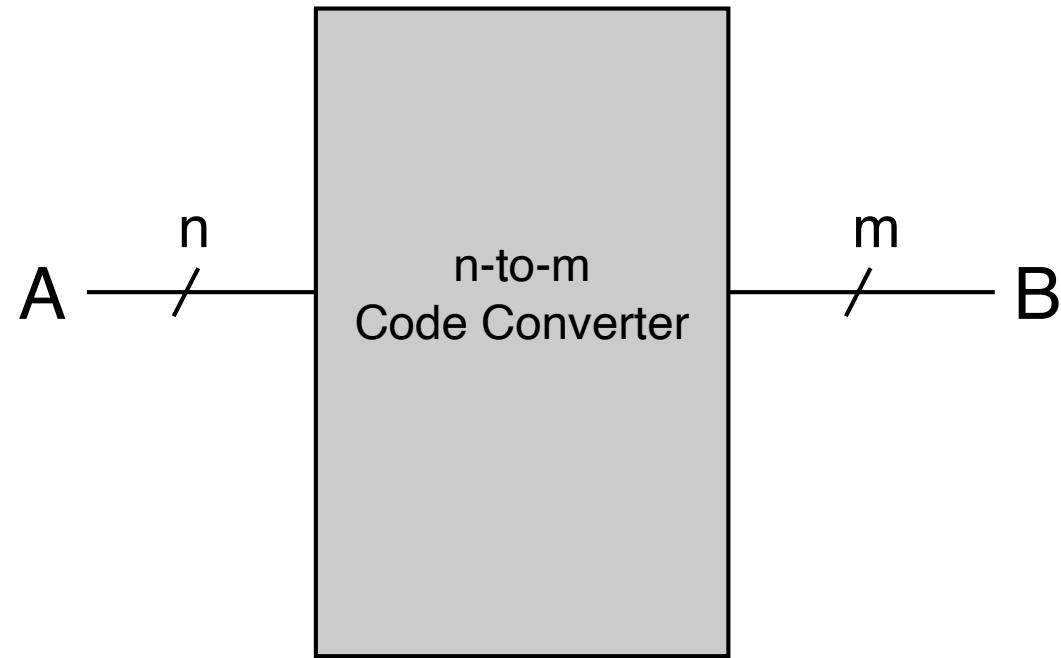- General term for a circuit that takes n input A, produces m output B
- n, m can be any values
- Each of the m outputs is a function of the n inputs



General Code Converter Example: LED digits

3-3

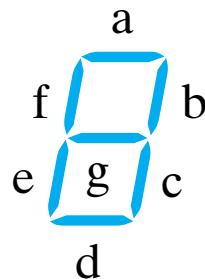


(a) Segment designation



(b) Numeric designation for display

Code conversion

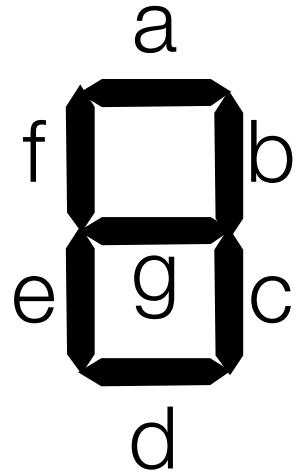


Input is 4 variables WXYZ,
representing Va, an unsigned binary
value (only care about 0-9)

Input Output

Val	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X


Code conversion

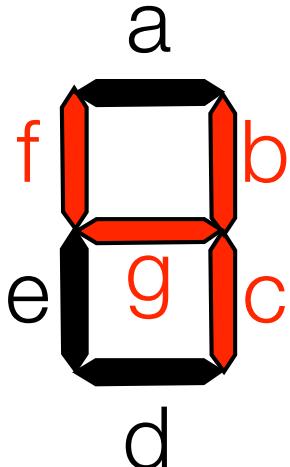


e.g., what outputs
“light up” when input
 $V_a=4$?

Val	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Code conversion

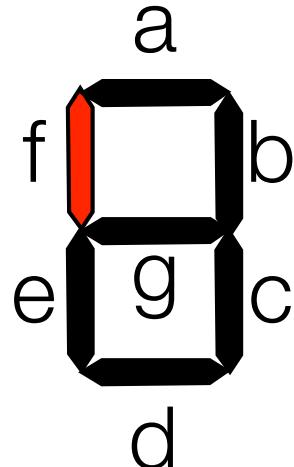


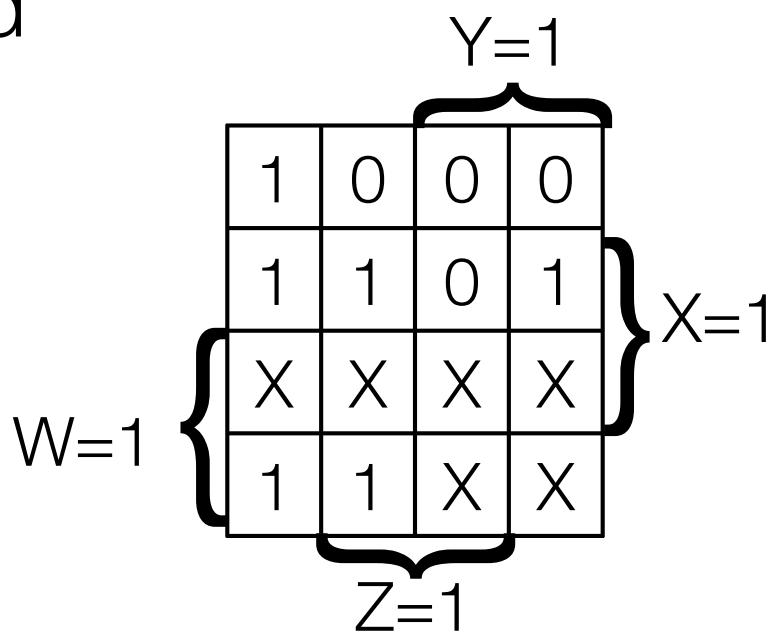For what values does output f “light up” for?




Val	W	X	Y	Z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1
X	1	0	1	0	X	X	X	X	X	X	X
X	1	0	1	1	X	X	X	X	X	X	X
X	1	1	0	0	X	X	X	X	X	X	X
X	1	1	0	1	X	X	X	X	X	X	X
X	1	1	1	0	X	X	X	X	X	X	X
X	1	1	1	1	X	X	X	X	X	X	X

Algebra and Circuit for “f”

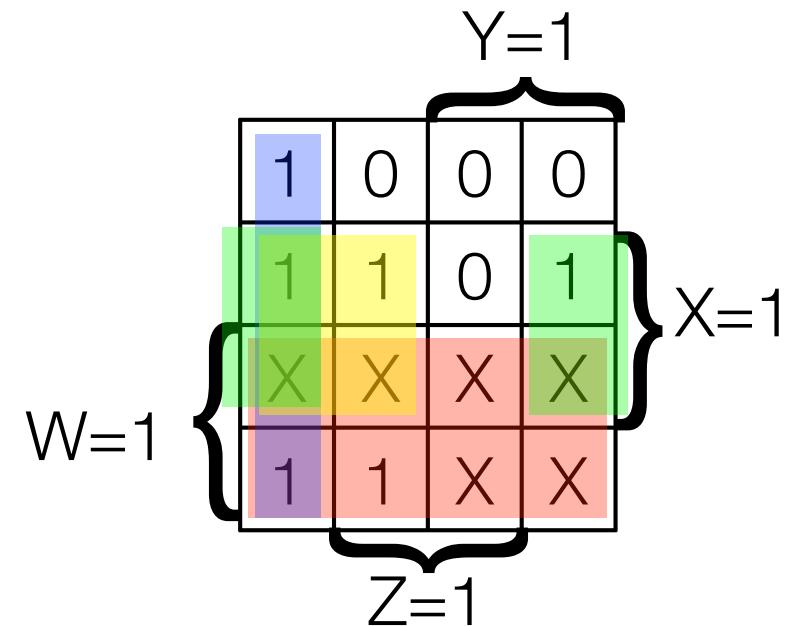
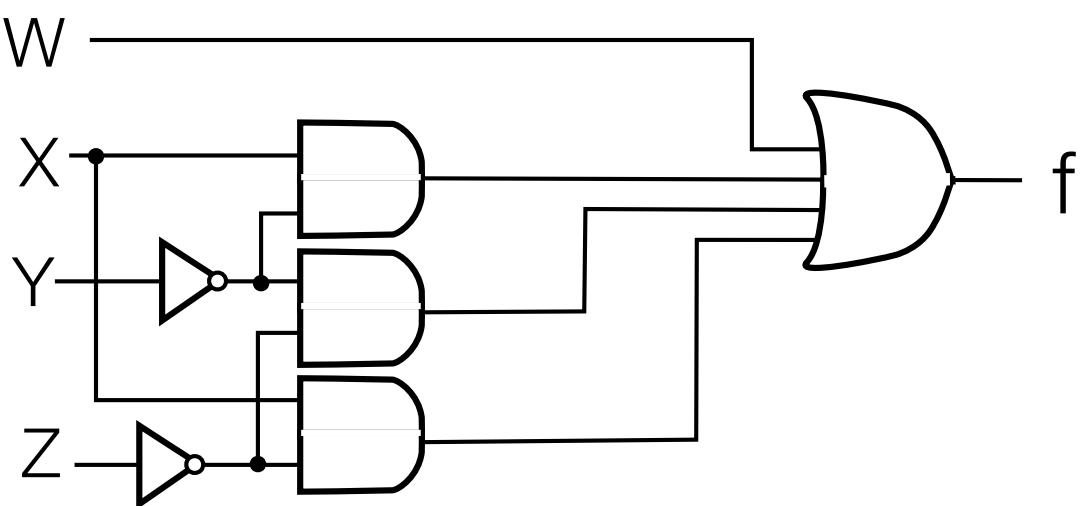
$$f = W + X\bar{Y} + \bar{Y}\bar{Z} + X\bar{Z}$$




Adder Circuits

(Hierarchical Approach)

(Unsigned) Adder Circuit (High-level)

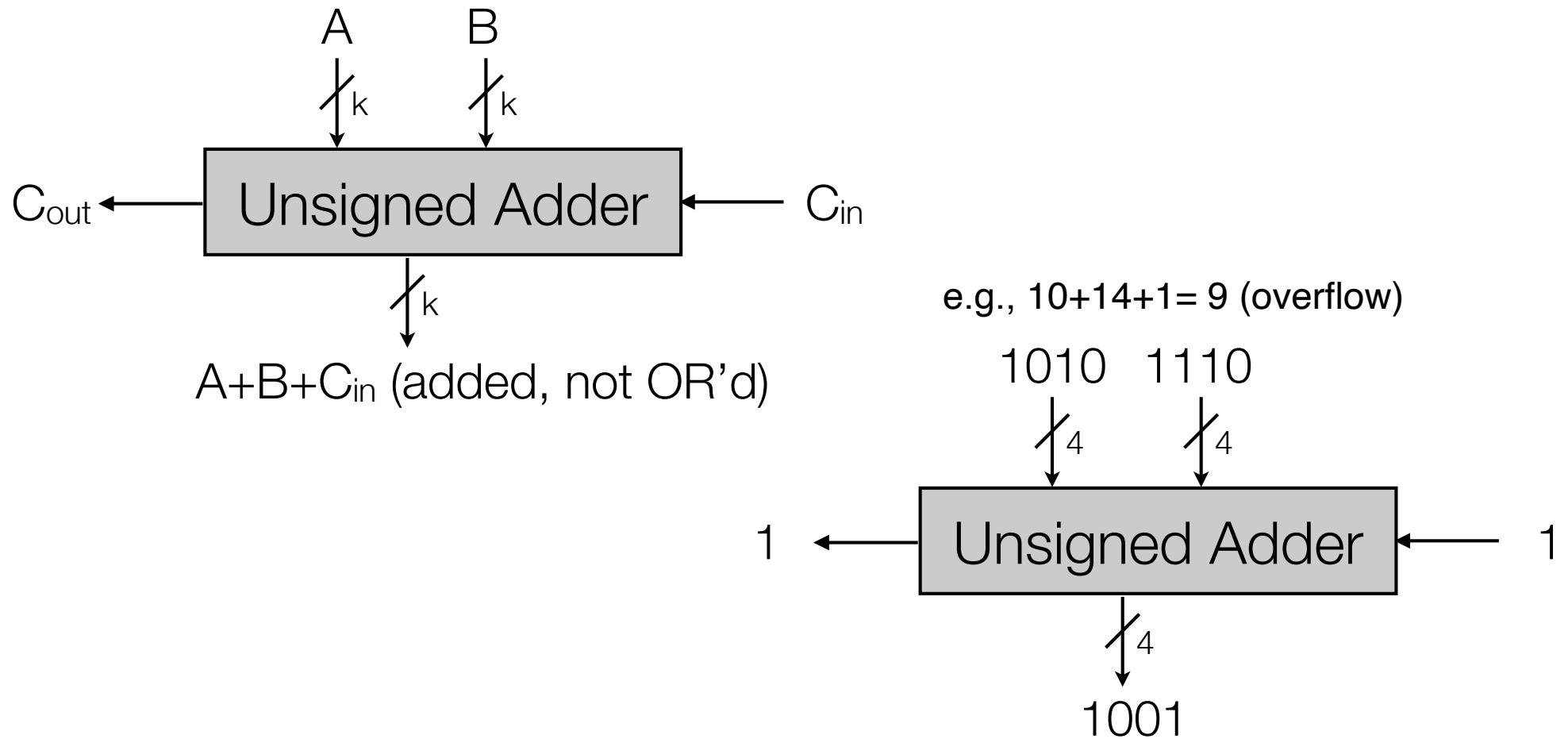- Two k-bit data values, A and B, and 1 bit C_{in} (carry-in) entered as input
- output is k-bit $A+B+C_{in}$ (unsigned binary addition), and 1-bit C_{out} (carry-out), i.e., the overflow




Addition: The Half-Adder

- Addition of 2 bits: A & B produces a summand (S) and carry (C)

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = A \oplus B$$

$$C = AB$$

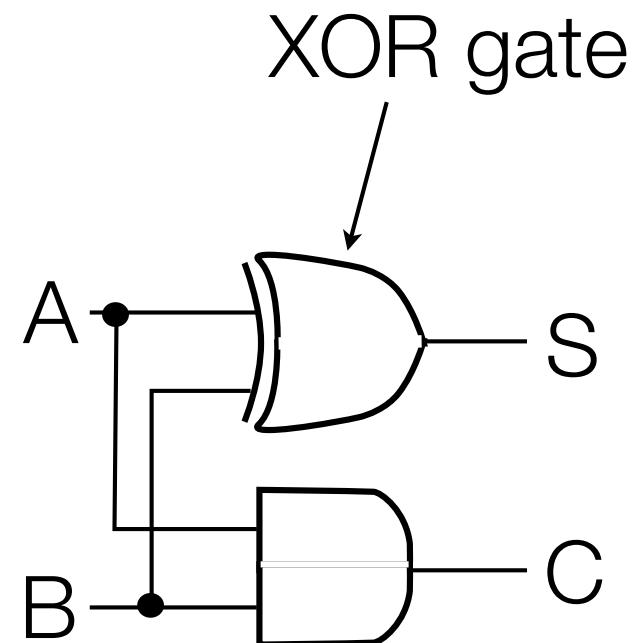


- But to do addition, we really need to add 3 bits at a time (to account for carries), e.g.,

$$\begin{array}{r} 011 \leftarrow \text{carry bits} \\ + 1011 \\ \hline 10100 \end{array}$$

The Full Adder



- Takes as input 2 digits (A&B) and a previous carry (P)

P	A	B	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

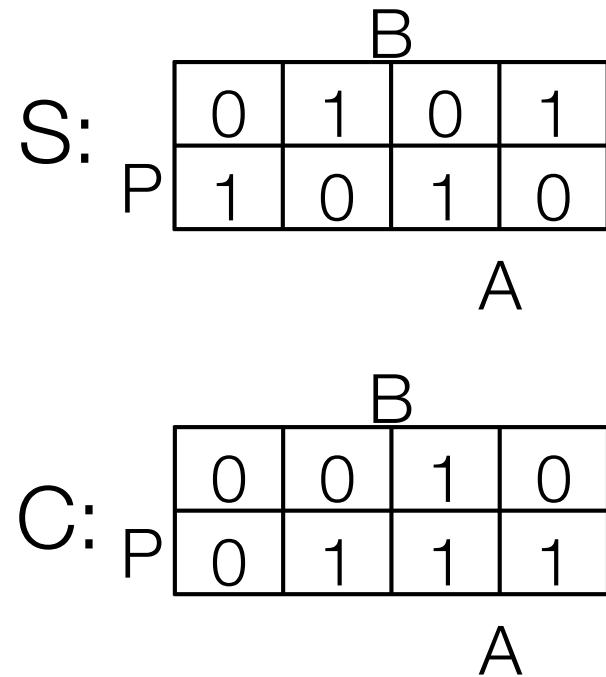


$$S = A \oplus B \oplus P$$

$$C = AB + AP + BP$$

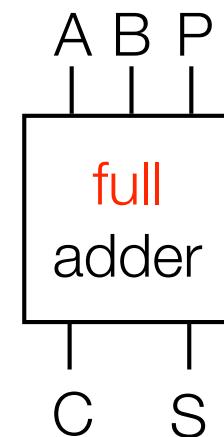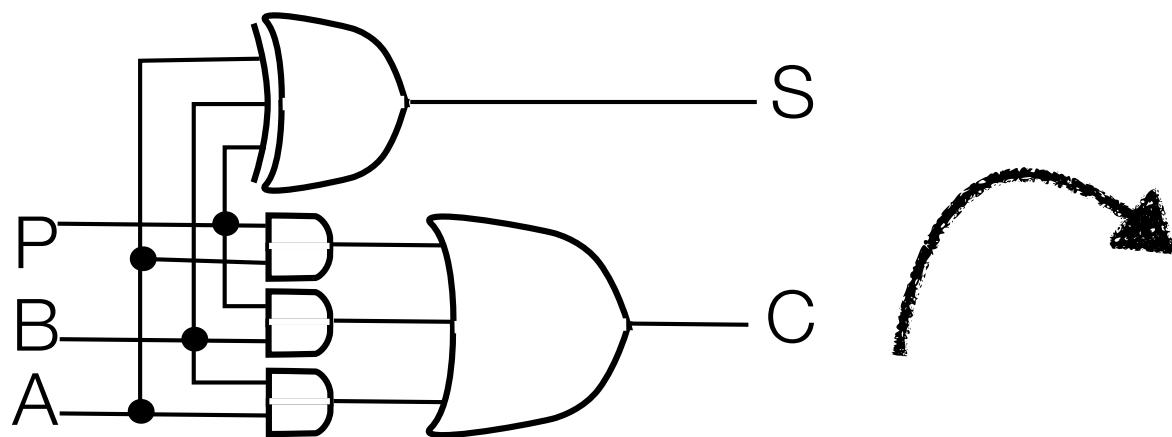

5-bit ripple carry adder

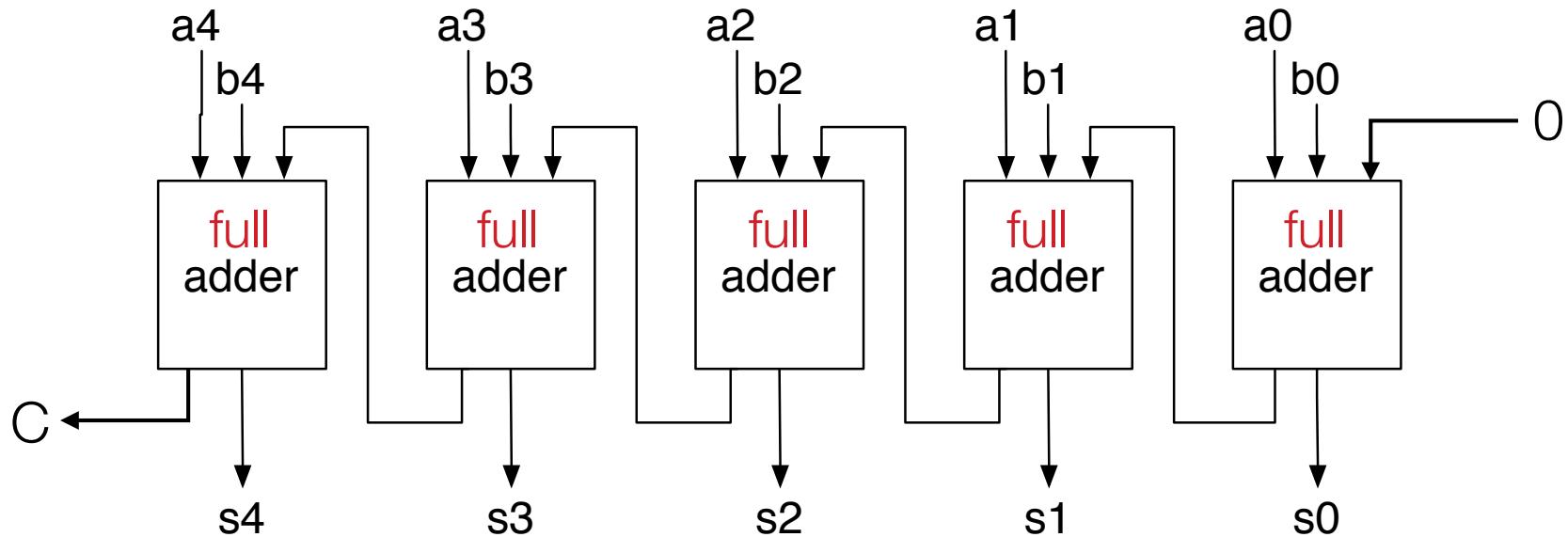Computes $a_4a_3a_2a_1a_0 + b_4b_3b_2b_1b_0$



- Note how computation “ripples” through adders from right to left
 - Each full adder’s has depth 2 (inputs pass through 2 gates to reach output)
 - Full adder that computes s_i cannot “start” its computation until previous full adder computes carry
 - The longest depth in a k -bit ripple carry adder is $2k$

Subtraction review (2's complement)

- Suppose A and B are 2's complement numbers:
- To perform A-B:
 - Version 1:
 - Negate B:
 - $B_F = \text{Flip Bits in } B$
 - $Y = B_F + 1, Y = -B$
 - return $A+Y$

Subtraction review (2's complement)


- Suppose A and B are 2's complement numbers:
- To perform A-B:
 - Note: $A+Y = A+(B_F+1) = (A+B_F)+1$
- Version 1:
 - Negate B:
 - $B_F = \text{Flip Bits in } B$
 - $Y = B_F+1, Y=-B$
 - This is how our add/subtract circuit will do it...
- return $A+Y$

XOR refresher

- $X \oplus 0 = X$
- $X \oplus 1 = \overline{X}$ (i.e., XOR'ing with 1 flips the bit)

Adder/subtractor for #'s in 2's complement form

4-7

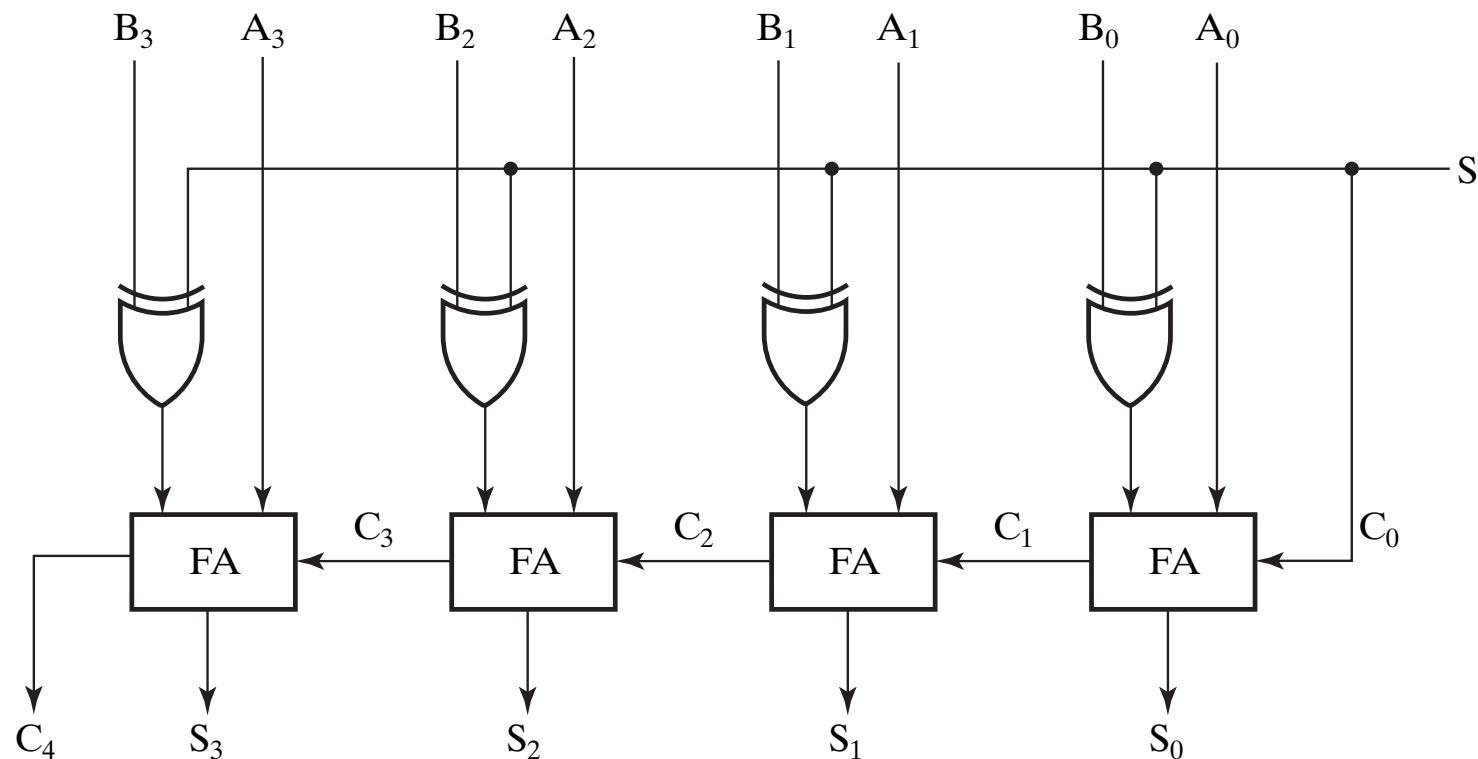


S=0: B
unchanged,
C₀=0: add

S=1: B
complemented,
C₀=1 (bits flipped
and 1 added):
subtract

Overflow computation in 2's comp add/subtractor

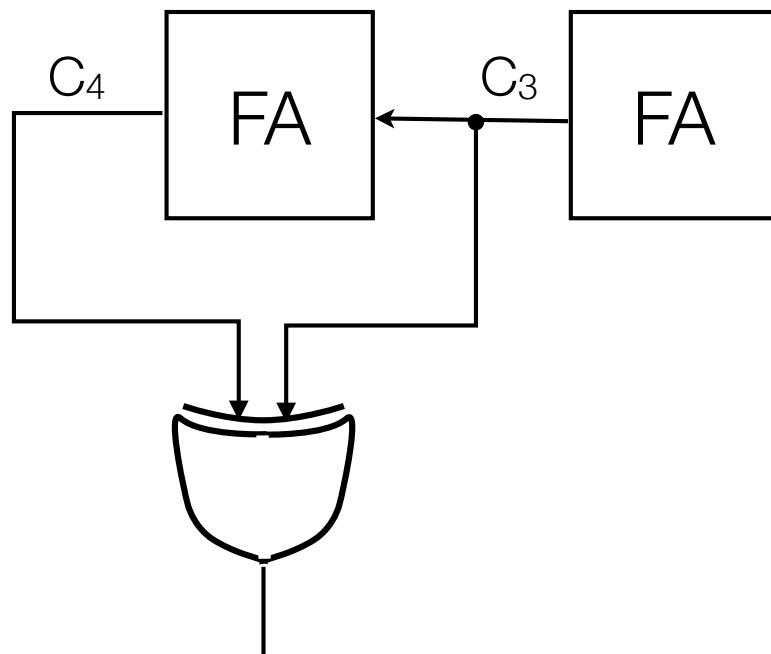- Recall: for 2's complement, overflow if 2 most significant carries differ



=0 then no overflow, =1 then overflow

Ripple Carry Adder


v

Carry Lookahead Adder

We built a Ripple-Carry adder: what is circuit depth?

$$A_3 A_2 A_1 A_0 + B_3 B_2 B_1 B_0 = S_3 S_2 S_1 S_0$$

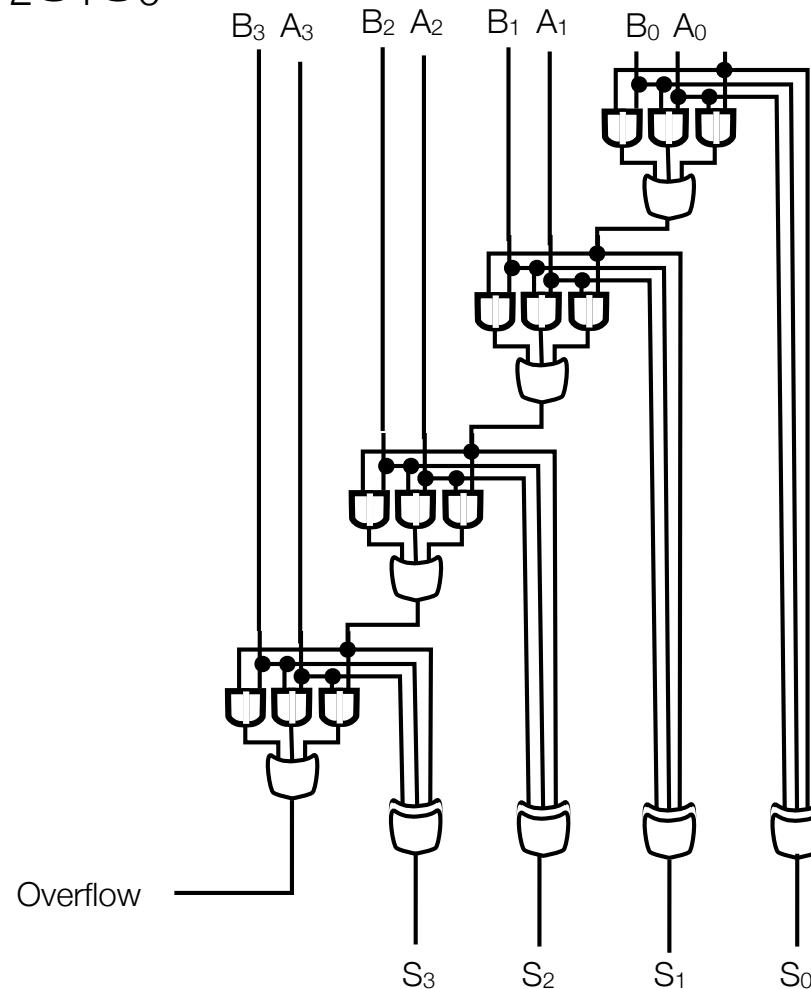
- Depth of a circuit is the longest (most gates to go through) path



We built a Ripple-Carry adder: what is circuit depth?

$$A_3 A_2 A_1 A_0 + B_3 B_2 B_1 B_0 = S_3 S_2 S_1 S_0$$

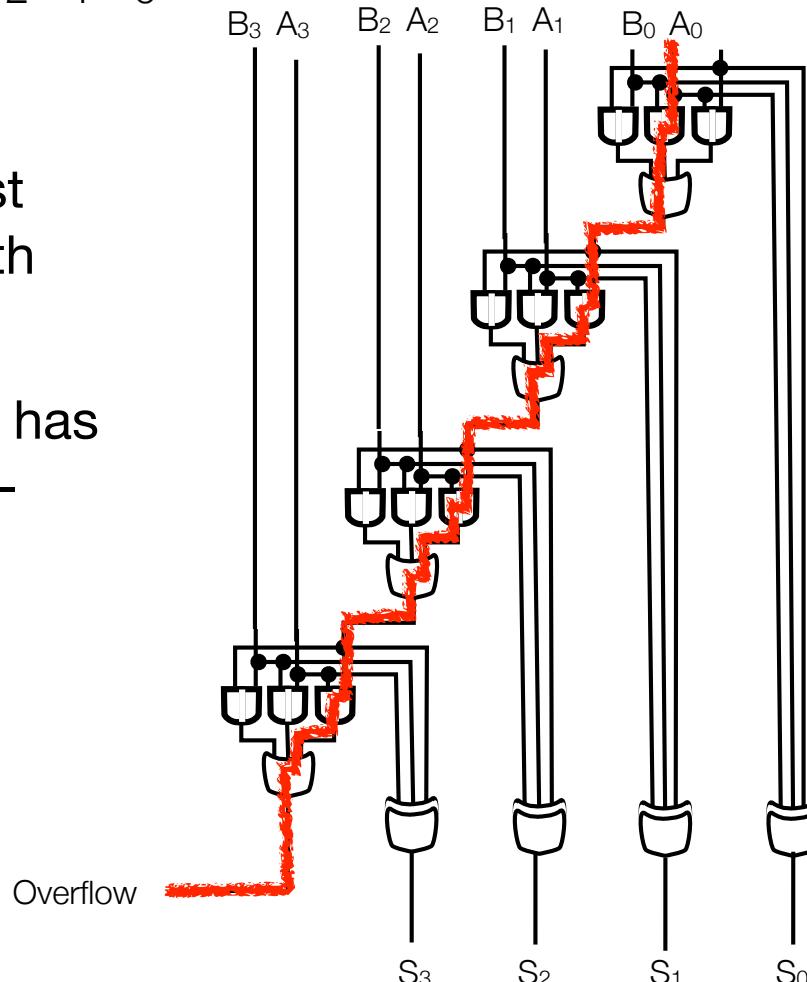- Depth of a circuit is the longest (most gates to go through) path
- Each carry computation stage has depth 3 (parallel ANDs, then 3-input OR)
- In general, C_k has depth $3k$ in Ripple-Carry Adder
- Linear depth!!!



Q: When does the i^{th} column yield a carry?

Column	$i+1$	i	$i-1$	$i-2$...
A					
B					

- When does column i produce a carry of 1?

Q: When does the i^{th} column yield a carry?

Column	$i+1$	i	$i-1$	$i-2$...
A		1			
B		1			

- When does column i produce a carry of 1?
- Both A and B are 1 in the i^{th} column: definitely have carry

Q: When does the i^{th} column yield a carry?

Column	$i+1$	i	$i-1$	$i-2$...
A		0			
B		0			

- When does column i produce a carry of 1?
- Both A and B are 0 in the i^{th} column: definitely no carry

Q: When does the i^{th} column yield a carry?

Column	$i+1$	i	$i-1$	$i-2$	\dots
A		1 or 0			
B		0 or 1			

- When does column i produce a carry of 1?
- A and B differ in i^{th} column: column i carries if and only if column $i-1$ carries

$$\begin{array}{ccccccc} 1 & & 0 & \text{or} & 1 & & 1 \\ 1 & & 1 & \text{or} & 0 & & 1 \\ & & & & & & \end{array}$$

$$\bullet \text{ i.e., } C_i = A_i B_i + (A_i \oplus B_i) A_{i-1} B_{i-1} + (A_i \oplus B_i)(A_{i-1} \oplus B_{i-1}) A_{i-2} B_{i-2} + \dots$$

$$\begin{array}{ccccc} 0 & & 0 & \text{or} & 1 \\ \text{or} & & \text{or} & & 0 \\ 1 & & 1 & & 1 \\ & & & & \end{array}$$
$$+ (A_i \oplus B_i)(A_{i-1} \oplus B_{i-1}) \dots (A_2 \oplus B_2)(A_1 \oplus B_1) A_0 B_0$$

Depth to produce C_k ?

1 0 or 1 1 0 or 1 0 or 1 1
1 1 or 0 1 1 or 0 1 or 0 1

- i.e., $C_k = A_k B_k + (A_k \oplus B_k) A_{k-1} B_{k-1} + (A_k \oplus B_k)(A_{k-1} \oplus B_{k-1}) A_{k-2} B_{k-2} + \dots$

0 or 1 0 or 1 0 or 1 0 or 1 1
1 or 0 1 or 0 1 or 0 1 or 0 1

$$+ (A_k \oplus B_k)(A_{k-1} \oplus B_{k-1}) \dots (A_2 \oplus B_2)(A_1 \oplus B_1) A_0 B_0$$

- What is depth of above circuit?

$$\left. \begin{array}{l} (3) \text{ XOR pairwise-AND (1)} \\ \text{AND at most } k+1 \text{ of the above together } (\log_2(k+1)) \\ \text{OR at most } k+1 \text{ of the above together } (\log_2(k+1)) \end{array} \right\} \begin{array}{l} 3 \\ + \\ \log_2(k+1) = 3 + 2 \log_2(k+1) \\ + \\ \log_2(k+1) \end{array}$$

Final Thoughts on Carry Lookahead Adder


- Showed C_k can be computed with depth $3 + 2 \log_2(k+1)$
- Actually can be reduced to depth $1 + 2 \log_2(k+1)$
 - (XORs can be replaced by ORs,
 - e.g., consider $A_iB_i + (A_i \oplus B_i)A_{i-1}B_{i-1}$: replace with $A_iB_i + (A_i + B_i)A_{i-1}B_{i-1}$
 - The product term A_iB_i already forces expression true when $A_i=B_i=1$
 - Depth of $k-1^{\text{st}}$ sum bit adds depth 2 to perform XOR
 - Bottom line: depth $3 + 2 \log_2(k+1) << 3k$ for large k
 - e.g., $k=32$, 15 vs 96
 - e.g., $k=64$, 17 vs 192

Contraction

Contraction

- Simplification of a circuit through constant input values.
- e.g., suppose you want to build an “increment” circuit that adds 1 to an input value
 - step 1: take an all-purpose adder
 - step 2: fix one of the inputs to equal “1”
 - step 3: reduce the circuitry

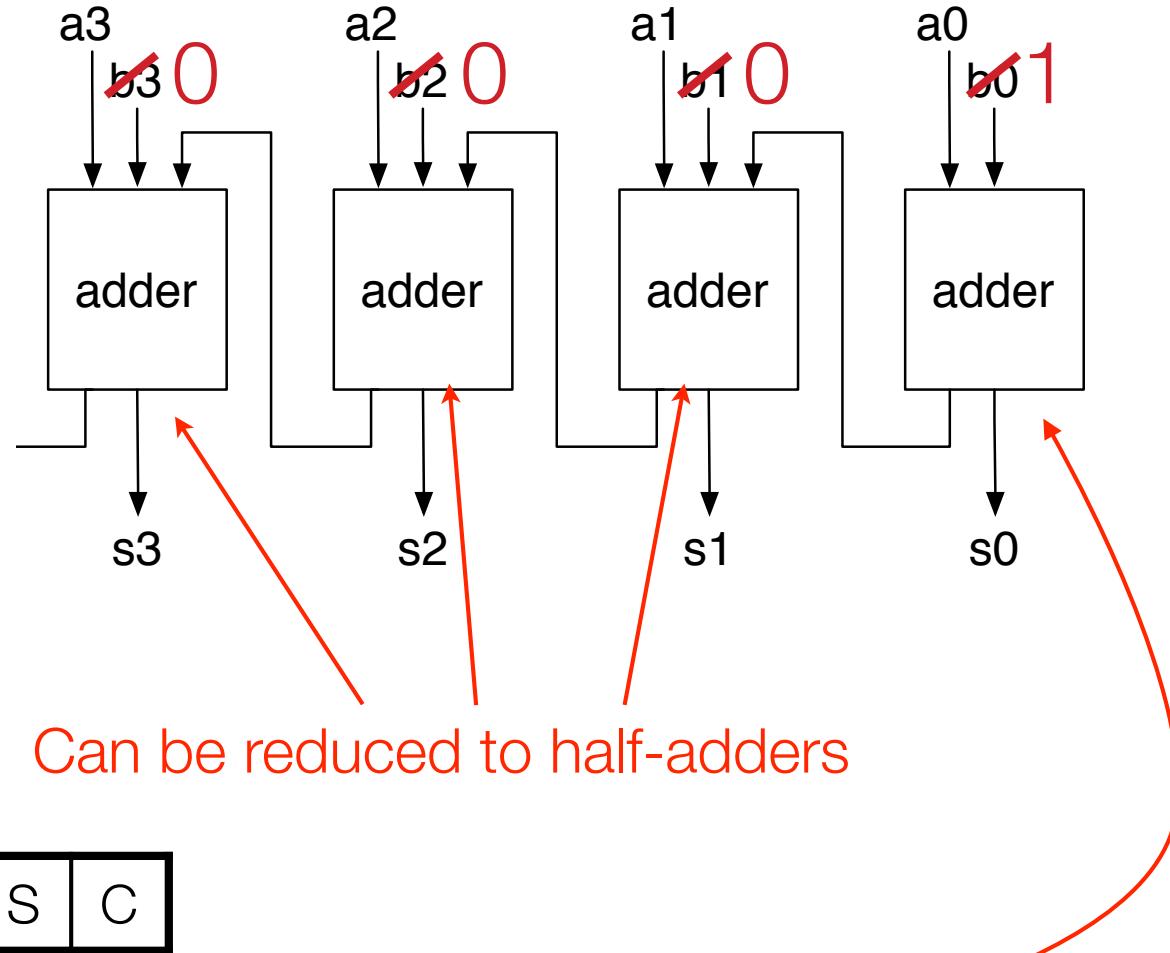Contraction example: adder to incrementer




Incrementer
circuit

a_0	S	C
0	1	0
1	0	1

$$S_0 = \overline{a}_0, C_0 = a_0$$

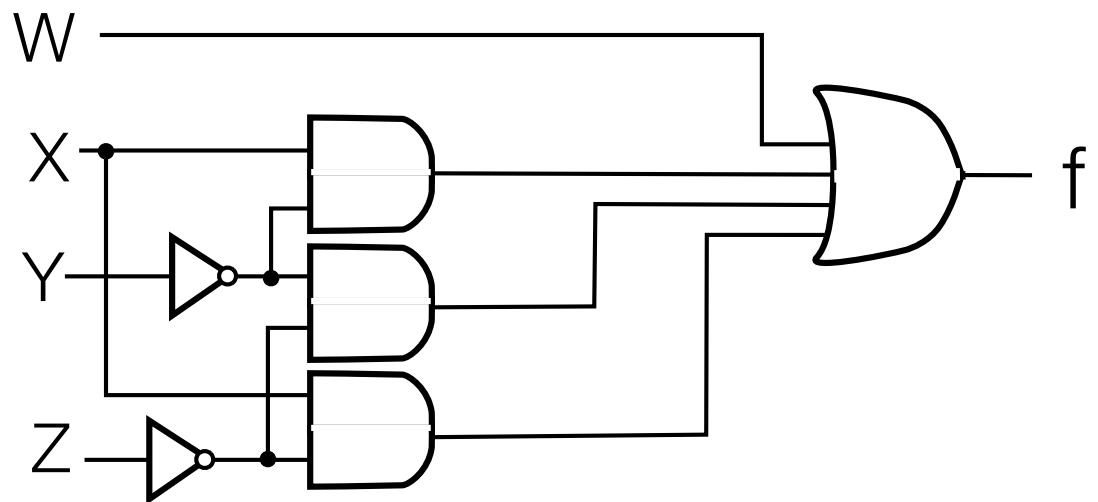
Example 2 of contraction

Suppose: use circuit below in cases where $X=0$ always



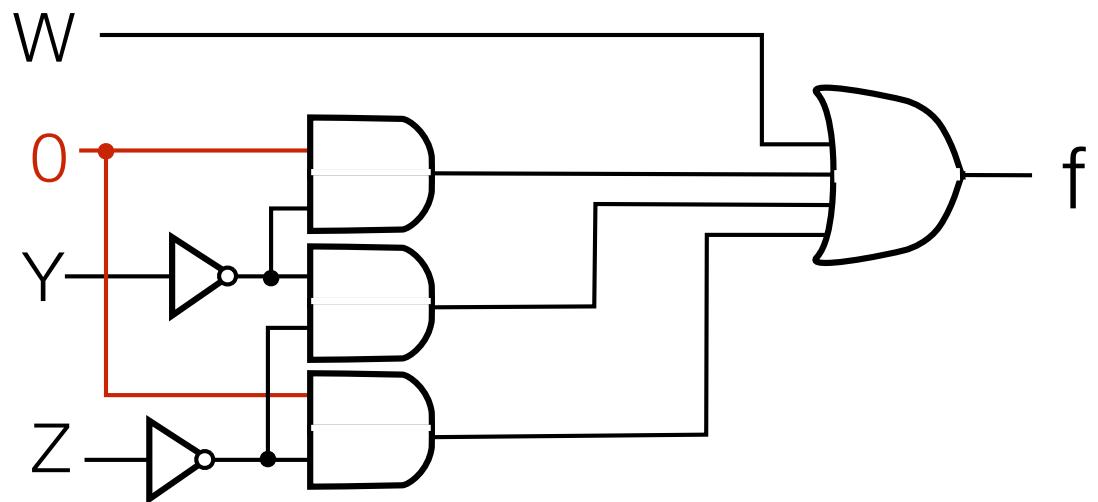
Example 2 of contraction

Suppose: use circuit below in cases where $X=0$ always



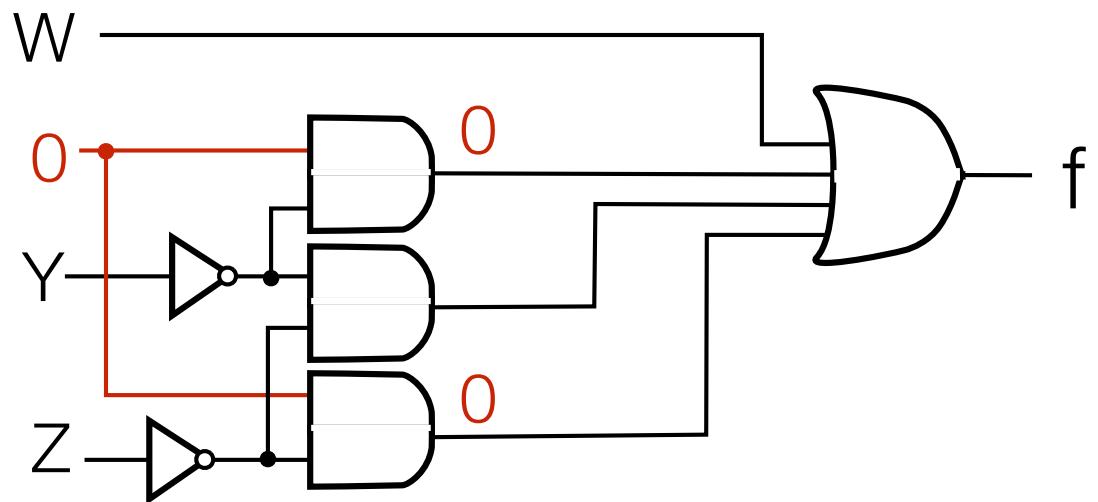Example 2 of contraction


Suppose: use circuit below in cases where $X=0$ always



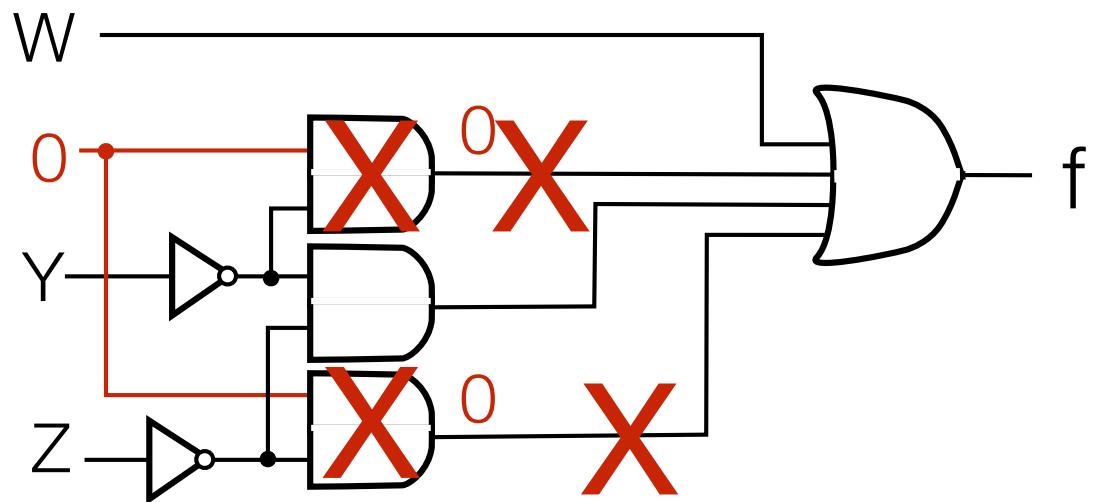Example 2 of contraction

Suppose: use circuit below in cases where $X=0$ always

Can remove gates whose outcome is known (is constant)



Example 2 of contraction

Suppose: use circuit below in cases where $X=0$ always

